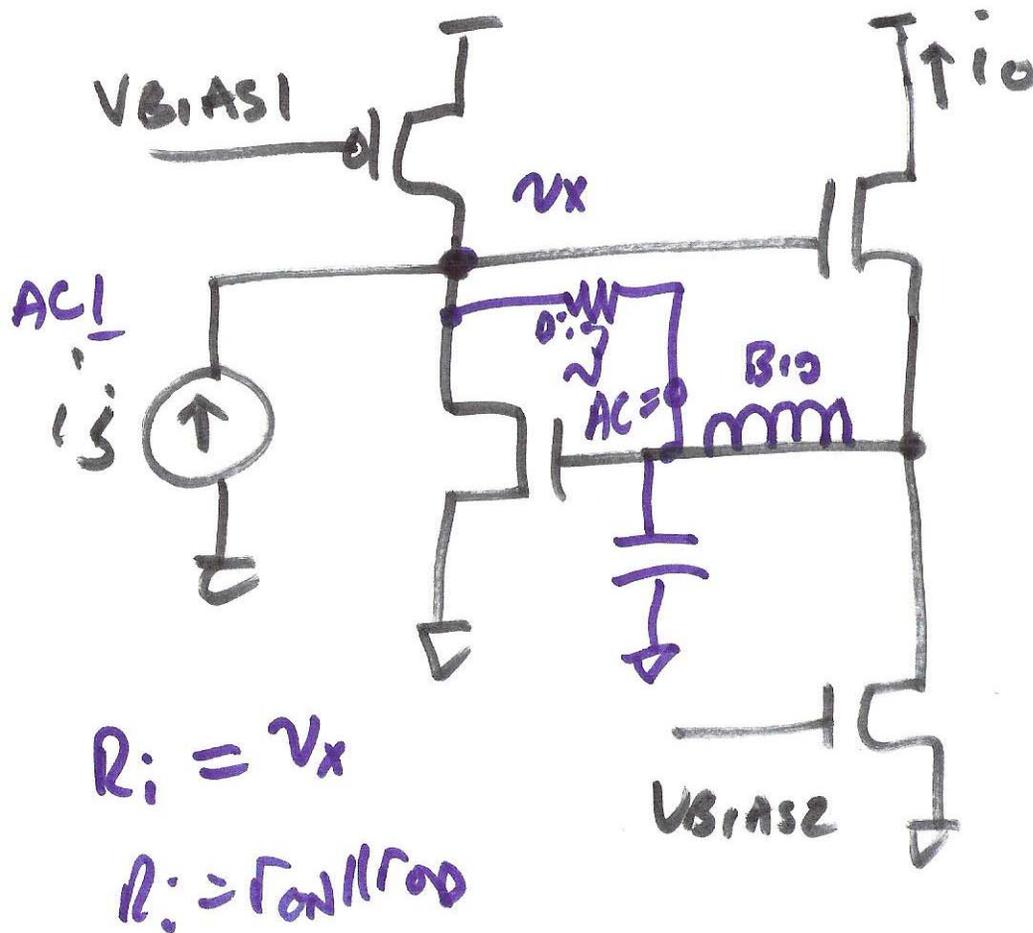


Lecture 7 Sept. 13, 2011




$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}}$$

$\beta A_{OL} = \text{loop gain}$

$$\beta A_{OL} = -1 \rightarrow |A_{OL}| < 1$$

UNstable f.b. system!

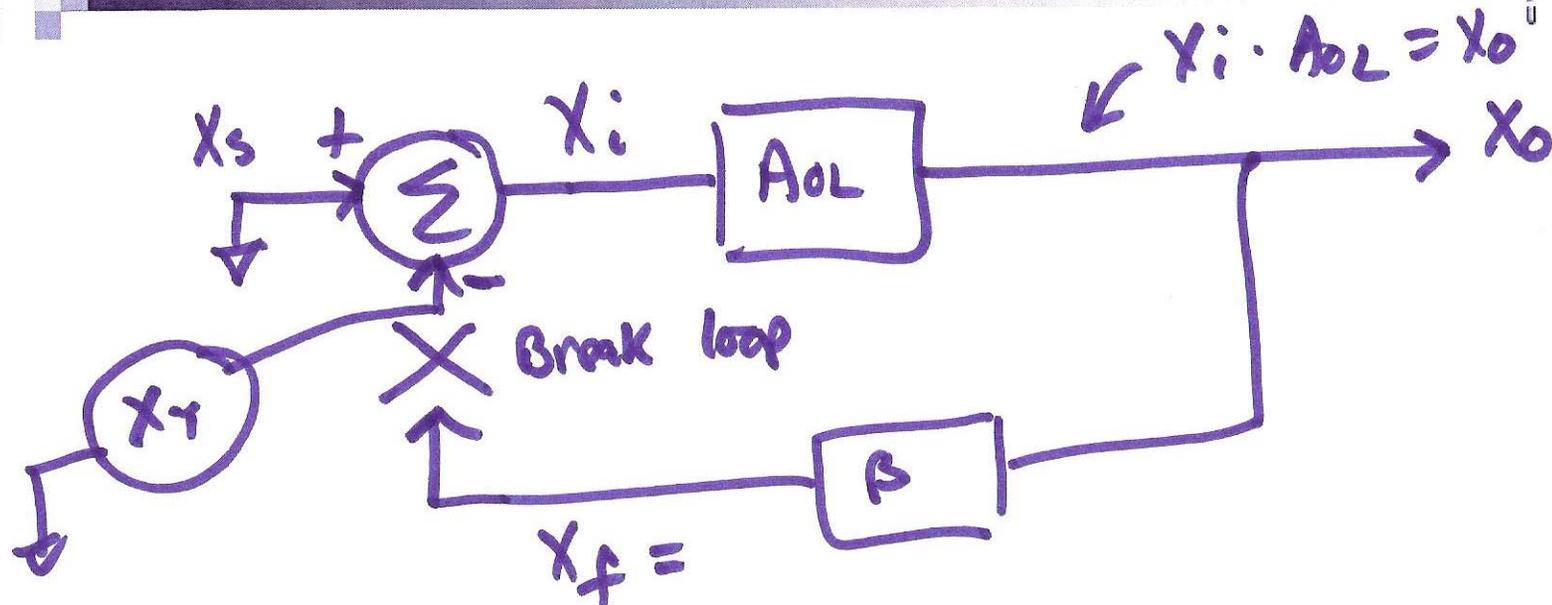plotting loop gain  
can tell you how  
stable your system  
is.



$$X_f = X_o \cdot \beta$$


$$X_f = X_i \cdot A_{OL} \cdot \beta \rightarrow \frac{X_f}{X_i} = A_{OL} \cdot \beta$$

$$X_f = -X_\gamma \cdot A_{OL} \cdot \beta$$

$$\frac{X_f}{X_i} = A_{OL} \cdot \beta$$

$$\frac{X_f}{X_\gamma} = \frac{-A_{OL} \cdot \beta}{\text{loop gain}}$$

2)

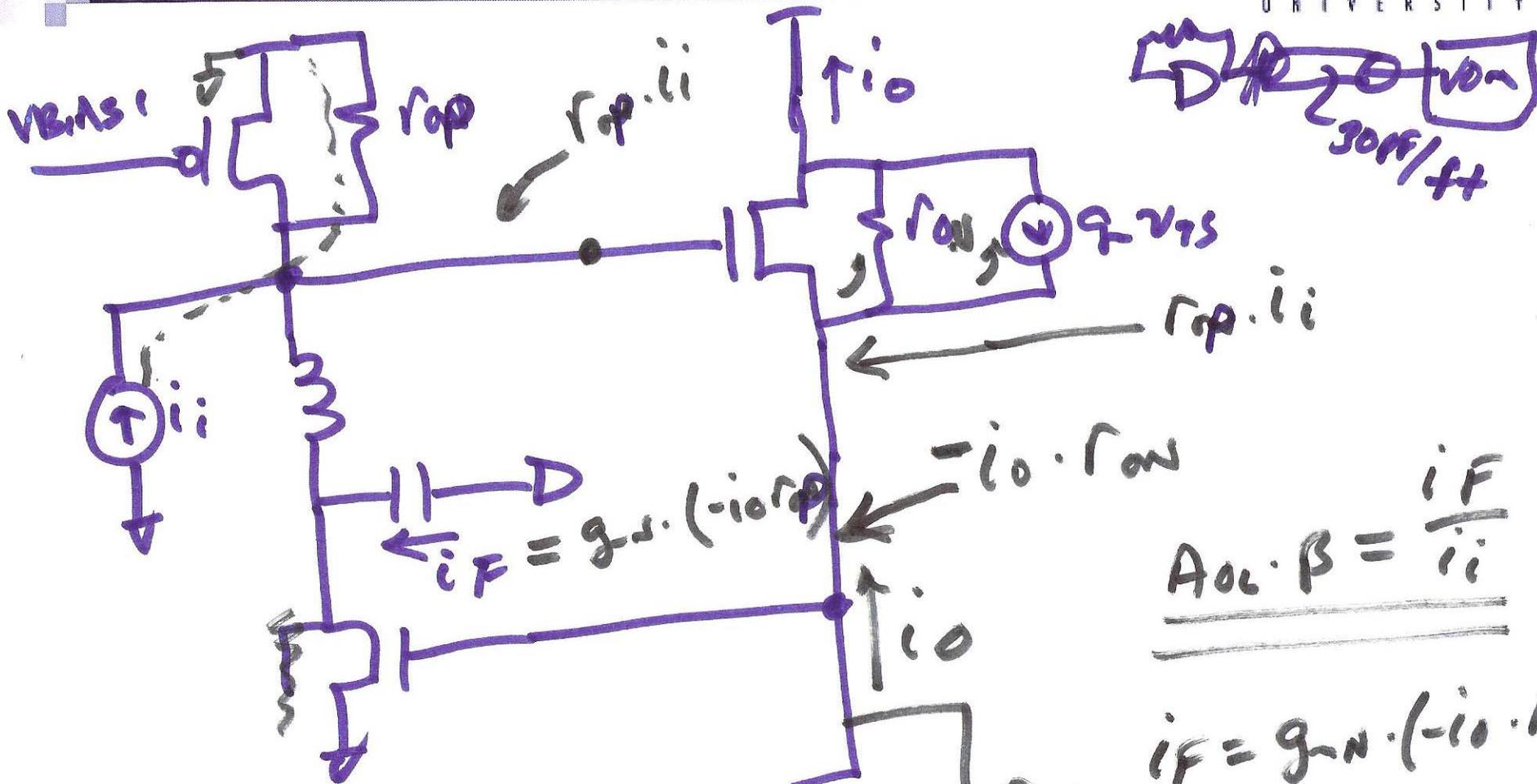

$$i_F = g_{mN} \cdot r_{op} \cdot i_i$$

$$\frac{i_F}{i_i} = g_{mN} \cdot r_{op} = 25 \rightarrow \underline{\underline{28dB}}$$

3)


$$\underline{\underline{A_{OL} \cdot \beta = \frac{i_F}{i_i}}}$$



$$i_F = g_{mN} \cdot (-i_o \cdot r_{on})$$


$$i = \frac{v}{j\omega L}$$

$$v = j\omega L \cdot i$$

$$i = \frac{v}{j\omega L}$$

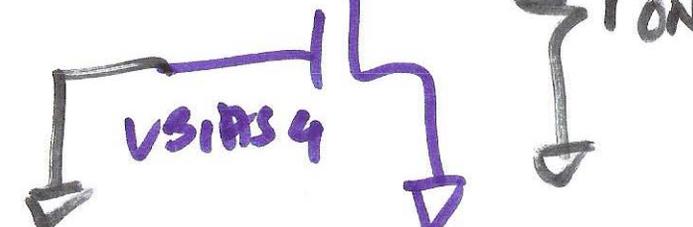

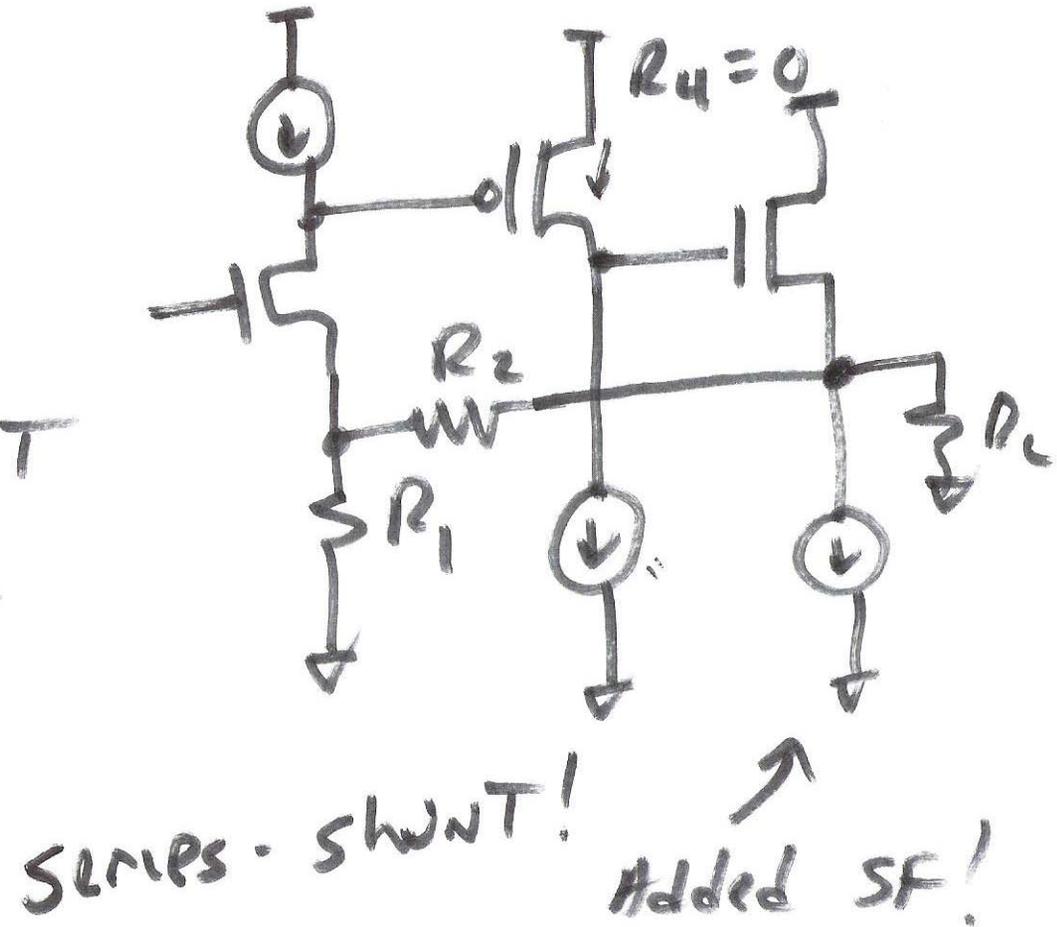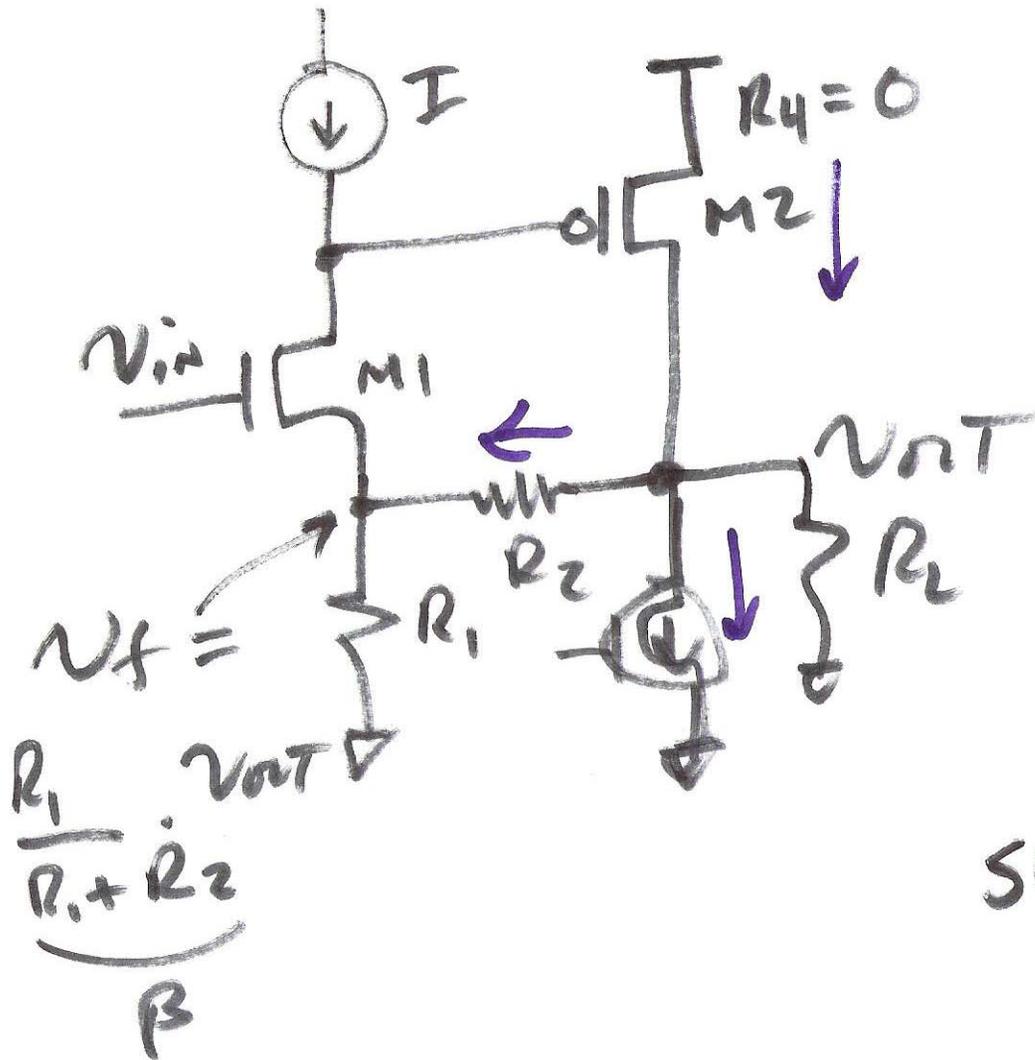

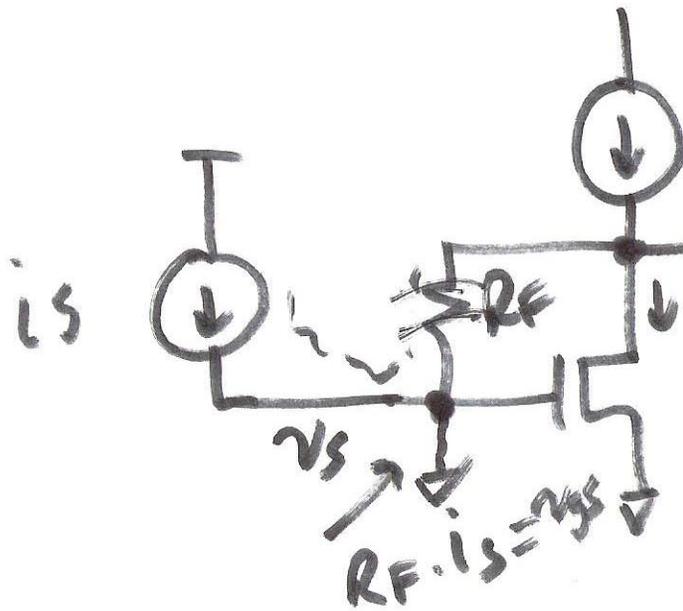

$$R_F g_m \cdot R_F \cdot i_s = v_{out}$$

$$\frac{v_{out}}{i_s} = g_m R_F^2$$

SHUNT - SHUNT  
I V

$$\frac{v_{out}}{v_s} = g_m R_F$$

TRANSIMPEDANCE AMP

we will return to this in Ch. 8.

5)