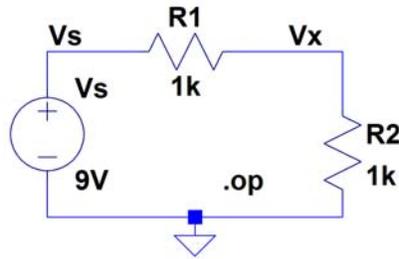


H.W. #2 EE 220 Fall 2016

Show your work for credit!

- Write a text file containing the LTspice netlist for the following circuit. Verify that the simulation results match your hand calculations. (3 points)



- Find the voltages and currents in each of the following circuits. Verify your answers with LTspice. (9 points)

