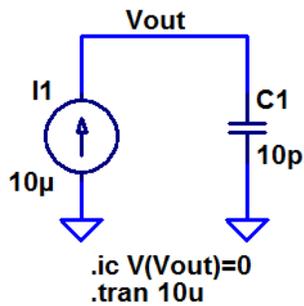


Quiz #10 EE 220 Fall 2016 Name: _____

Closed book and notes.

Show your work for credit!

1. Plot V_{out} vs. time for the following circuit for times ranging from 0 to 10 μs . Assume that the capacitor is initially discharged. Note that to get credit you need to correctly label your plot's axis. (2 points)



2. The following current is applied to a discharged 10 pF capacitor. Plot the voltage across the capacitor **on this same plot** using the right side of the plot to indicate the capacitor's voltage. Hint: from 0 to 1 μs the voltage across the capacitor is 0 V. (3 points)

