

Quiz #11 EE 220 Fall 2016 Name: _____

Closed book and notes.

Show your work for credit!

1. Plot V_r for the following simulation. Write an equation that describes V_r . Do not derive the equation, simply write it. (5 points)

