

Quiz #2 EE 220 Fall 2016 Name: _____

Closed book and notes.

Show your work for credit!

1. Determine the current through V_s . Again, show your work for credit. (5 points)

