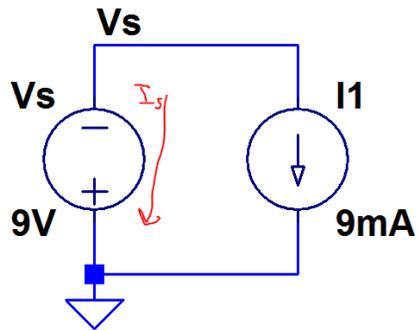


Quiz #5 EE 220 Fall 2016 Name: _____

Closed book and notes.

Show your work for credit!

1. What is I_s as defined in the direction seen below? Just write the answer. (1 point)



2. Find V_s and V_x in the following circuit. (4 points)

