

Quiz #7 EE 220 Fall 2016 Name: \_\_\_\_\_

Closed book and notes.

Show your work for credit!

1. Find  $V_{out}$  in the following circuit. Note that H1 is a current-controlled voltage source (CCVS) also known as a current-dependent voltage source. (5 points)

