

Quiz #9 EE 220 Fall 2016 Name: _____

Closed book and notes.

Show your work for credit!

1. Find the op-amp's output voltage in the following circuit. (5 points)

