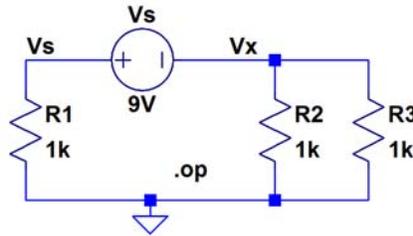


H.W. #2 EE 220 Spring 2017

Show your work for credit and place a box around each of your answers!

- Write a text file containing the LTSpice netlist for the following circuit. Verify that the simulation results match your hand calculations. (3 points)



- Find the voltages and currents in each of the following circuits. Verify your answers with LTSpice. (9 points)

