
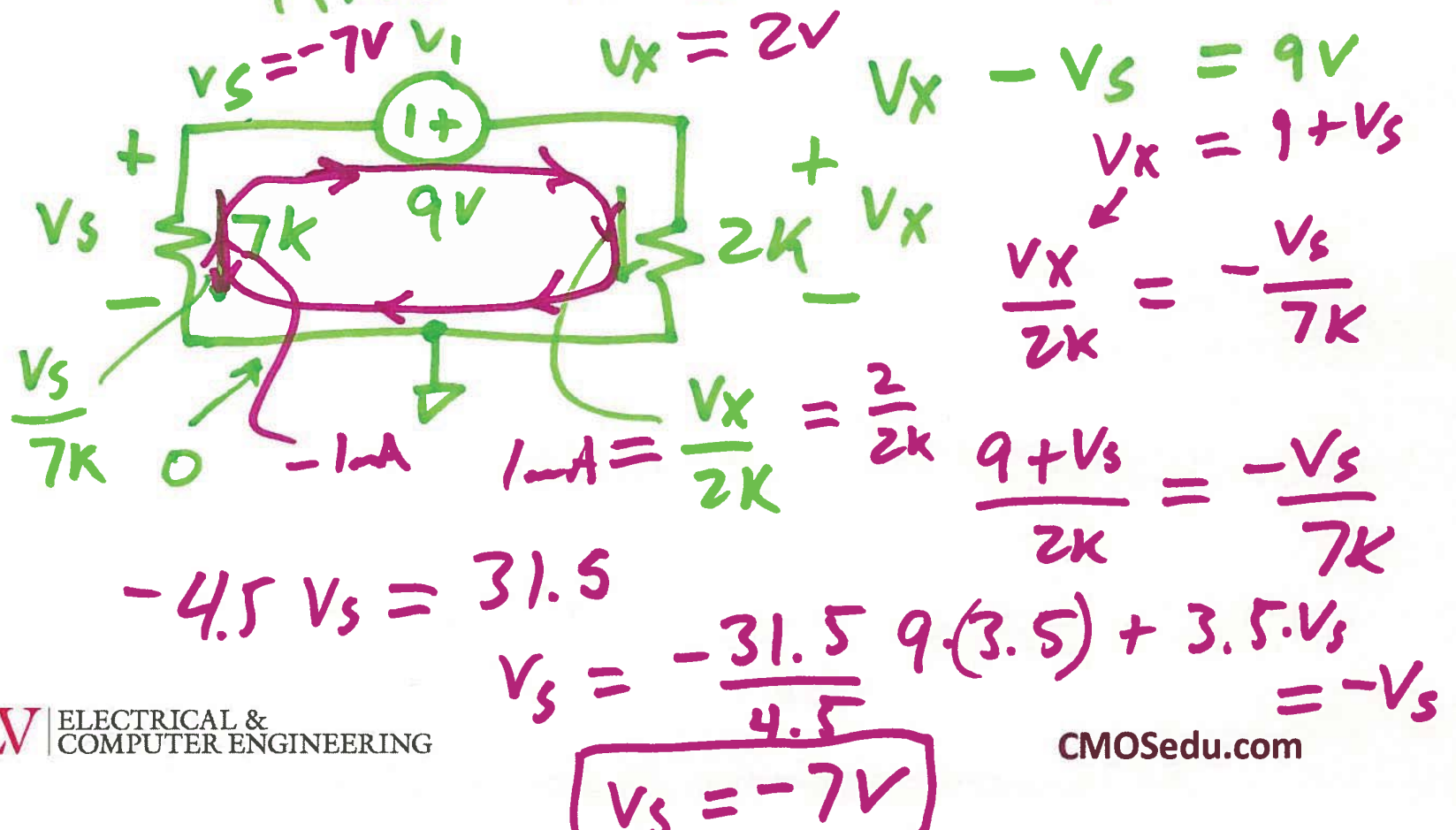


EE 220


Circuits I

H.W. # 3 Help

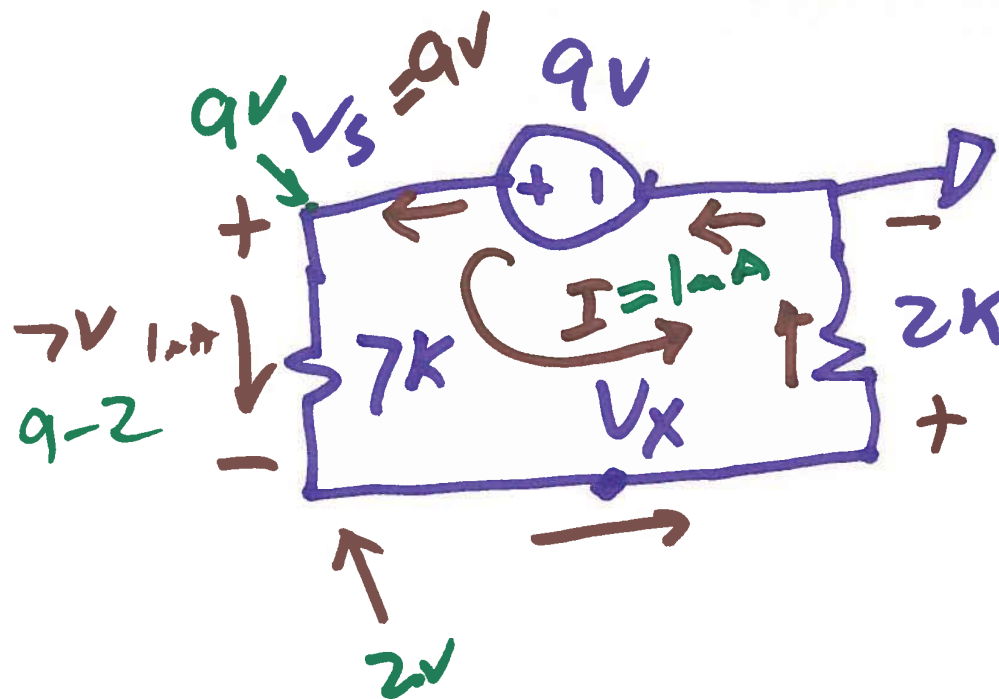


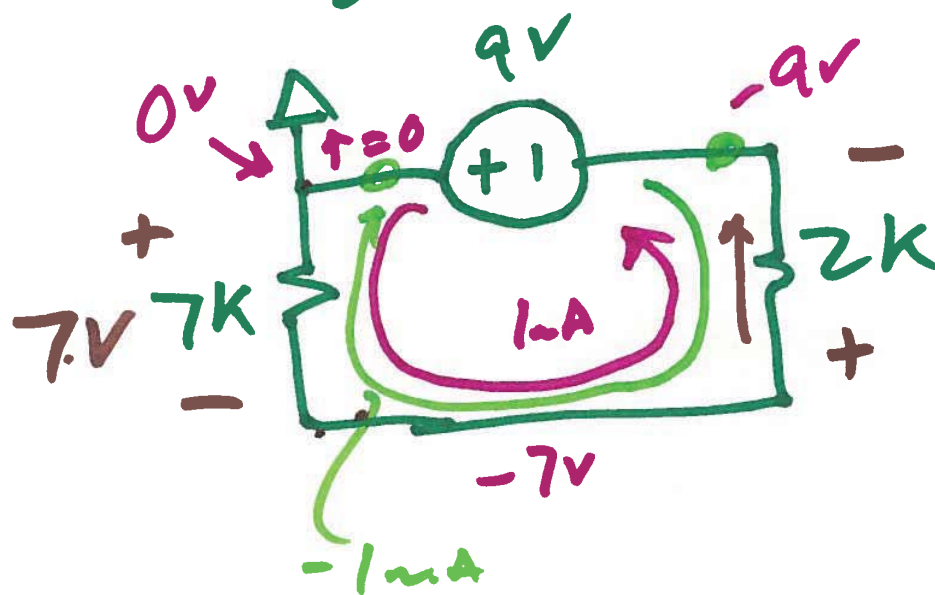
$$I = \frac{9\text{V}}{9\text{k}} = 1\text{mA}$$



$$\frac{0 - (-9)}{2\text{k} + 7\text{k}} = 1\text{mA}$$

$$\frac{-9 - 0}{9\text{k}} = -1\text{mA}$$