
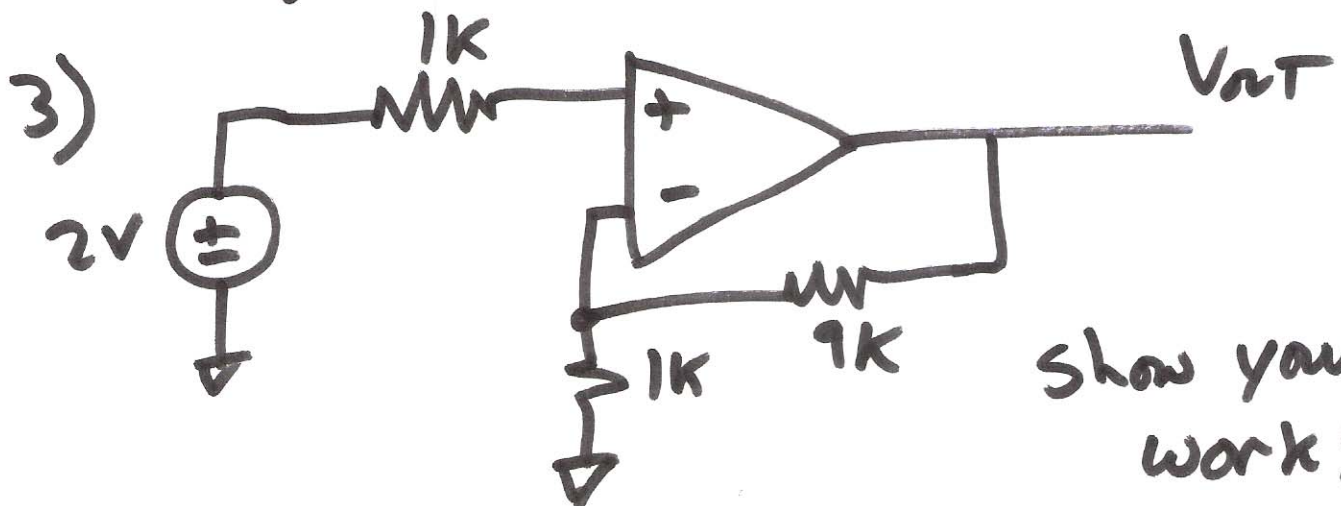
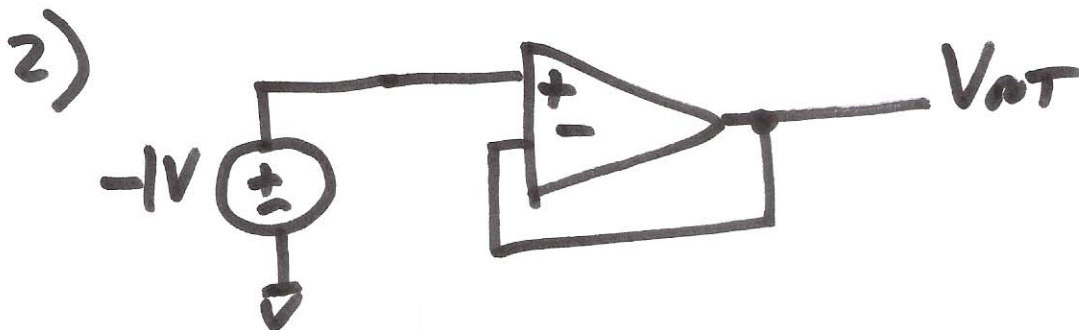


H.W. #1 EE 320 Spring 2013

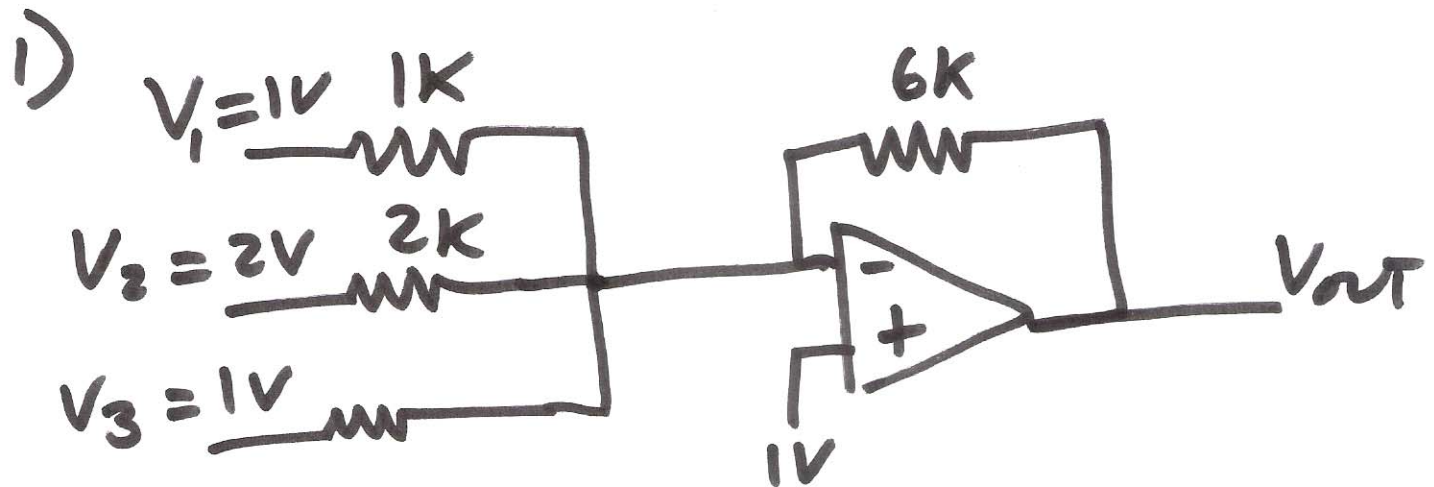Hand calculate, and verify with simulations, the outputs of each of the following circuits.



Show your work!