

Lecture 10

2/25/13

2/25/13

$$I_D \approx I_S e^{V_D / n V_T}$$

$$V_D = n V_T \ln \frac{I_D}{I_S}$$

$$V_D = 1.25 \text{ mV} \cdot \ln \frac{10^{-7}}{10^{-15}}$$

$$V_D = I_D + i_d = i_D$$


DC diode current


AC diode current

$$v_D = V_D + v_d$$

DC AC


$$I_D = 1 \text{ mA}$$

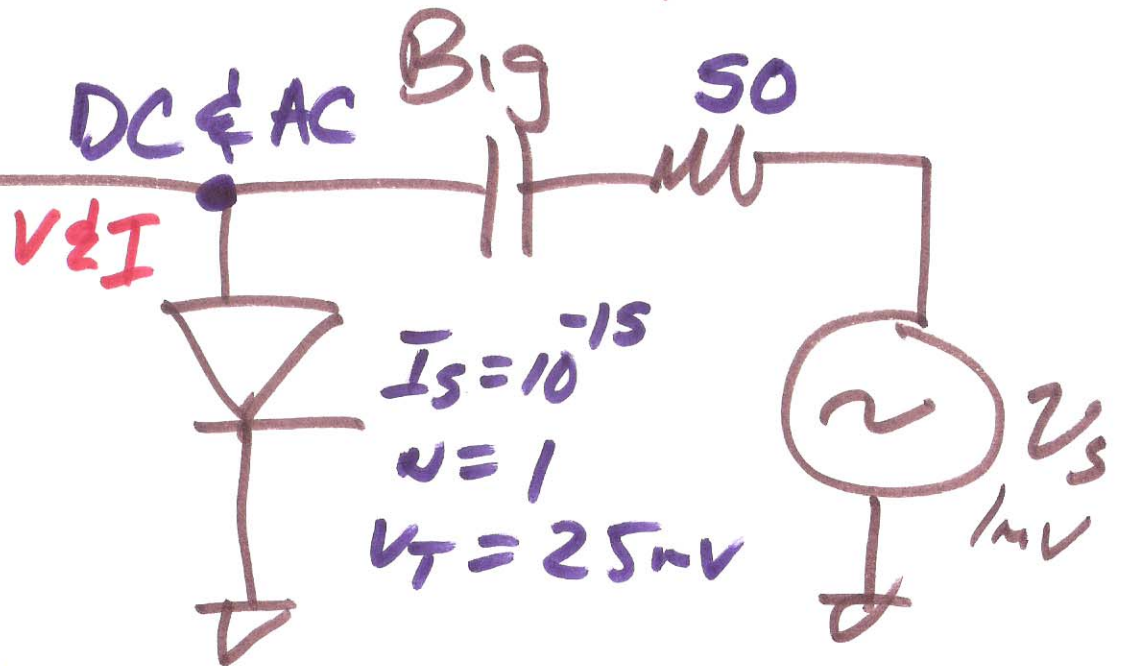

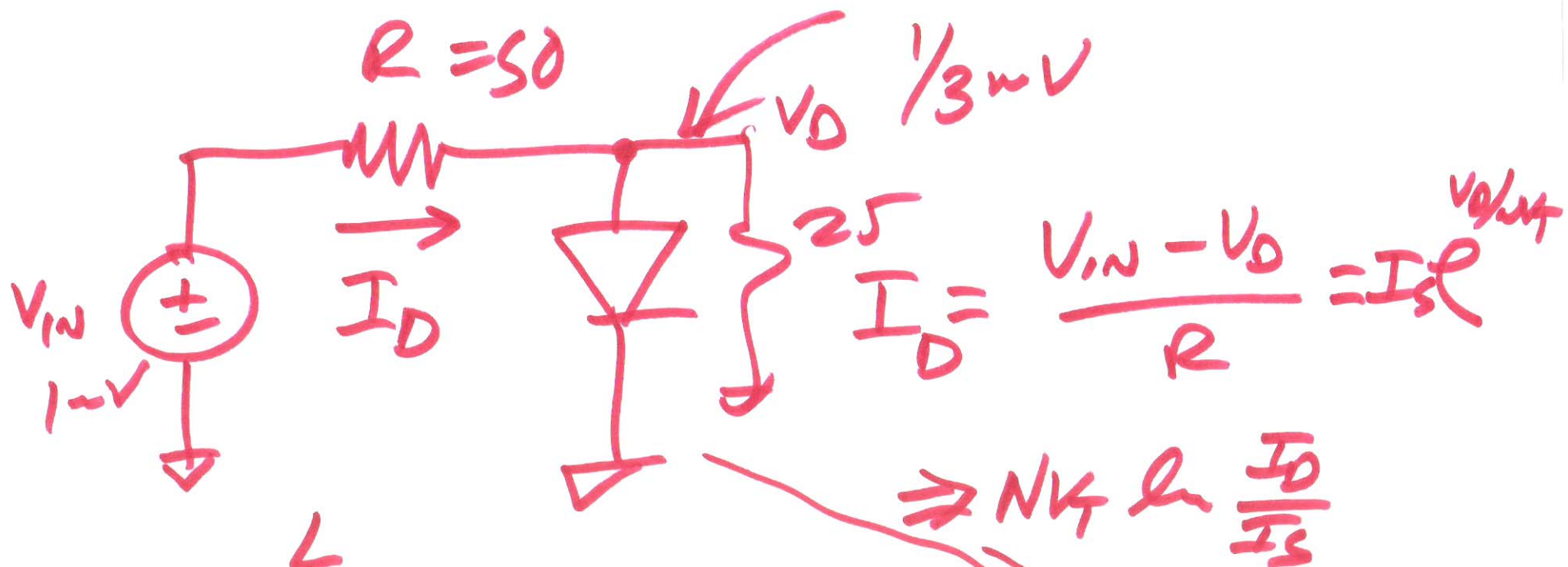

$$\frac{V_{IN} - V_D}{R} = I_S e^{\frac{V_D}{N V_T}} \Rightarrow N V_T \ln \frac{I_D}{I_S}$$

| L | R | $V_D$ | diff |
|---|---|-------|------|
|   |   |       |      |

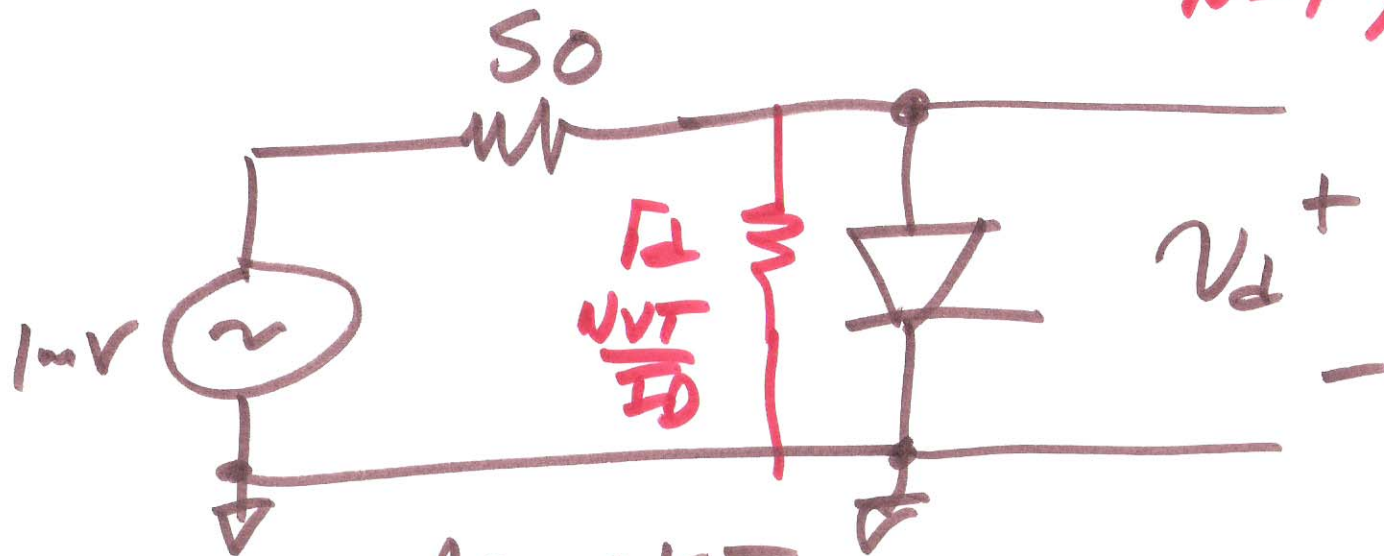


$N=1, V_T = 25mV$

$I_D = 1\mu A$

$r_d = 25\Omega$

AC-CKT

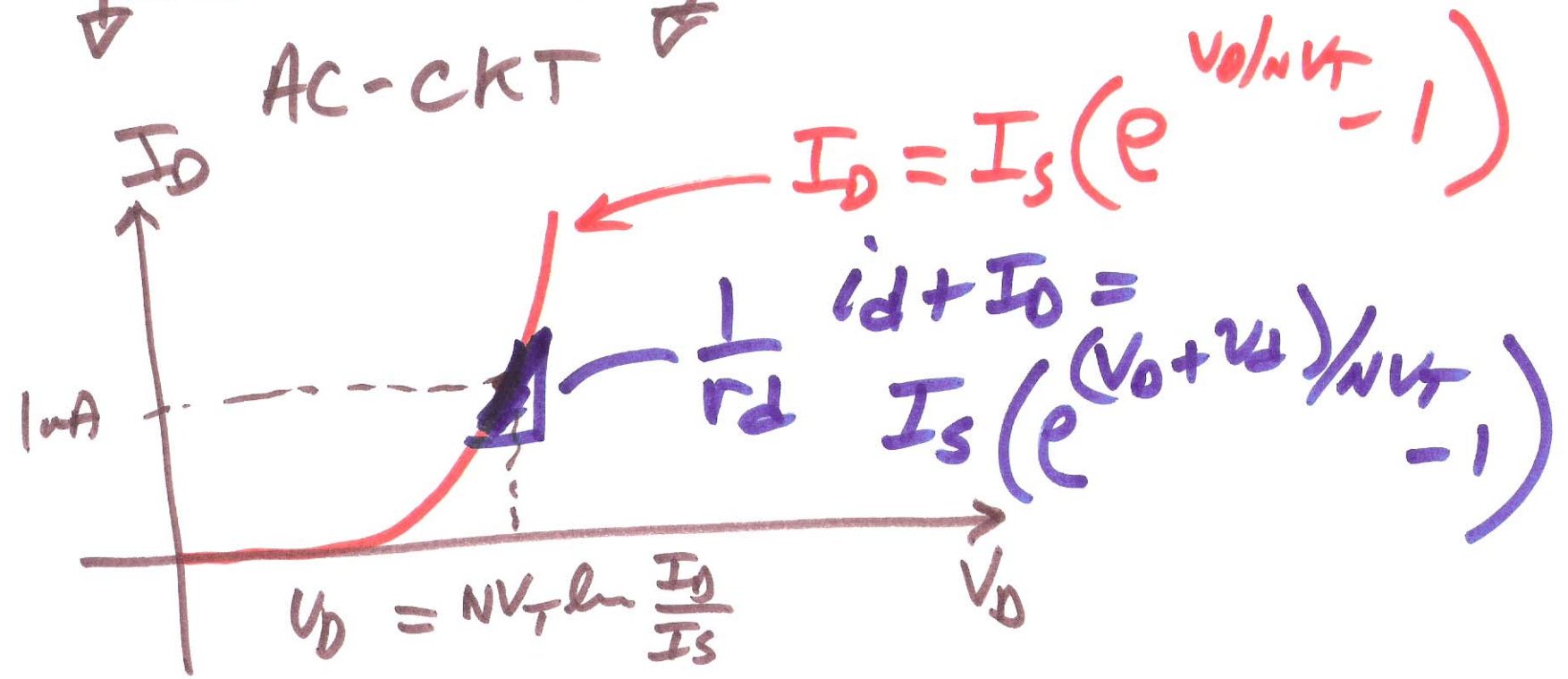

$$\frac{1}{r_d} = \left. \frac{\delta i_D}{\delta v_D} \right|_{\substack{I_D = \text{CONST} \\ V_D = \text{CONST}}} = \frac{\delta (I_D + i_d)}{\delta v_D}$$



$$= \left. \frac{\delta}{\delta v_D} \right|_{\substack{I_D = \text{CONST} \\ V_D = \text{CONST}}} I_S e^{v_D / N V_T}$$

$$r_d = \frac{N V_T}{I_D}$$

$$= \frac{I_S}{N V_T} e^{v_D / N V_T} = I_S e^{\frac{v_D + v_{D1}}{N V_T}} \approx I_D$$

$v_D \gg v_{D1}$

$$\frac{1}{r_d} = \frac{I_D}{N V_T}$$

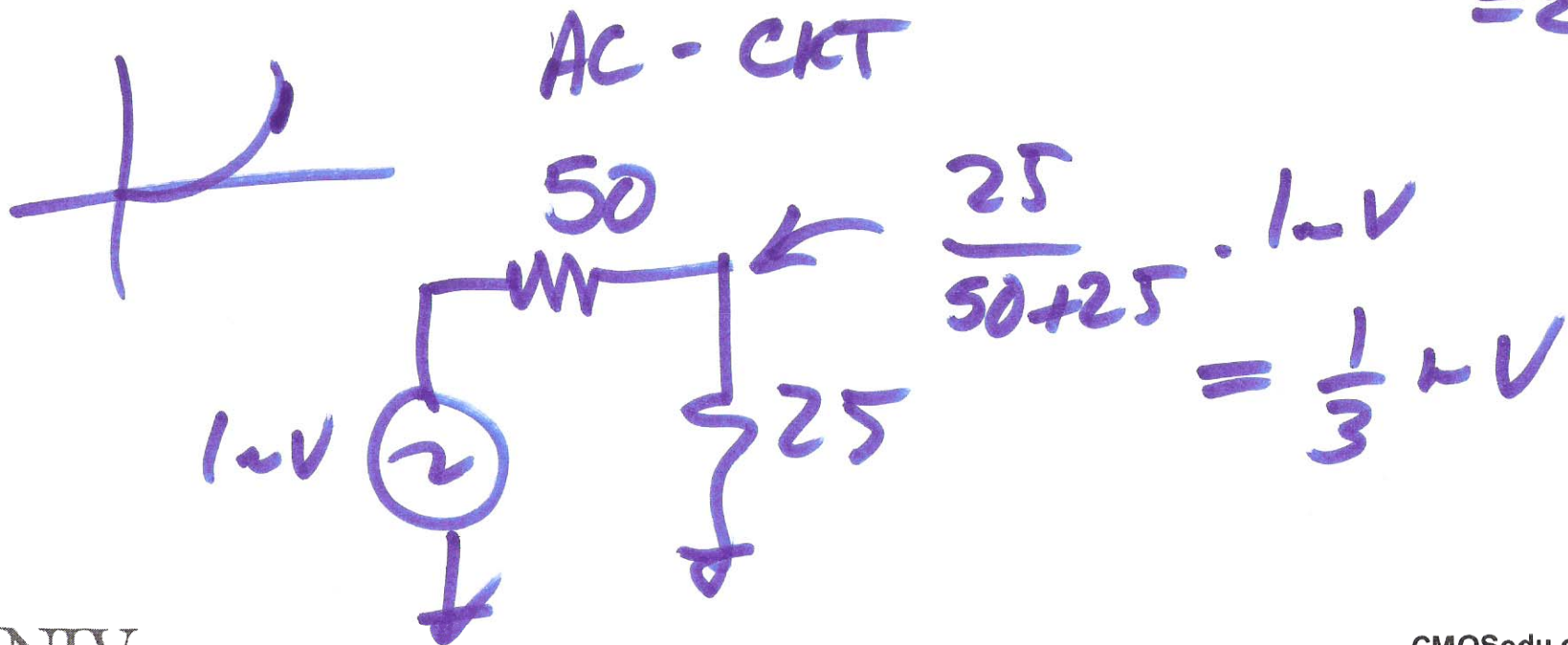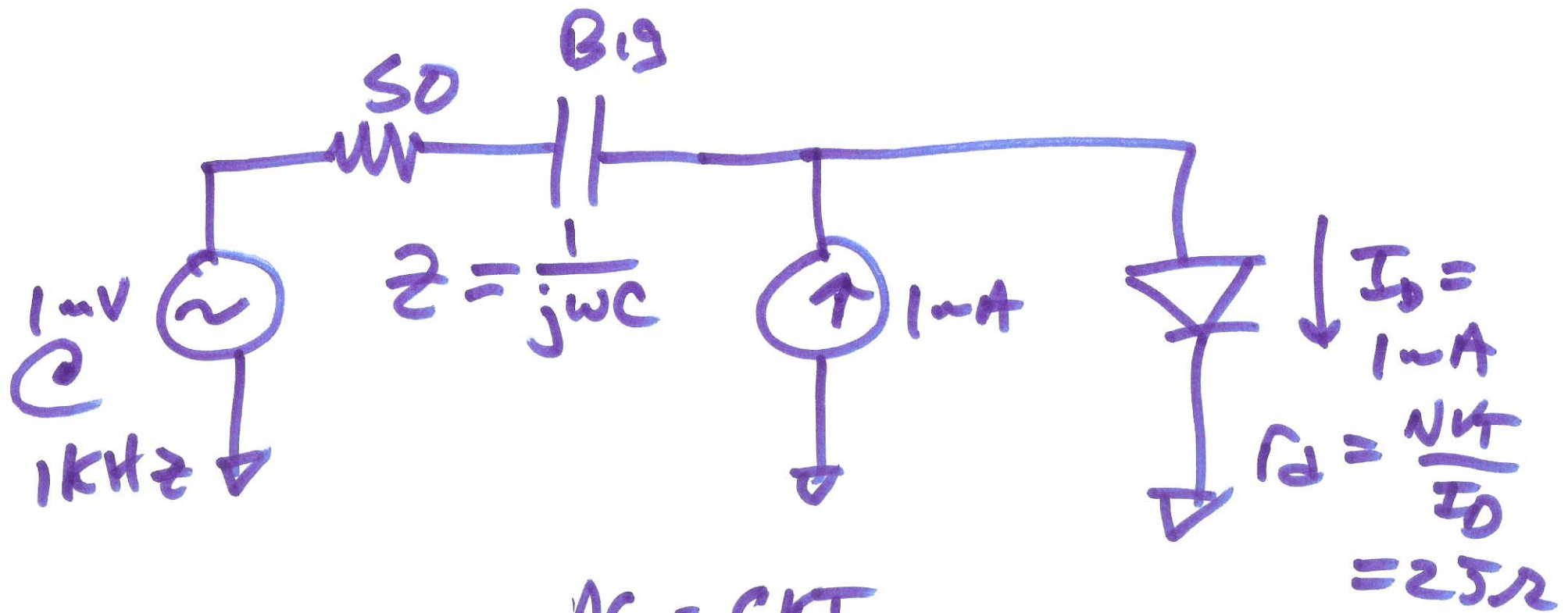

$$1 \text{ mV} = 10^{-3} \text{ V}$$

$$\text{dB} = 20 \log 10^{-3} \\ = -60 \text{ dB}$$

$$\frac{1}{2} \text{ mV} \rightarrow -66 \text{ dB}$$

$$\frac{1}{2} \rightarrow -6 \text{ dB}$$

$$\times 2 \rightarrow 6 \text{ dB}$$



$$\times 5 \rightarrow 14 \text{ dB}$$


$$\times 10 \rightarrow 20 \text{ dB}$$

$$\times 20 \rightarrow 26 \text{ dB}$$

$$\times 50 \rightarrow 34 \text{ dB}$$

$$\times 100 \rightarrow 40 \text{ dB}$$

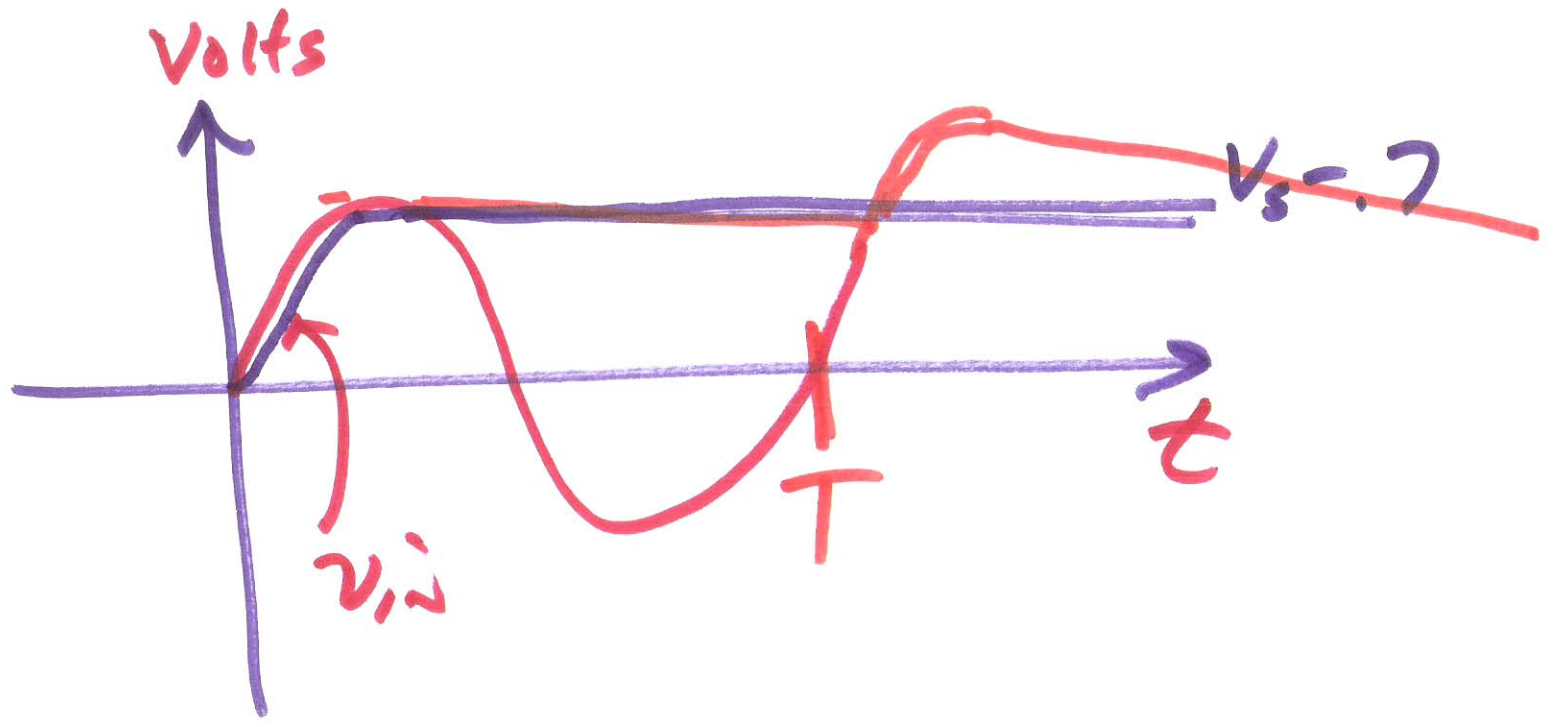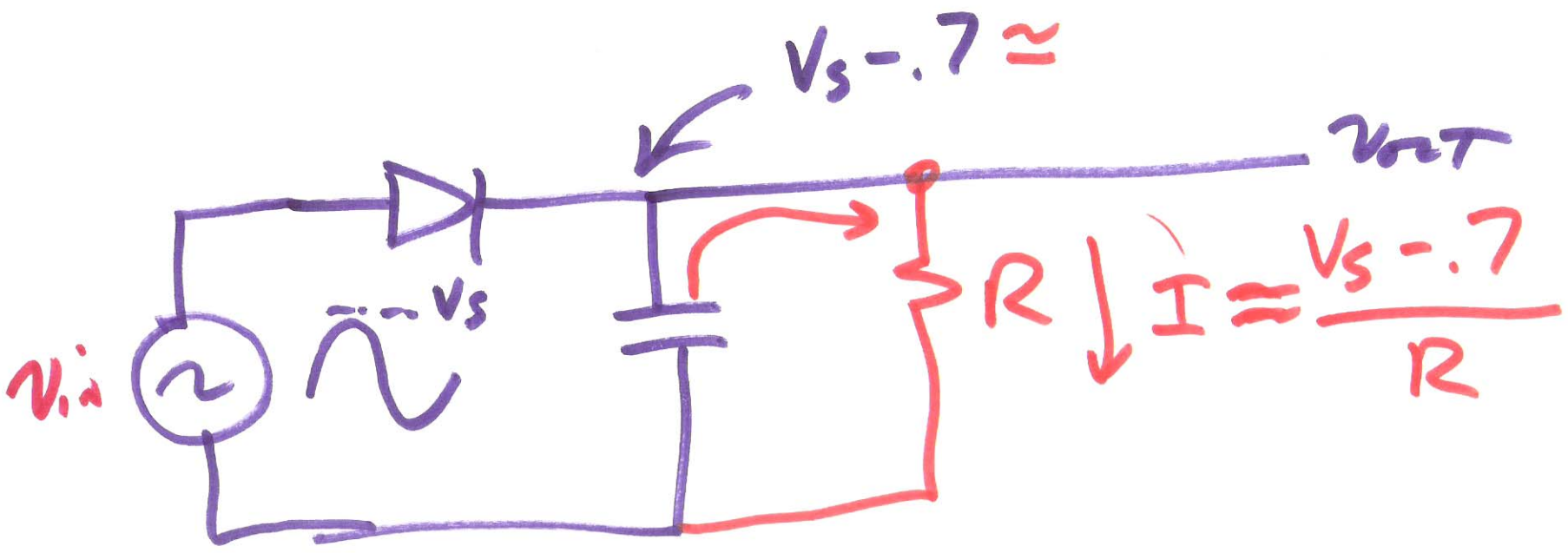

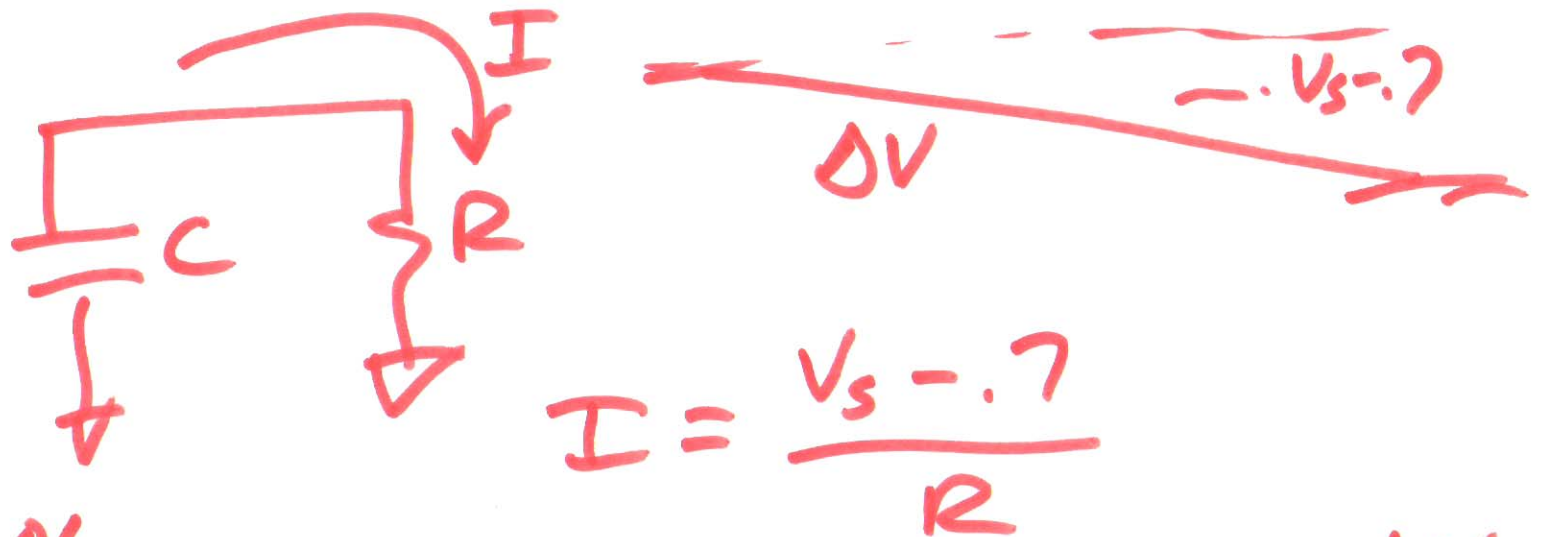

$$I = \frac{V_s - 0.7}{R}$$

$$\frac{\Delta V}{V} < 1\%$$

$$\Delta V < 5\% \text{ of } 5V$$

$$\Delta V \leq 50 \text{ mV}$$


$$I = C \frac{dV}{dT} = \frac{V_s - V_D}{R} = C \frac{\Delta V}{\cancel{dT}}$$

$$\Delta V = \frac{V_s - V_D}{R} \cdot \frac{T}{C} \leftarrow \frac{1}{f}$$

$$\Delta V = \frac{I_{L, \max}}{f \cdot C}$$

$$I_{L, \max}$$

8)

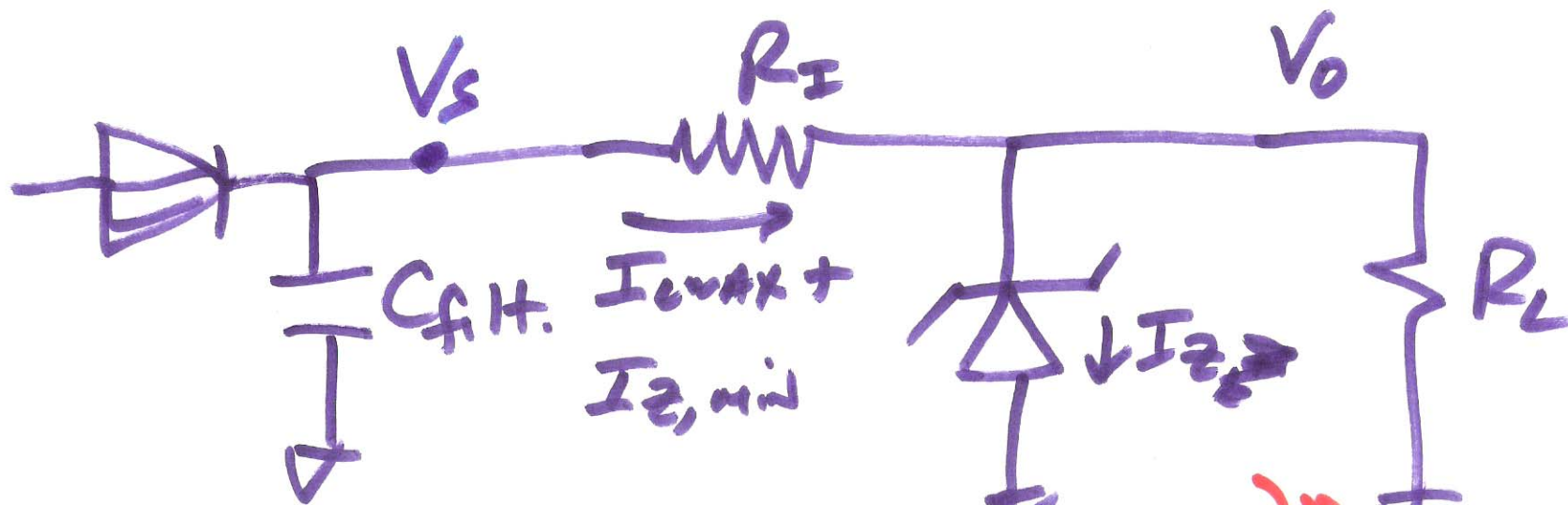


$$I_{L,MAX} = ?$$

$$= \frac{V_O}{R_{Lmin}}$$


$$V_Z + (I_{L,MAX} + I_{Z,min})r_Z$$
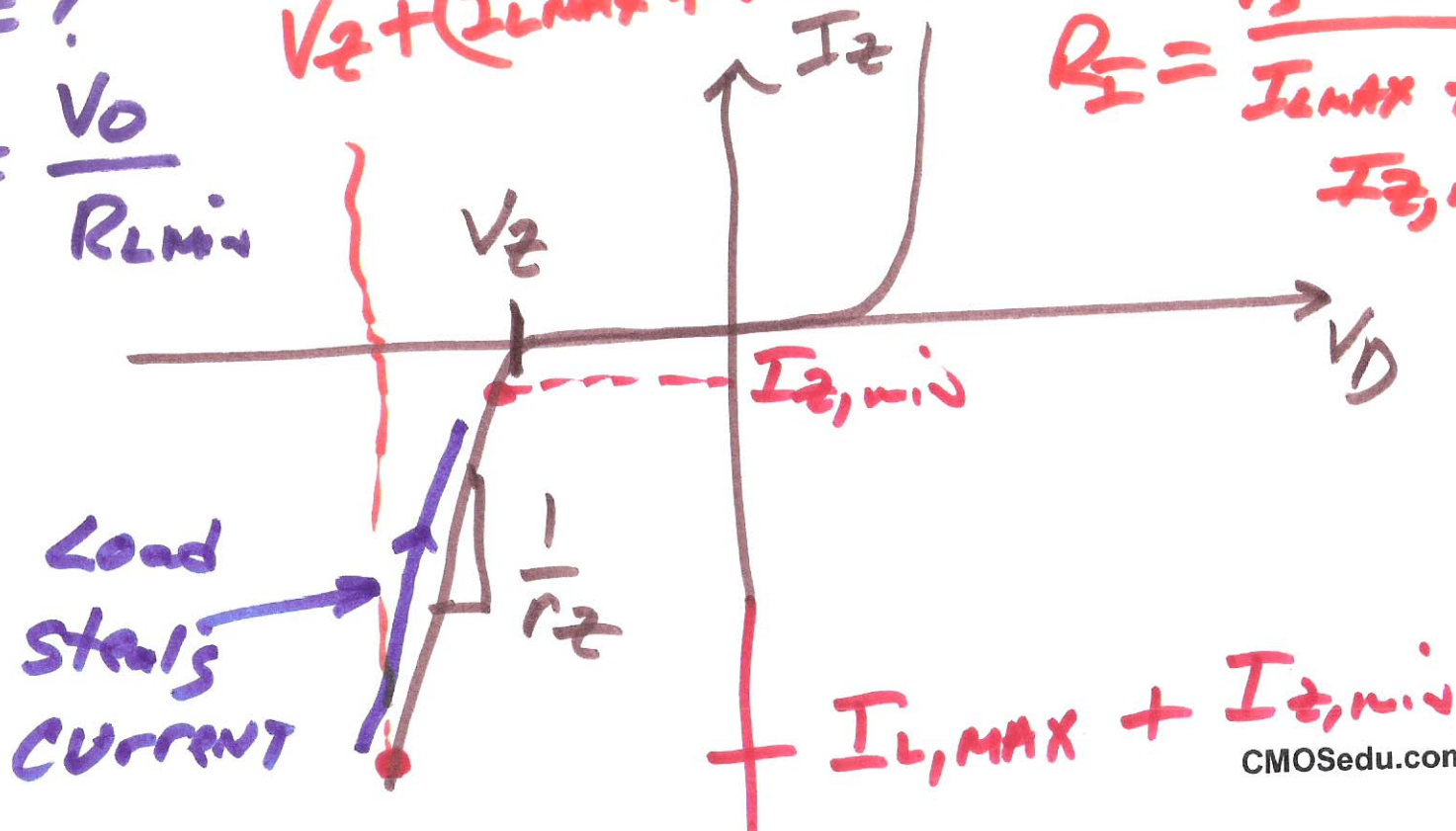
$$R_I = \frac{V_S - V_O}{I_{L,MAX} + I_{Z,min}}$$



$$V_{O1} = V_Z + (I_{LMAX} + I_{Zmin}) r_Z$$

$$V_{O2} = R_{L,min} \cdot I_{LMAX}$$

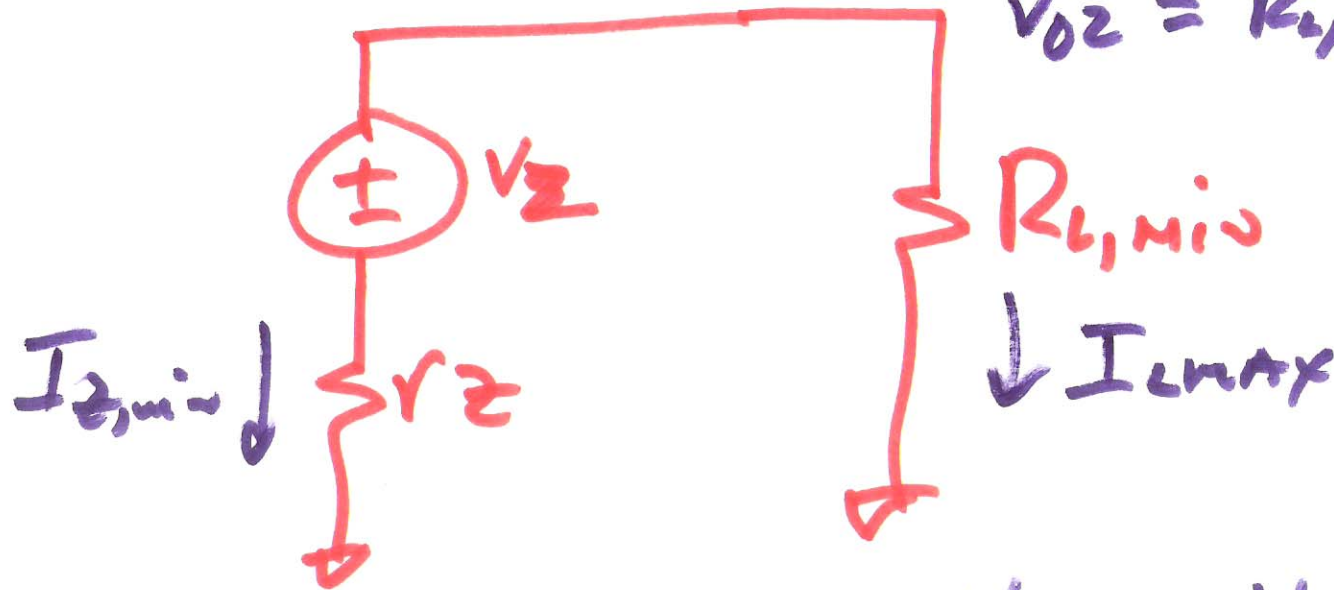

$$\Delta V = V_{O1} - V_{O2}$$