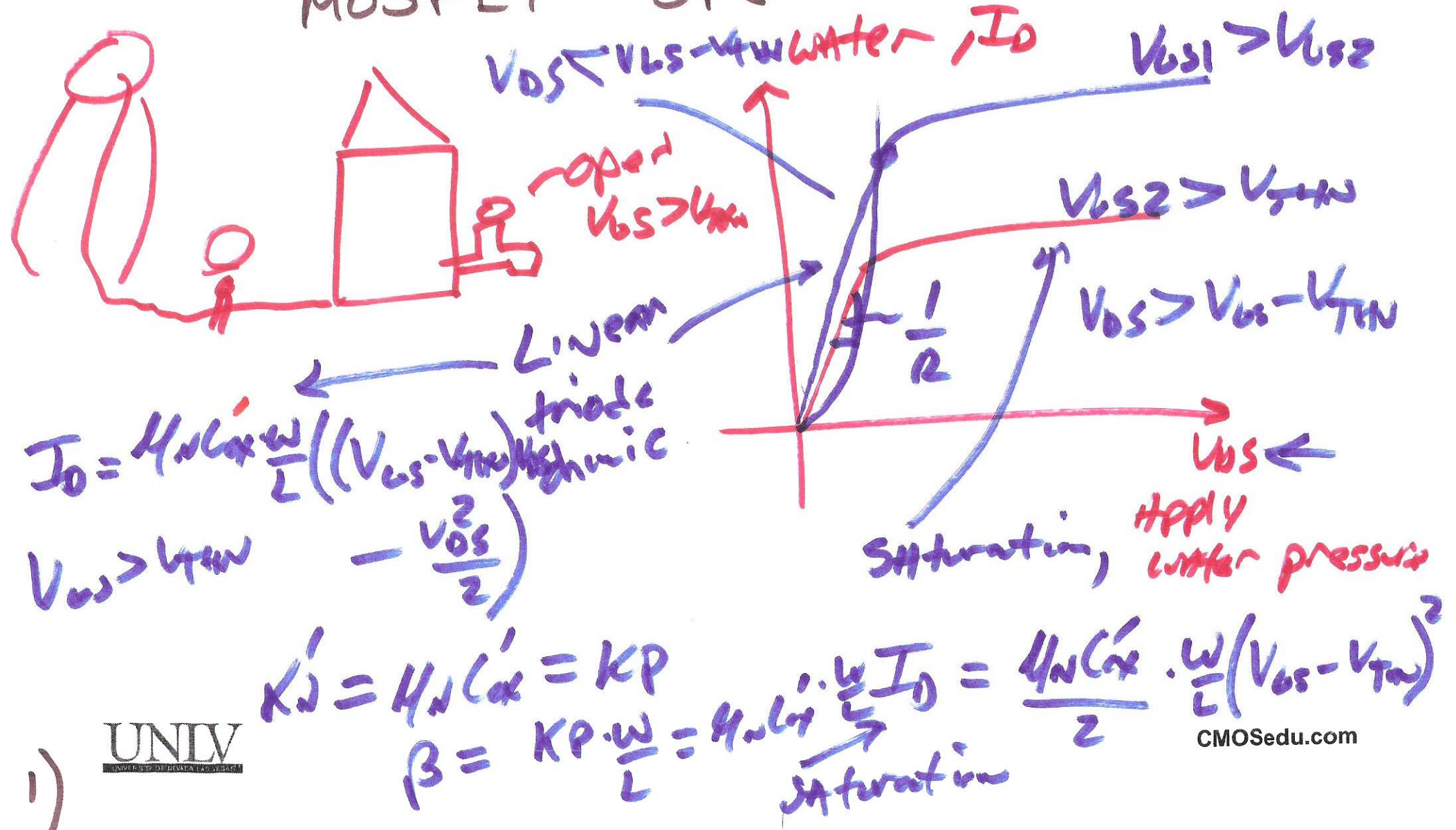


EE 320 Electronics

Lecture 14, 3/15/2013

MOSFET Operation



$$i_D = I_0 + i_d = \frac{\mu_n C_{ox}}{L} \left((V_{GS} - V_{THN}) V_{DS} - \frac{V_{DS}^2}{2} \right)$$

triode equation in triode


$$V_{GS} = V_{GS} + V_{GS}$$

$$V_{DS} = V_{DS} + V_{DS}$$

$$V_{GS} > V_{THN}$$

$$V_{DS} < V_{GS} - V_{THN}$$
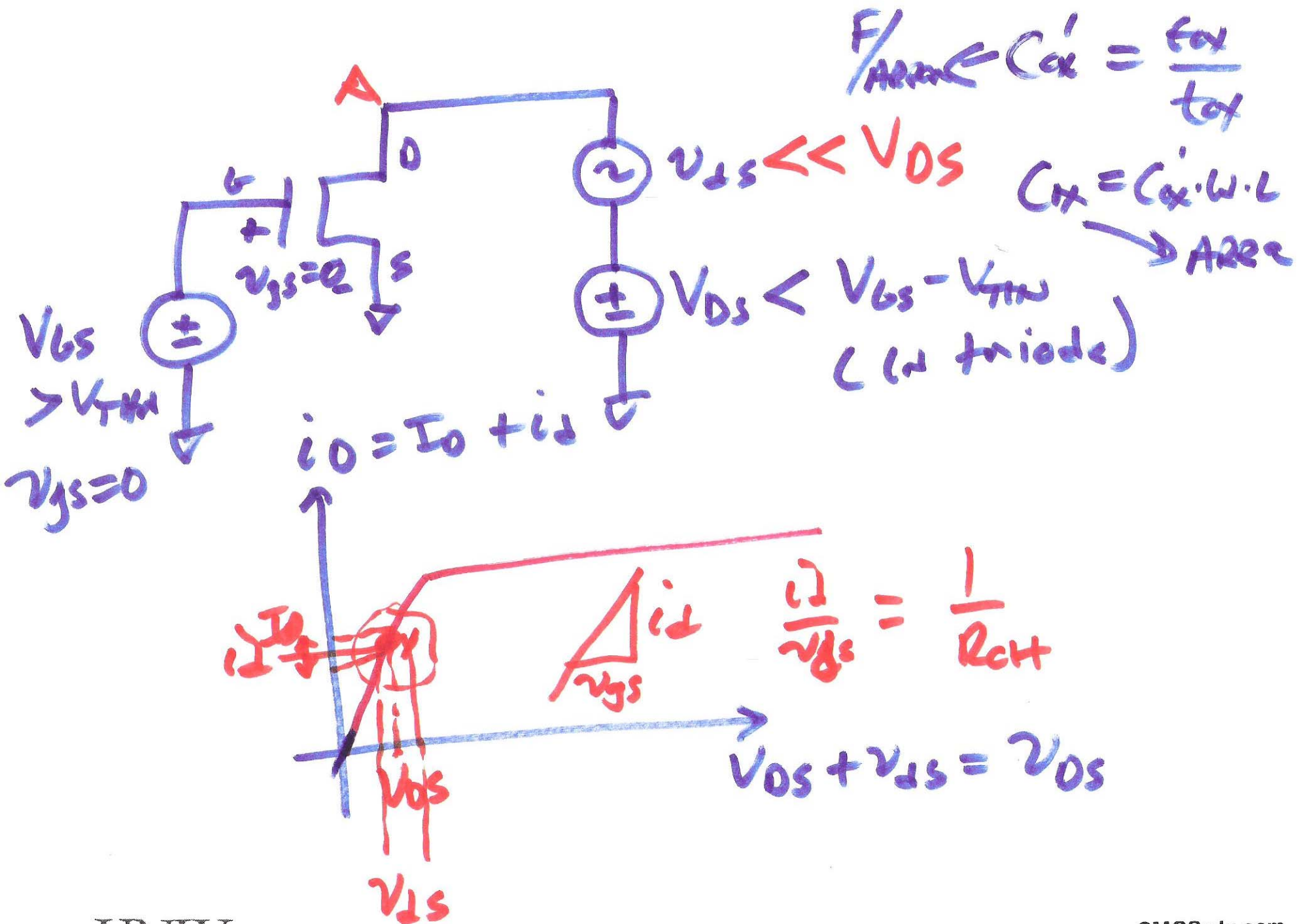
$$i_D = I_0 + i_d = \frac{\mu_n C_{ox}}{L} \left((V_{GS} - V_{THN}) V_{DS} - \frac{V_{DS}^2}{2} \right)$$



$$R_{ch}^{-1} = \left. \frac{\delta i_D}{\delta v_{DS}} \right|_{\substack{I_D = \text{const} \\ V_{GS} = \text{const}}} = \frac{\delta \frac{\mu_n C_{ox}}{L} \cdot ((V_{GS} - V_{THN}) \cdot (V_{DS} - \frac{V_{DS}^2}{2}))}{\delta v_{DS}}$$

$$R_{ch}^{-1} = \frac{\mu_n C_{ox}}{L} ((V_{GS} - V_{THN}) - V_{DS})$$

$V_{DS} \gg V_{DS}$ (Small-signal approximation)

$$R_{ch} \approx \frac{1}{\frac{\mu_n C_{ox}}{L} ((V_{GS} - V_{THN}) - V_{DS})}$$

$$V_{GS} > V_{THN}$$

$$V_{DS} < V_{GS} - V_{THN}$$

if V_{DS} is small $R_{ch} \approx \frac{1}{\frac{\mu_n C_{ox}}{L} (V_{GS} - V_{THN})}$

$$4.9) I_0 = ?$$

$$V_{GS} = 0, 1, 2, 3$$

$$V_{DS} = 0.25$$

$$W = 5 \mu$$

$$L = 0.5 \mu$$

$$V_{TN} = 800 \text{ mV}$$

$$K'_N = 200 \mu\text{A}/\text{V}^2$$

$$K_N = ?$$

$$K_N = K'_N \cdot \frac{W}{L}$$

$$= \frac{200 \mu\text{A}}{\text{V}^2} \cdot \frac{5 \mu}{.5 \mu}$$

$$V_{GS} = 0, I_0 = 0$$

$$V_{GS} < V_{TN}$$

$$V_{GS} = 1 \text{ V} \quad I_0 \neq 0$$

SAT.

$$V_{DS} \geq V_{GS} - V_{TN}$$

$$0.25 \geq 1 - .8 = 0.2$$

?

$$I_0 = \frac{K_N}{2} (V_{GS} - V_{TN})^2 = \frac{2 \mu\text{A}}{2} (1 - .8)^2$$

$$V_{GS} = 2V \quad I_D \neq 0$$

$$V_{DS} \geq V_{GS} - V_{THN} \text{ (for saturation)}$$

$$0.25 \geq 2 - .8 = 1.2$$

? NO, MUST be in triode

$$I_D = K_N \left((V_{GS} - V_{THN}) V_{DS} - \frac{V_{DS}^2}{2} \right)$$


$$I_D = \frac{2 \mu A}{V_2} \left((2 - .8) \cdot .25 - \frac{.25^2}{2} \right)$$

$V_{DS} = V_{GS} - V_{THN}$ triode or saturation?

$$I_D = K_N \left((V_{GS} - V_{THN}) (V_{GS} - V_{THN}) - \frac{(V_{GS} - V_{THN})^2}{2} \right)$$

$$= K_N \left((V_{GS} - V_{THN})^2 - \frac{(V_{GS} - V_{THN})^2}{2} \right)$$

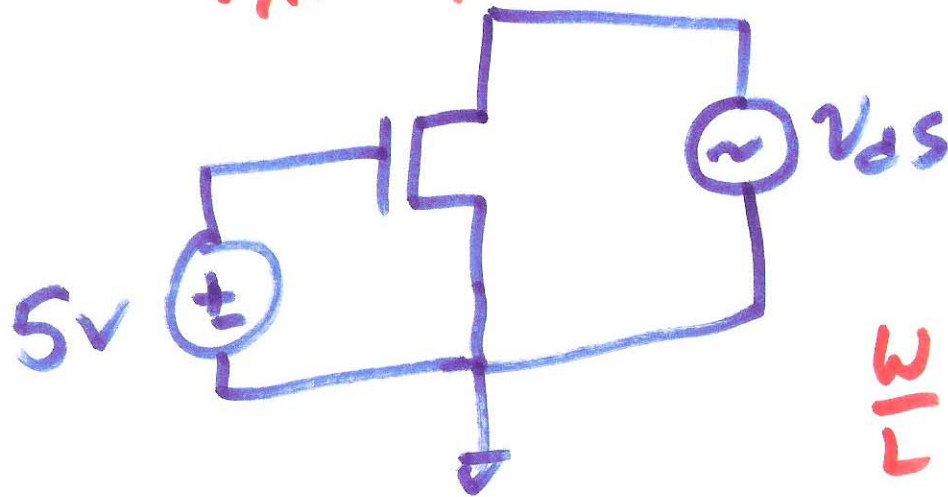4.16) $V_{TN} = 0.75$
 $K' = 100 \mu A/V$
 $= \mu_n \cdot C_{ox}$



$$R_{CH} = \frac{1}{K' \cdot \frac{W}{L} \cdot (V_{GS} - V_{TN})}$$



$$500 = \frac{1}{100 \mu \cdot \frac{W}{L} \cdot (5 - 0.75)}$$

$$\frac{W}{L} = \frac{1}{500 \cdot 100 \mu \cdot 4.25}$$


$$= 4.7$$

$$W = 47 \mu$$

$$L = 10 \mu$$

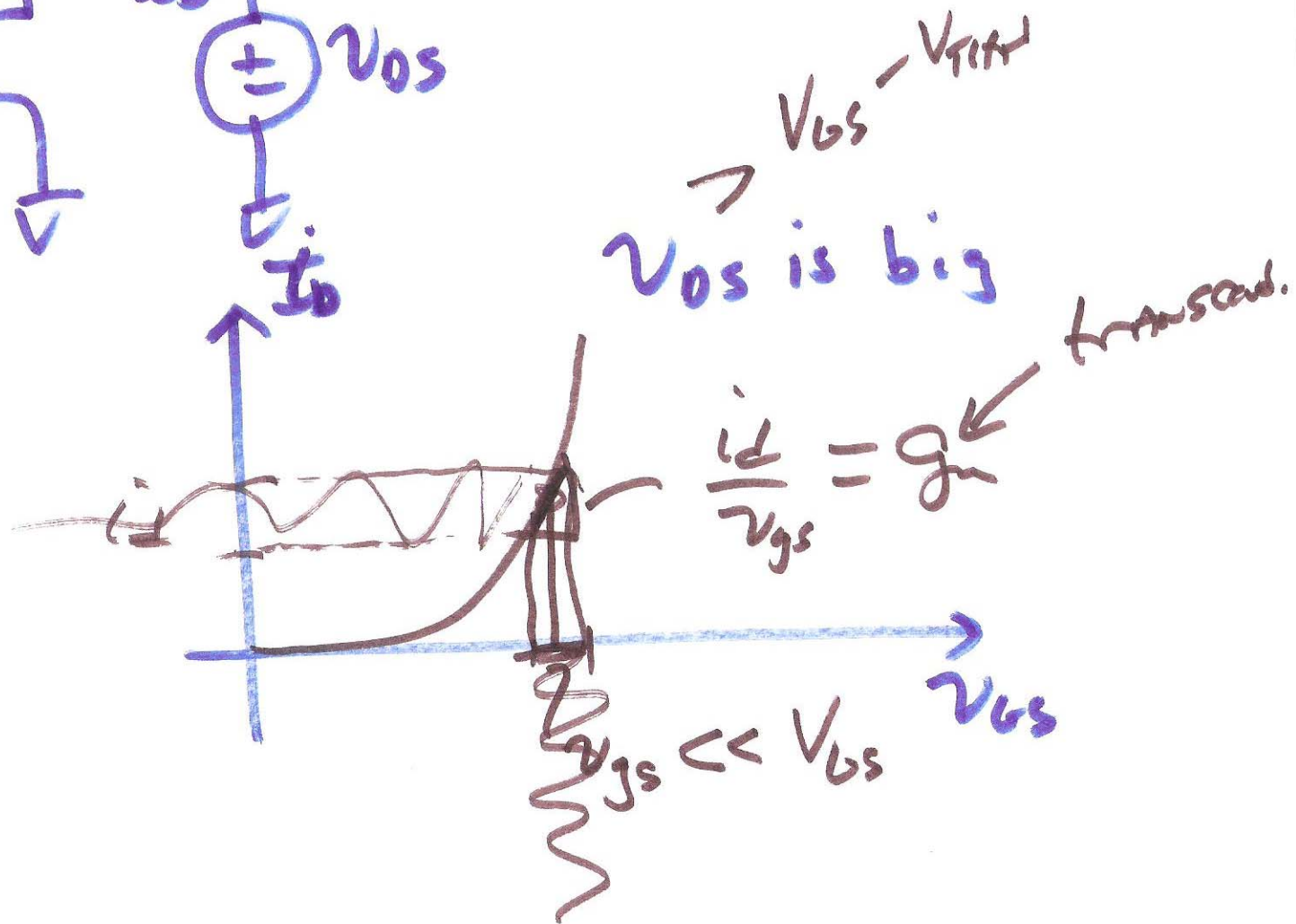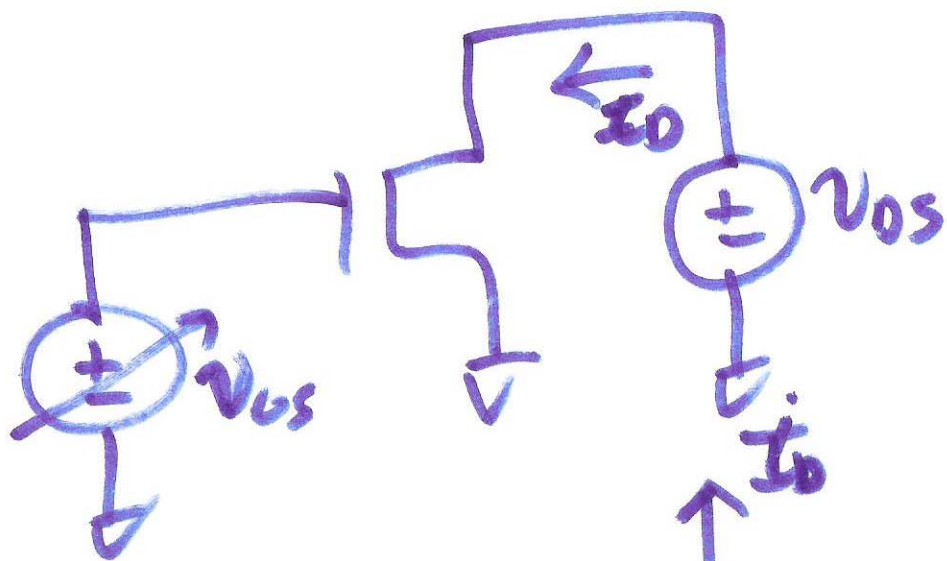

9)

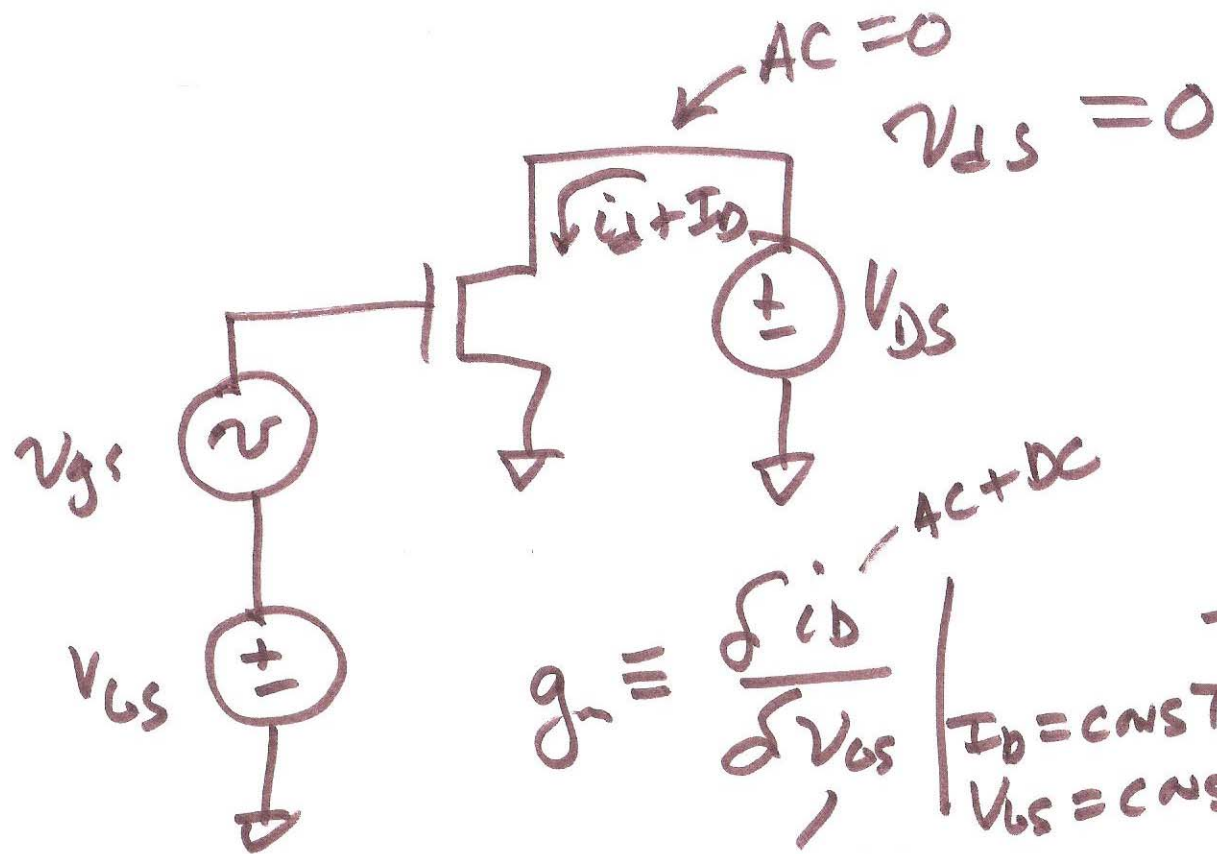

$$g_m \equiv \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{\substack{I_D = \text{CONST} \\ V_{DS} = \text{CONST}}} = \frac{i_d^{AC}}{v_{gs}^{AC}}$$

$$= \frac{\partial}{\partial V_{GS}} \left(\frac{K'W}{2L} (V_{GS} - V_{THN})^2 \right)$$

$$\boxed{\frac{K'W}{L} (V_{GS} + v_{gs} - V_{THN}) = g_m}$$

$$= \left. \frac{\partial}{\partial V_{GS}} \right|_{\substack{I_D = \text{CONST} \\ V_{DS} = \text{CONST}}} \frac{K'W}{2L} (V_{GS} + v_{gs} - V_{THN})^2$$

$$V_{GS} \gg v_{gs}$$

$$I_D = \frac{K' \cdot W}{2L} (V_{GS} - V_{TH})^2$$

$$= \frac{100\mu}{2} \cdot 5 \cdot 1^2 = 250\mu A$$


Made-up example

$$g_m = \frac{K' \cdot W}{L} (V_{GS} - V_{TH})$$

$$V_{GS} = 1\text{mV}$$

$$V_{GS} = 1.75$$

AC = 0

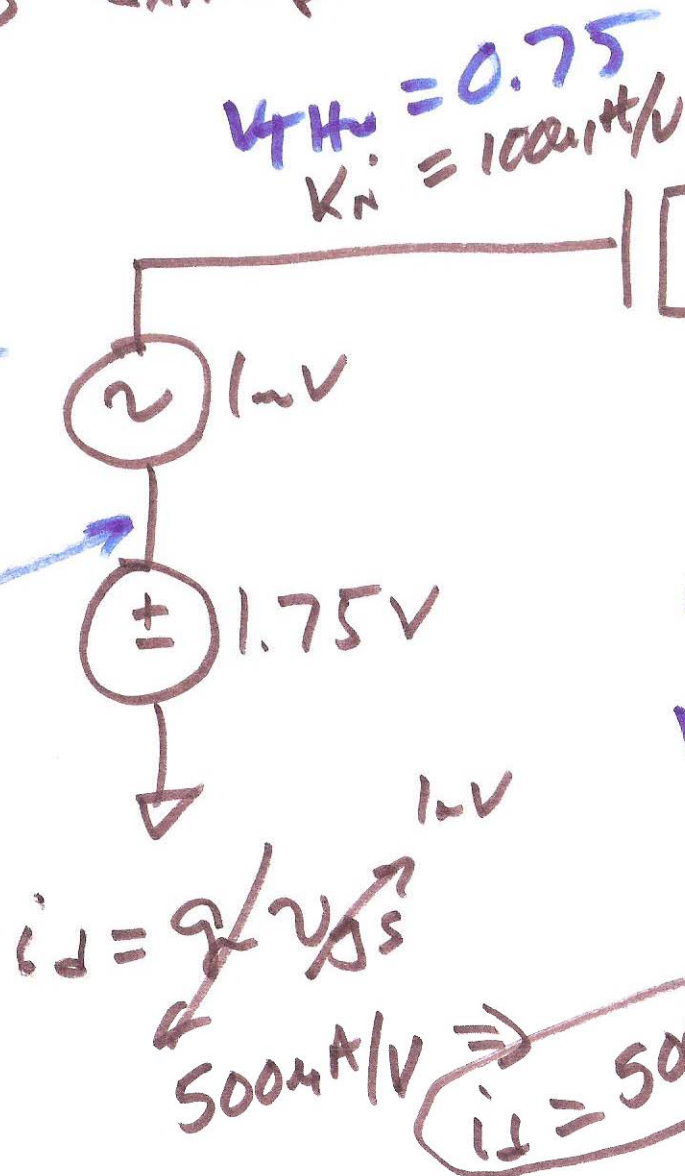

$$V_{DS} = 0$$

$$V_{DS} = 3$$

is transistor in SAT?

$$V_{DS} \geq V_{GS} - V_{TH}$$

$$3 \geq 1.75 - 0.75$$

$$3 \geq 1$$

yes, in SAT!