
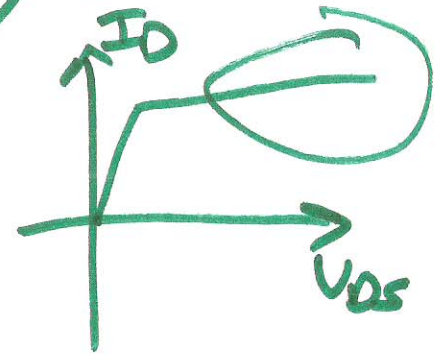


Lecture

17


April 1, 2013


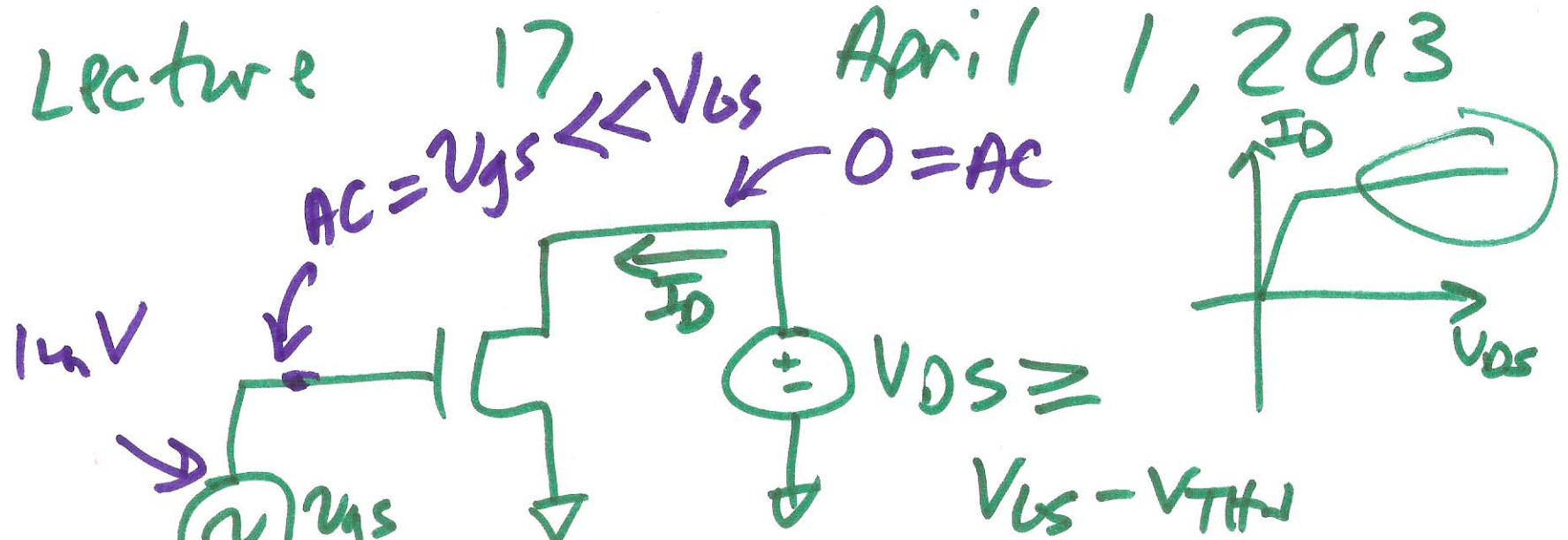


Calculate DC current

$AC = 0$

$i_D = I_D + i_d$



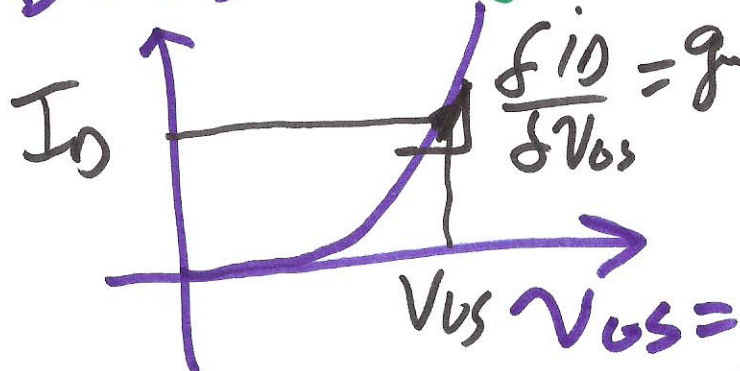


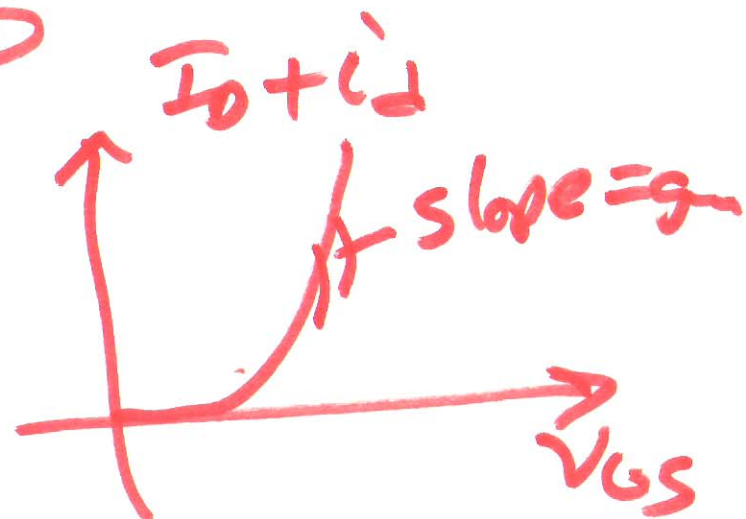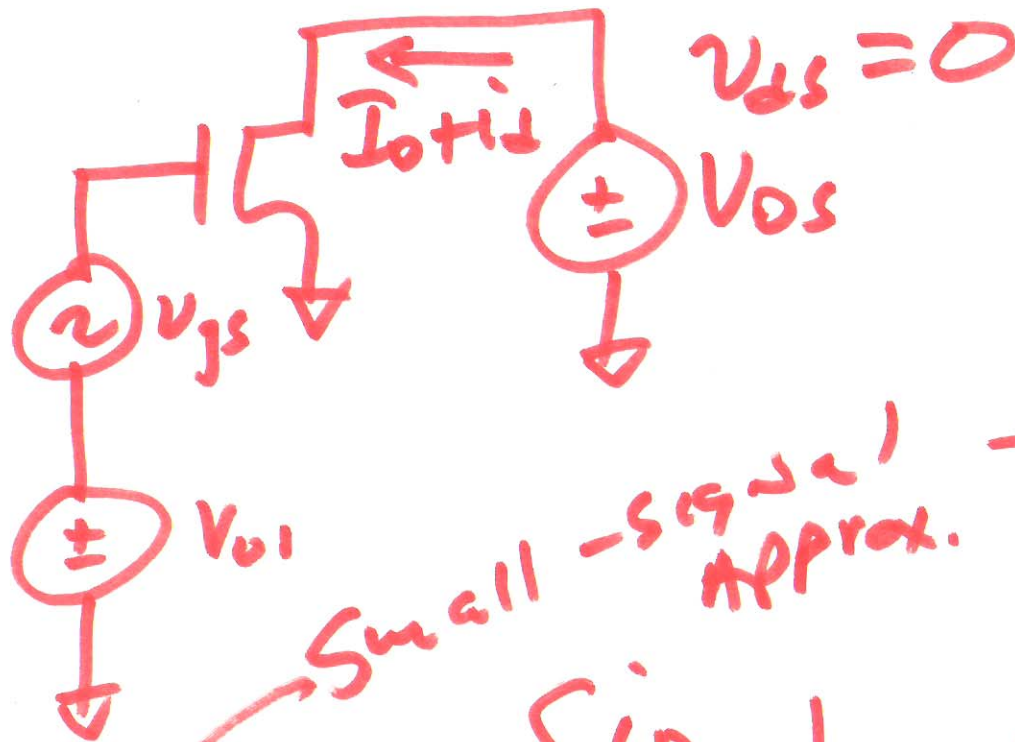


$$g_m = \frac{\delta i_D}{\delta V_{GS}} \Big|_{\substack{I_D = \text{CONST} \\ V_{DS} = \text{CONST}}} = \frac{\delta}{\delta V_{GS}} \frac{K_n' W}{2 L} (V_{GS} + V_{gs} - V_{TN})^2$$

$V_{GS} \gg V_{gs}$
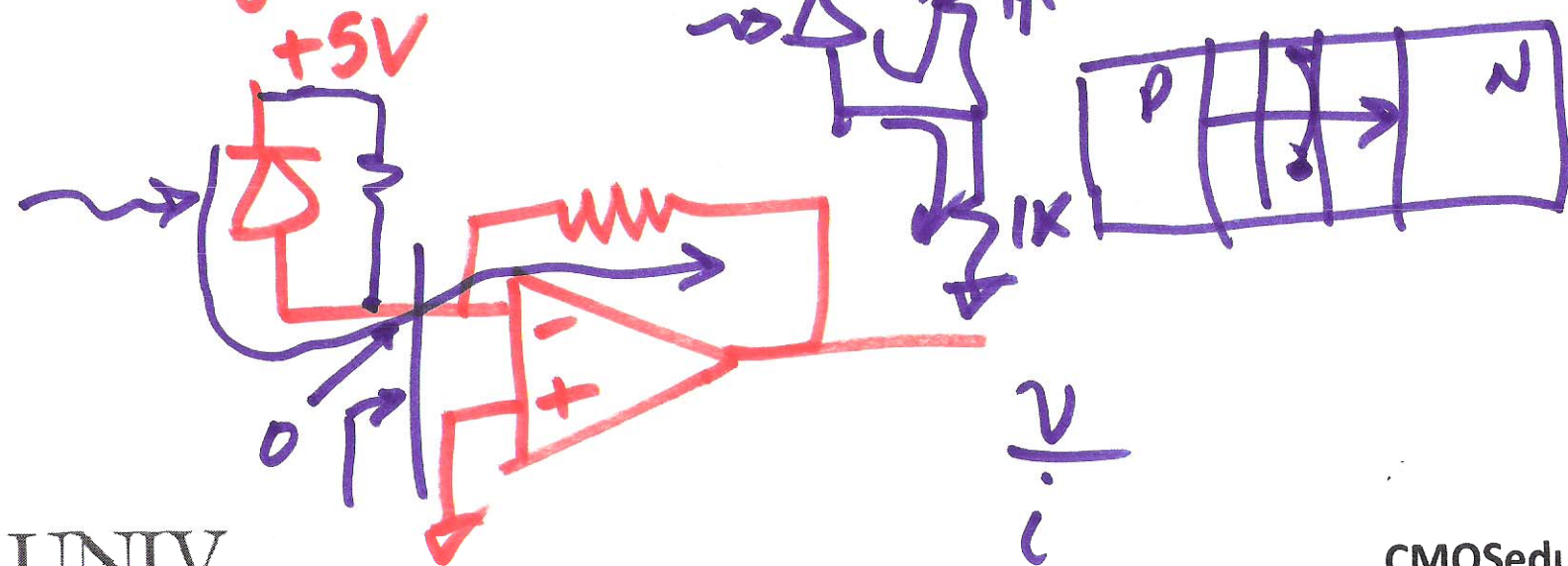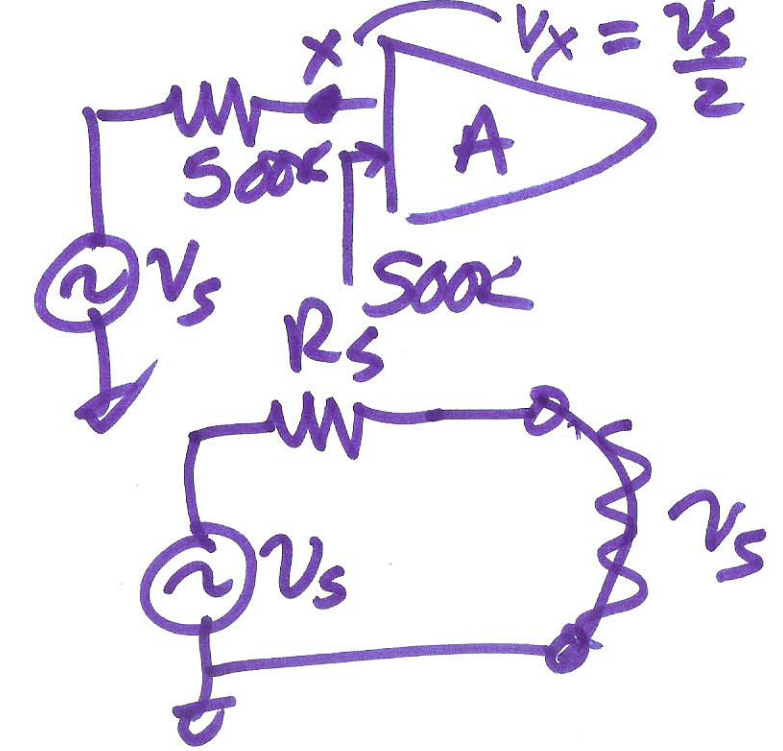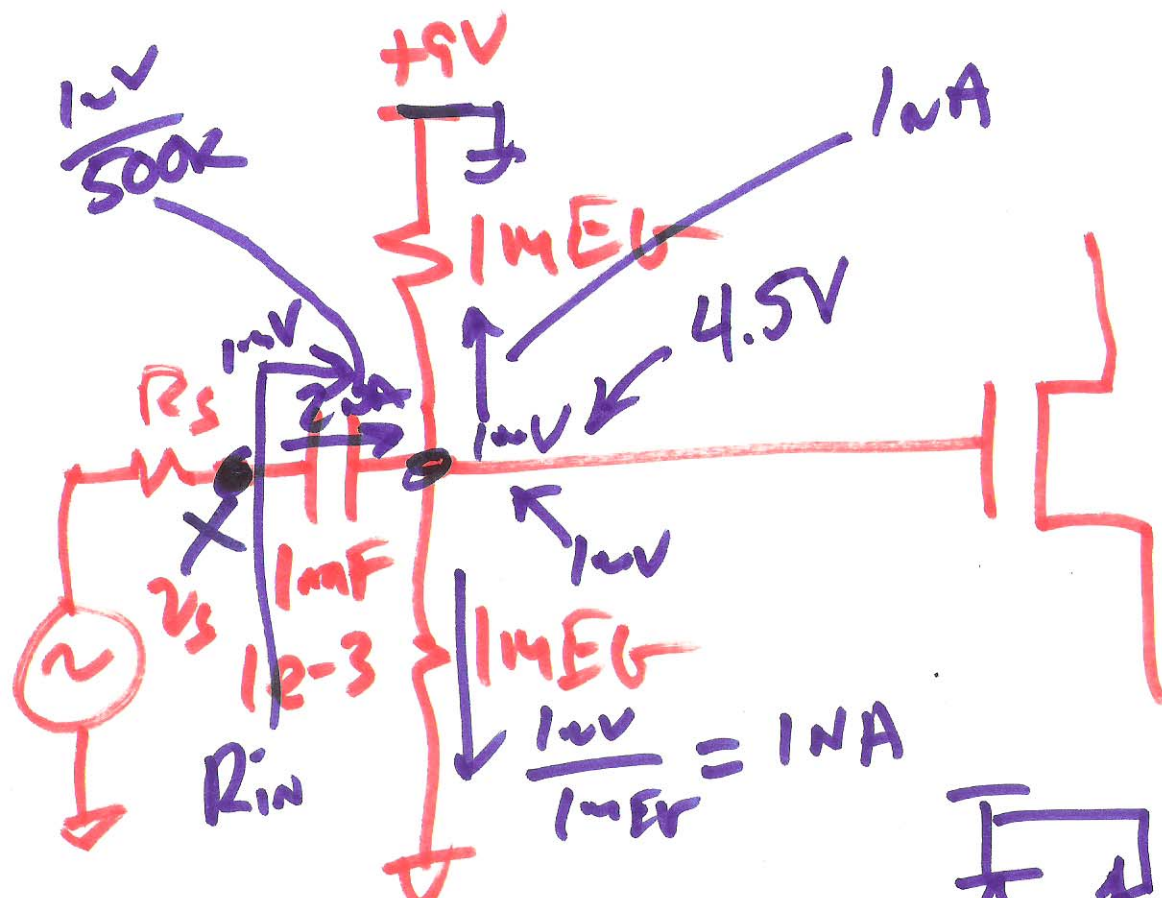
$$\sqrt{2I_D \cdot K_n' \frac{W}{L}} = g_m = 2 \cdot \frac{K_n' W}{2 L} (V_{GS} + V_{gs} - V_{TN}) \cdot \frac{\delta V_{GS}}{\delta V_{GS}}$$




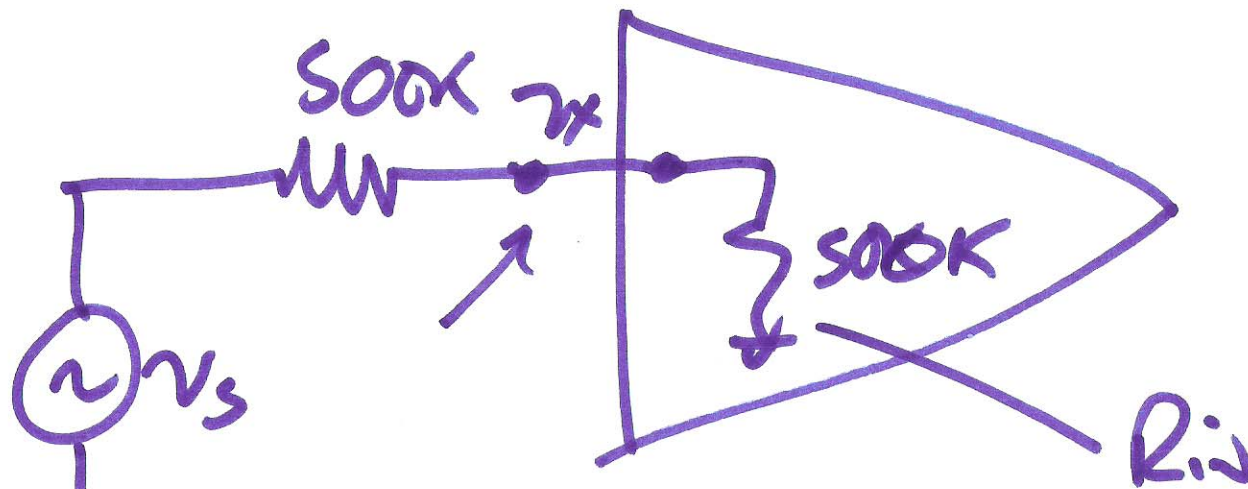

$$v_x = v_s = \frac{500K \cdot v_s}{500K + 500K}$$

$$v_x = \frac{v_s}{2}$$

4)

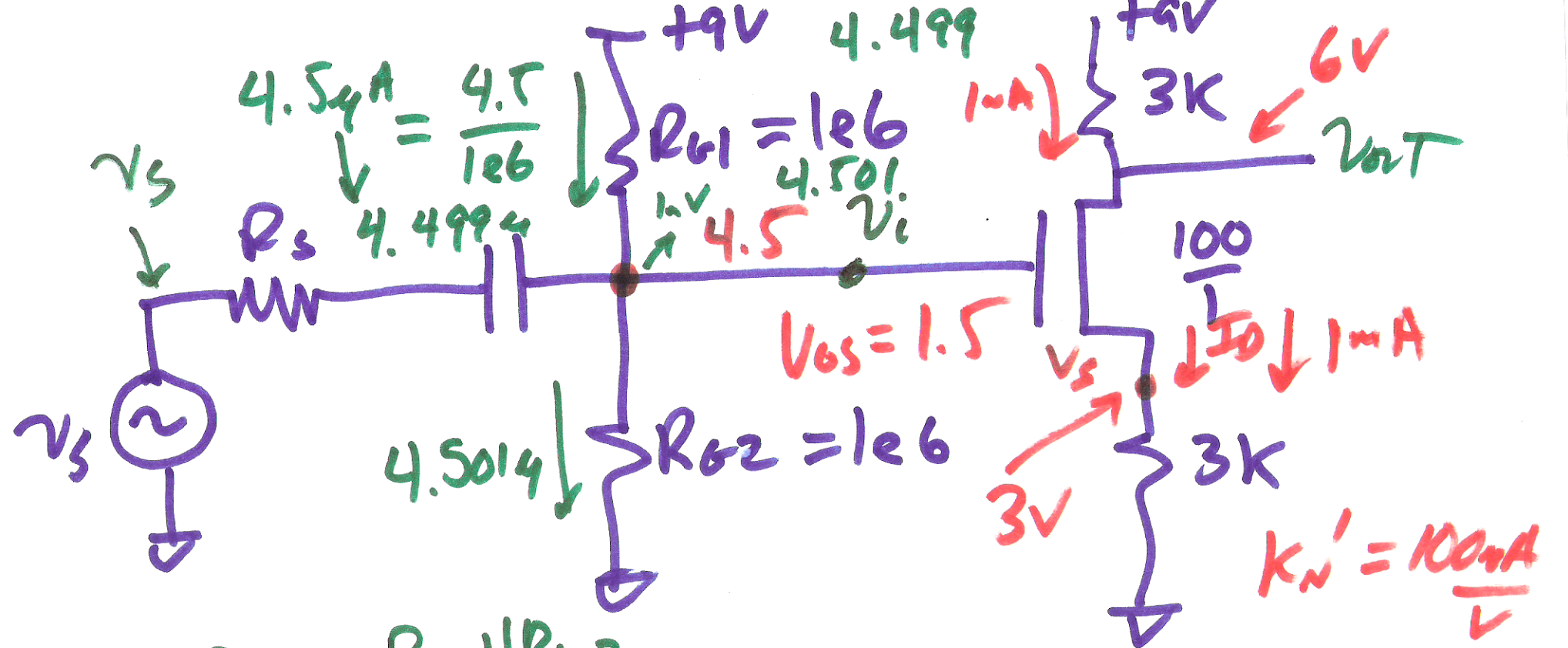

$$v_i = v_s \cdot \frac{R_{L1} \parallel R_{L2}}{R_{L1} \parallel R_{L2} + R_s} v_s = I_b \cdot 3k$$

$$K_N' = \frac{100 \mu A}{V}$$

$$V_{TN} = .75$$

$V_i = V_s$


$$I_D = \frac{K_n' \cdot \frac{W}{L}}{2} (V_{GS} - V_{THN})^2$$

$$I_D = \frac{100 \mu A}{V^2 \cdot 2} \cdot \frac{100}{1} (4.5 - I_D \cdot 3k - 0.75)^2$$


UNLV

CMOSedu.com

5)

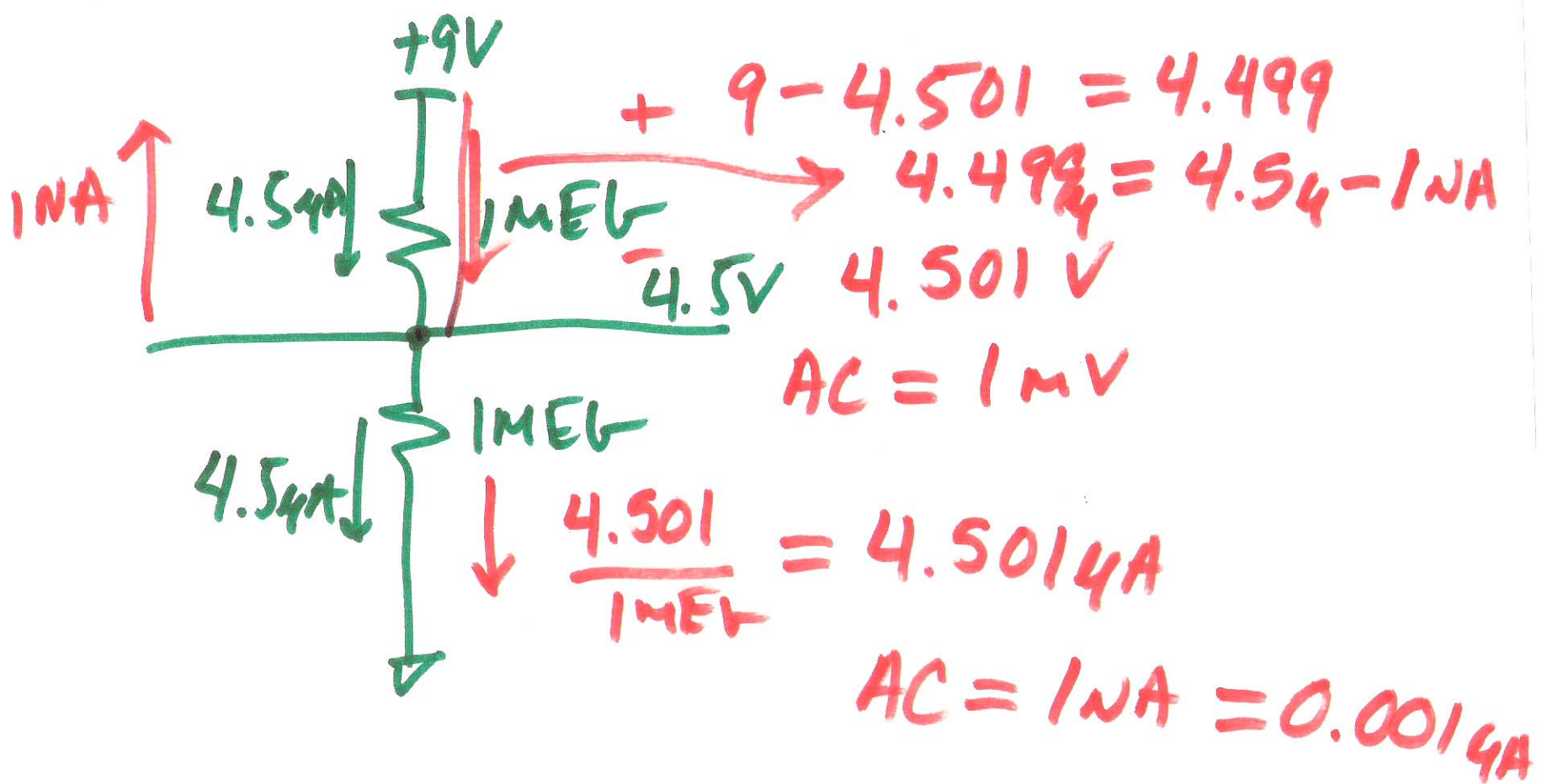

6)

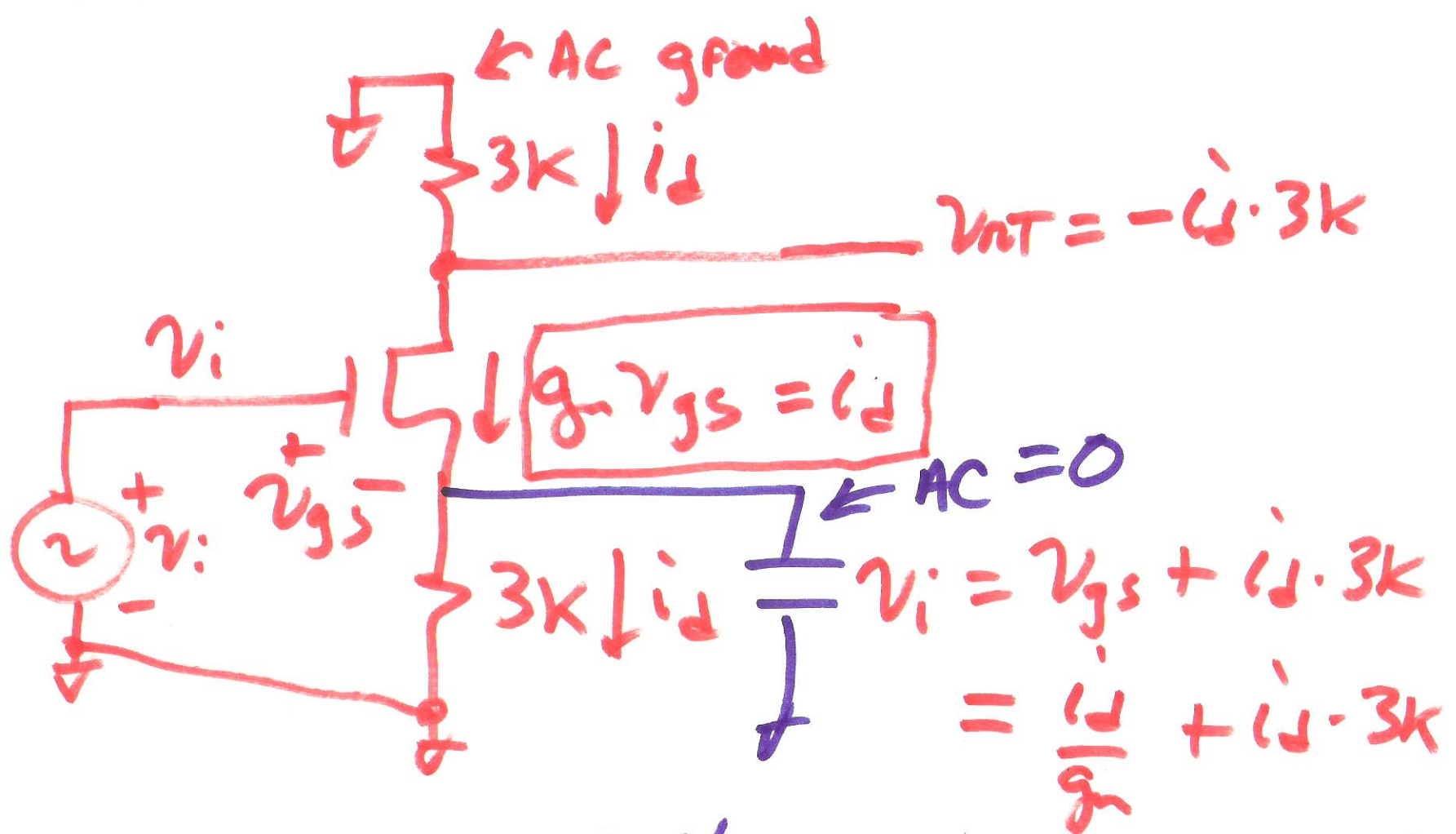

$i_d \uparrow \downarrow 3k$

$I \downarrow R$

$I \cdot R = V$

$v_i = i_d \left(\frac{1}{g_m} + 3k \right)$

$$\frac{v_{out}}{v_i} = \frac{-3k}{\frac{1}{g_m} + 3k} = \underline{\underline{-g_m 3k}}$$

$$g_m = \frac{K_n' \cdot W}{L} (V_{GS} - V_{TH})$$


$$= \frac{100 \mu A}{V^2} \cdot \frac{100}{1} (1.5 - .75)$$


$$g_m = K_n' \cdot \frac{W}{L} (V_{GS} - V_{TH}) = \frac{10 \text{ mA}}{V} \cdot 7.5 = 7.5 \frac{\mu A}{V}$$

$$\frac{v_{out}}{v_i} = -g_m 3k = -7.5 \frac{\mu A}{V} \cdot 3k$$

$$= -\frac{22.5 V}{16.5 V}$$

8)

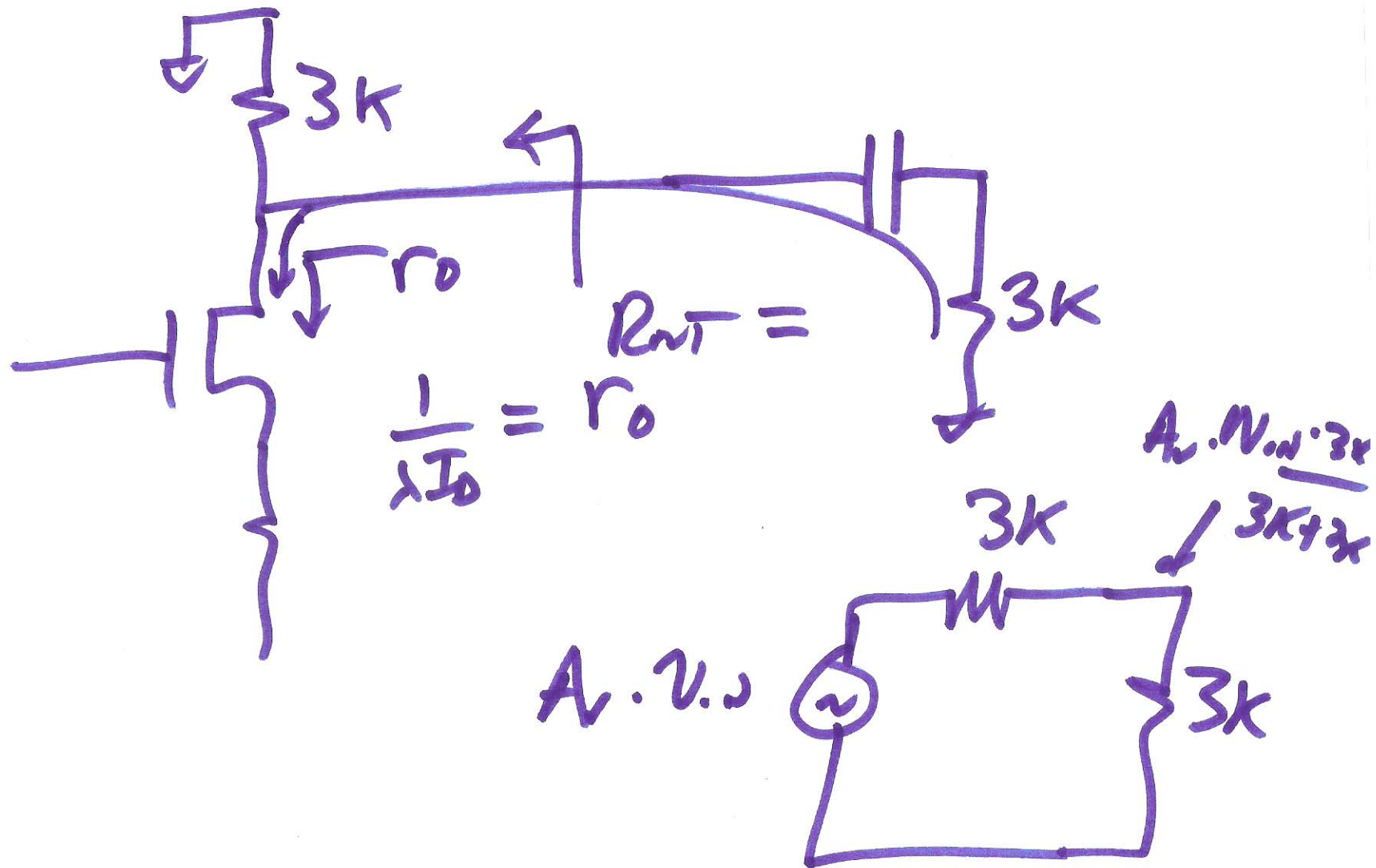

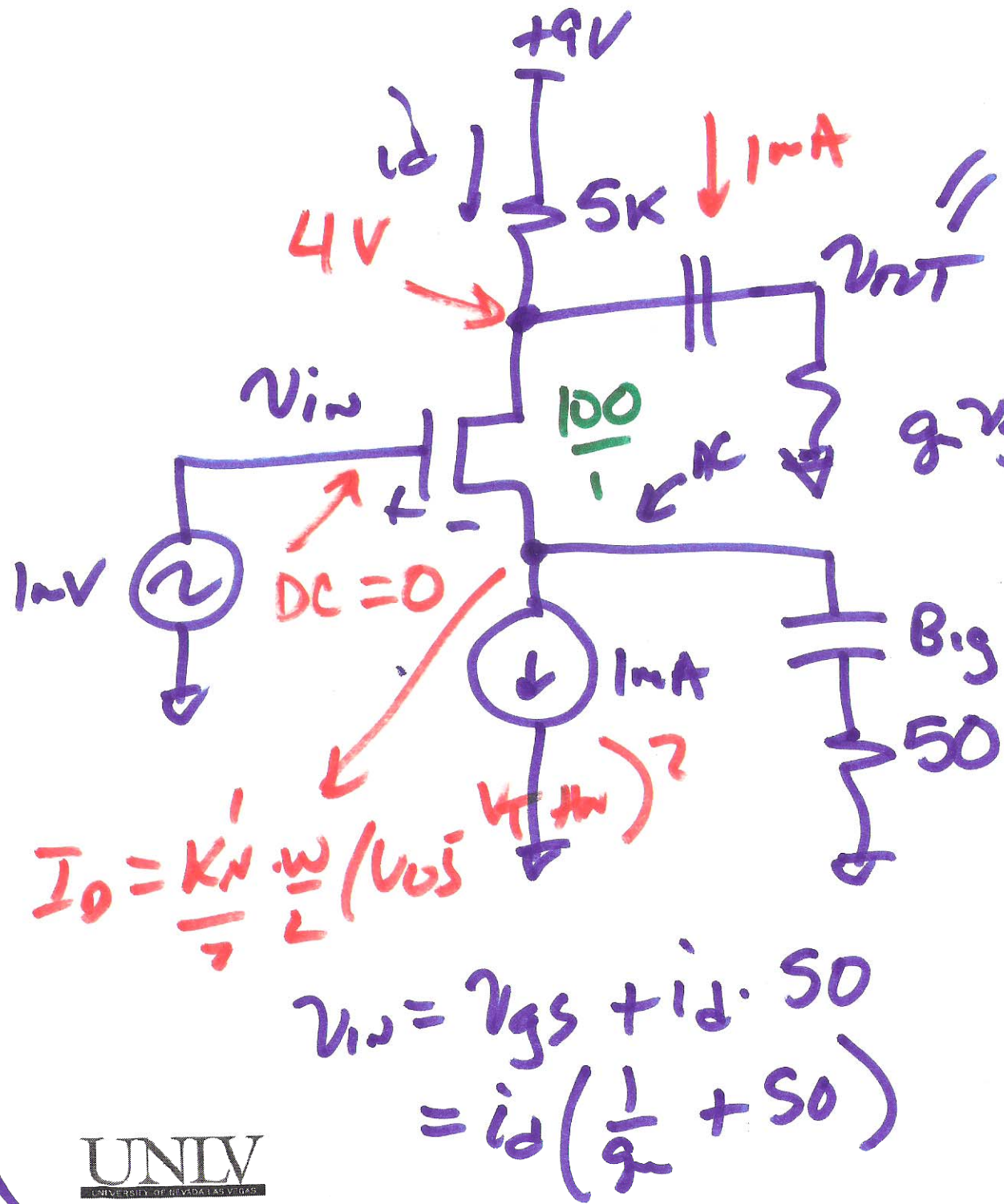

$$\frac{v_{NT}}{v_{i0}} \Big|_{\text{no load}} = -i_d \cdot 5K$$

$$g_m v_{gs} = i_d \quad \text{With } 5K \text{ load}$$

$$g_m = \sqrt{2 \cdot k_n' \cdot \frac{W}{L} \cdot I_{DQ}}$$

$$= \sqrt{2 \cdot 100 \mu A/V^2 \cdot 100 \cdot 1mA}$$

$$= \sqrt{20 mA/V^2 \cdot 1mA}$$

$$= \sqrt{20e-3 \cdot 1mA}$$


$$3.4 mA/V$$

$$I_D = \frac{k_n'}{2} \cdot \frac{W}{L} (V_{GS} - V_t)^2$$

$$v_{in} = v_{gs} + i_d \cdot 50$$

$$= i_d \left(\frac{1}{g_m} + 50 \right)$$
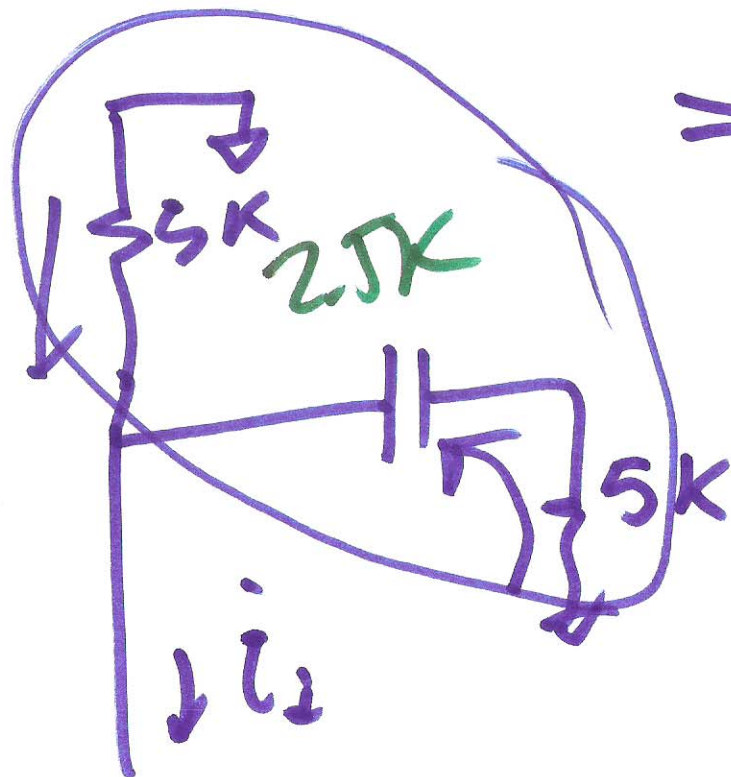
$$\frac{v_{nT}}{v_{in}} = \frac{-i_d \cdot 5K}{i_d \left(\frac{1}{g_m} + 50 \right)}$$



$$= \frac{-5K \rightarrow 2.5K}{\frac{1}{3.4\mu A} + 50}$$

$$= \frac{-5K}{344} = -14.5$$

$$\rightarrow -7.25$$