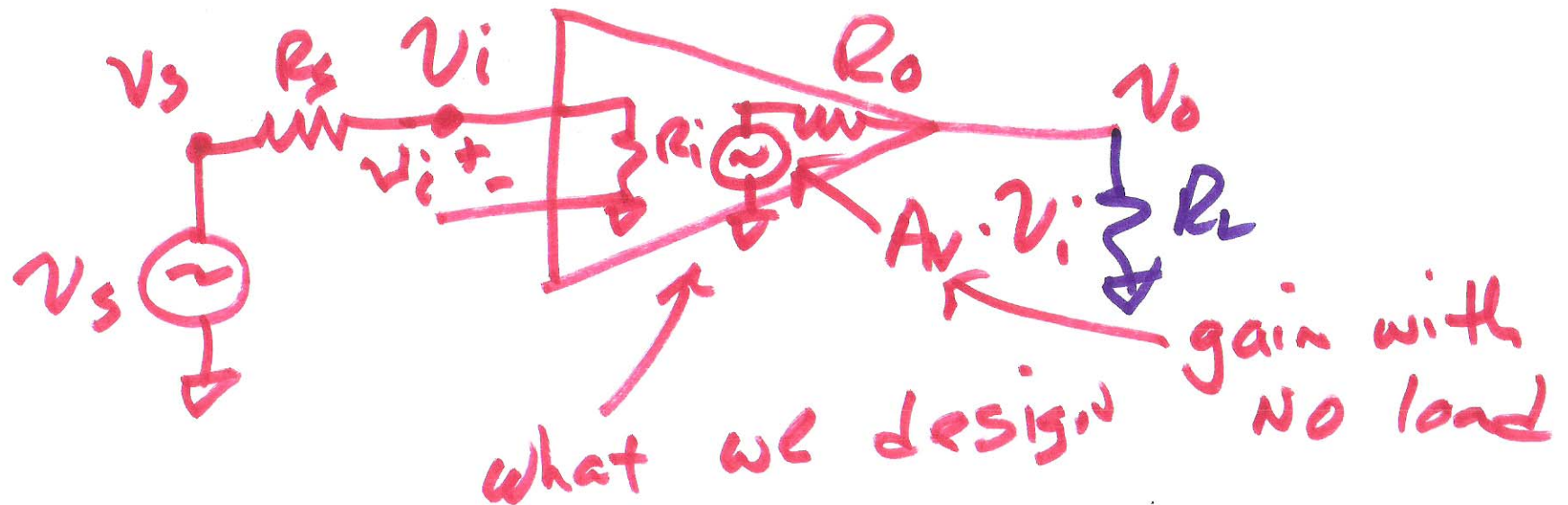


Lecture 18 EE 320

April 3, 2013

$$g_m = \sqrt{2K_P' \frac{W}{L} I_D}$$

$$= K_P' \frac{W}{L} (V_{GS} - V_{THN})$$




$$v_i = v_s \cdot \frac{R_i}{R_i + R_s}$$

$$v_o = A_v \cdot v_i \cdot \frac{R_L}{R_o + R_L}$$

$$\frac{v_o}{v_i} = A_v \cdot \frac{R_L}{R_o + R_L}$$

$$\frac{v_o}{v_i} = A_v \text{ when } R_L \rightarrow \infty \text{ (No load)}$$

2)

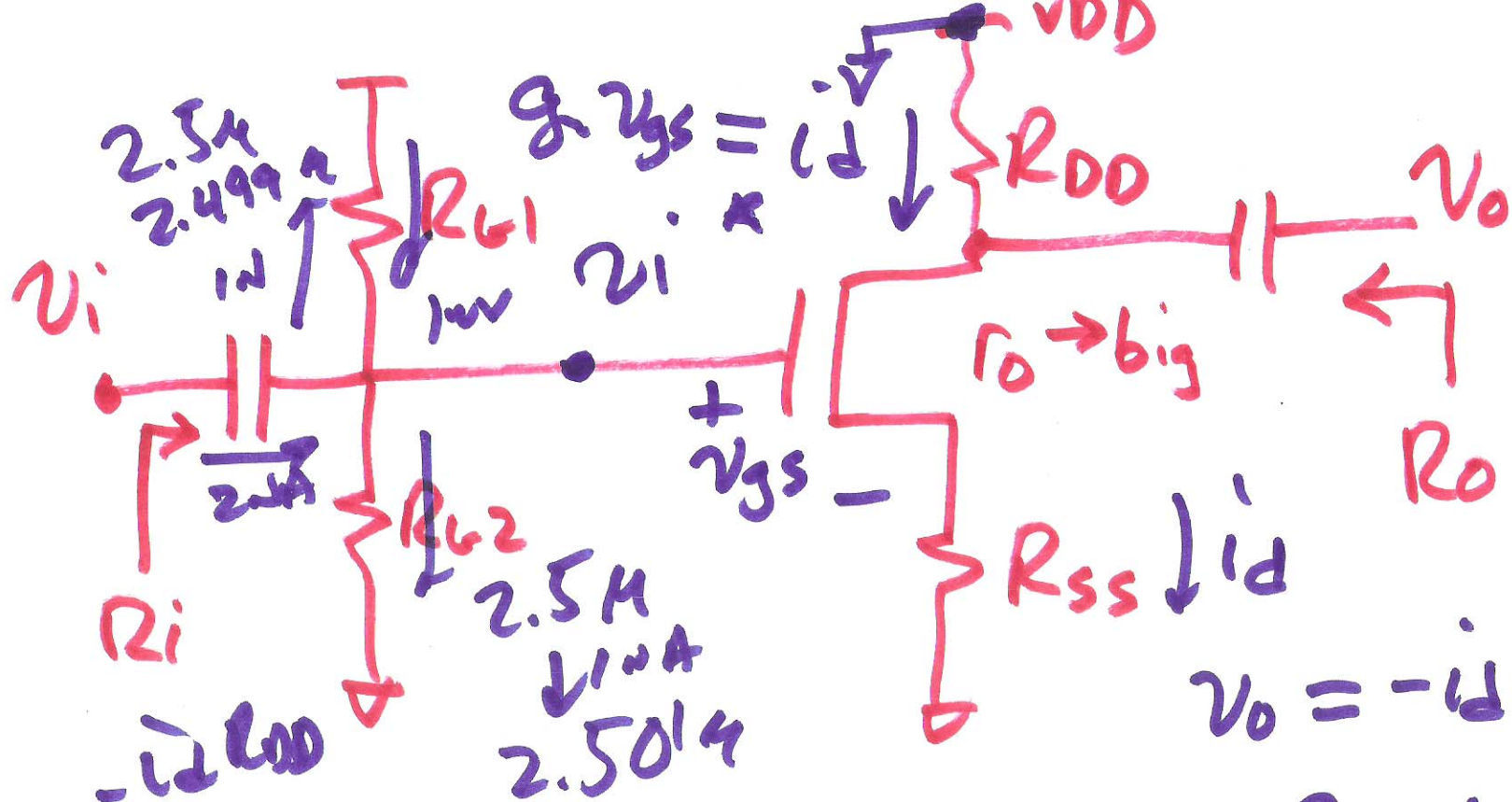

$$R_i = R_{G1} \parallel R_{G2}$$

$$R_o = R_{OD}$$


$$v_o = -i_d \cdot R_{OD}$$

$$v_i = v_{gs} + i_d \cdot R_{SS}$$

$$= i_d \left(\frac{1}{g_m} + R_{SS} \right)$$

$$A_v = \frac{v_o}{v_i} = \frac{-R_{OD}}{\frac{1}{g_m} + R_{SS}}$$

CMOSedu.com

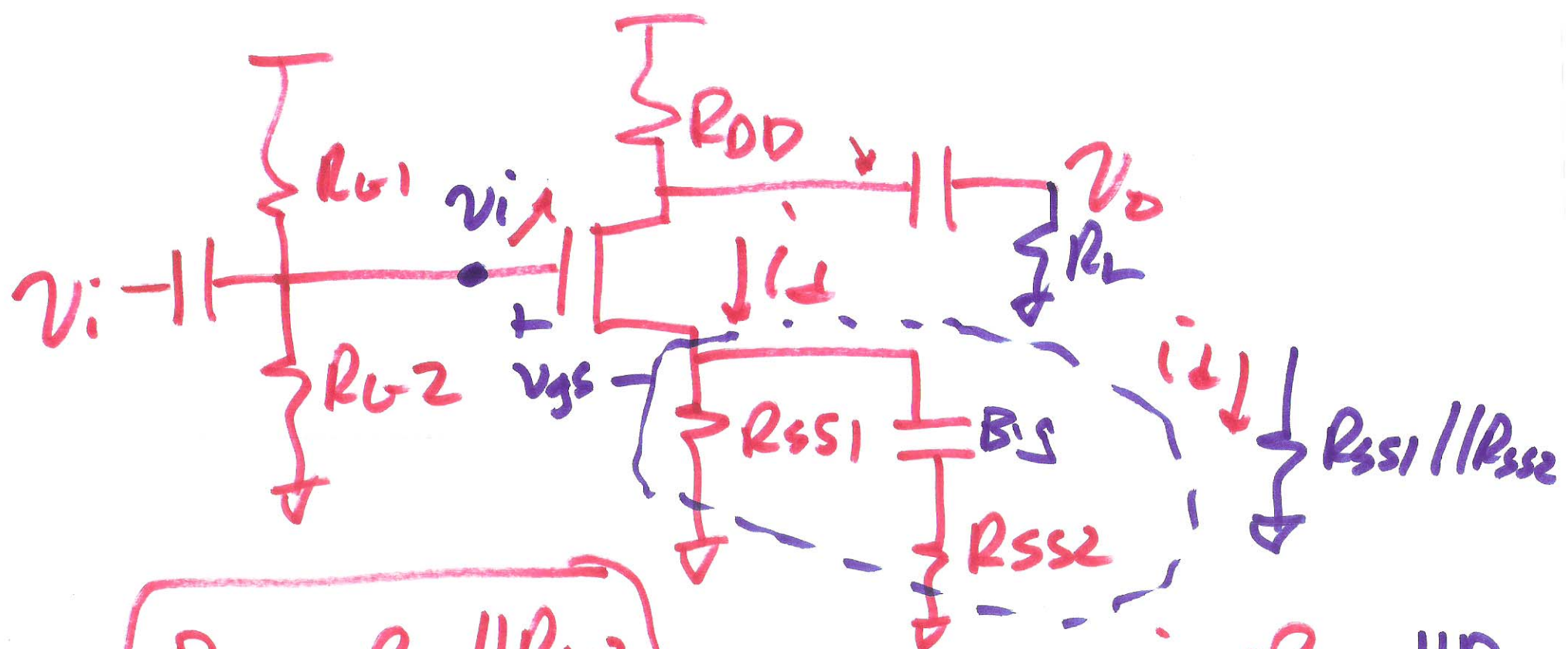


$$R_{in} = R_{G1} \parallel R_{G2}$$

$$R_o = R_{DD}$$

$$\frac{v_o}{v_i} = A_v = \frac{-R_{DD} \parallel R_L}{\frac{1}{g_m} + R_{S1} \parallel R_{S2}}$$

$$v_o = -i_d \cdot R_{DD} \parallel R_L$$
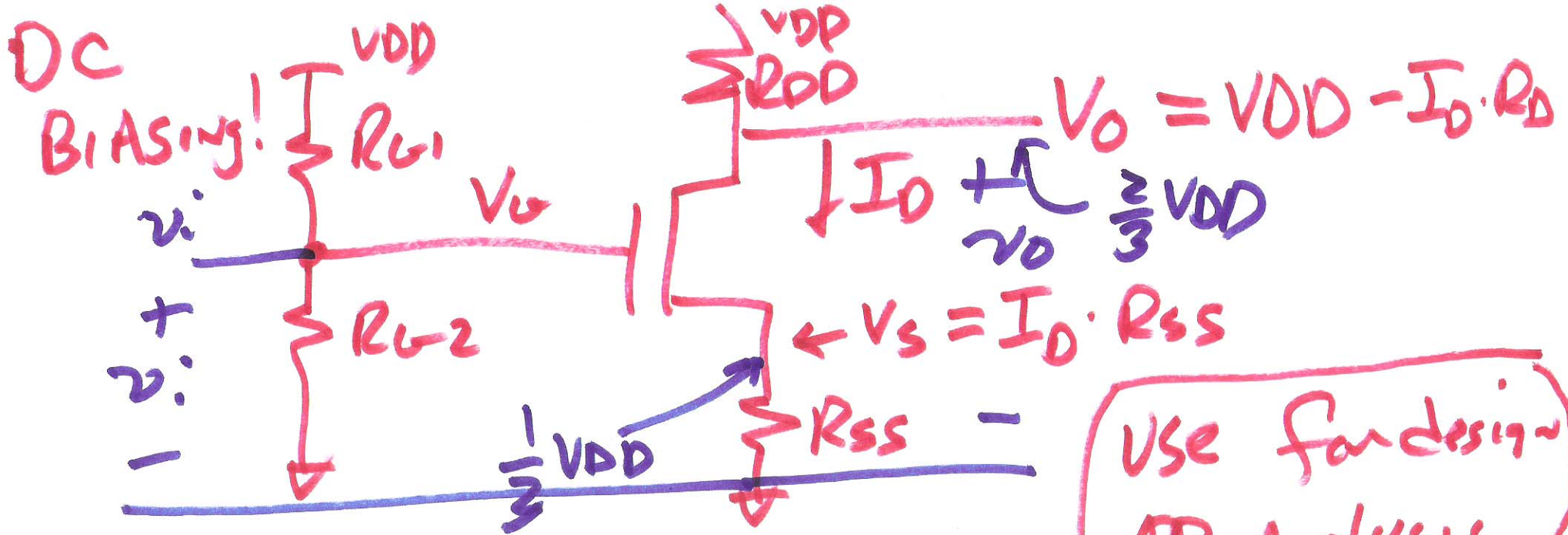
$$v_i = v_{gs} + i_d R_{S1} \parallel R_{S2} \\ = i_d \left(\frac{1}{g_m} + R_{S1} \parallel R_{S2} \right)$$




Use for design
OR Analysis


$$V_{GS} = V_G - V_S = \frac{V_{DD} \cdot R_{G2}}{R_{G2} + R_{G1}} - I_D \cdot R_{SS}$$


$$I_D = \frac{K_n'}{2} \cdot \frac{W}{L} (V_{GS} - V_{THN})^2$$

MAX OUTPUT

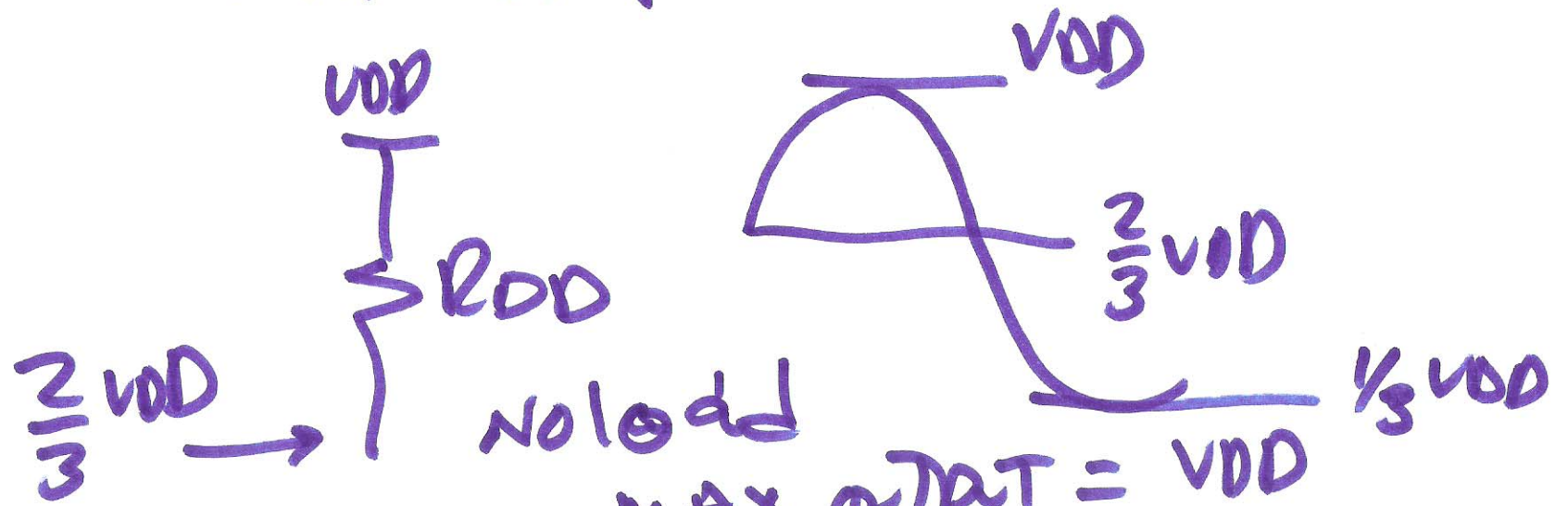

swing = $\frac{1}{3} V_{DD}$

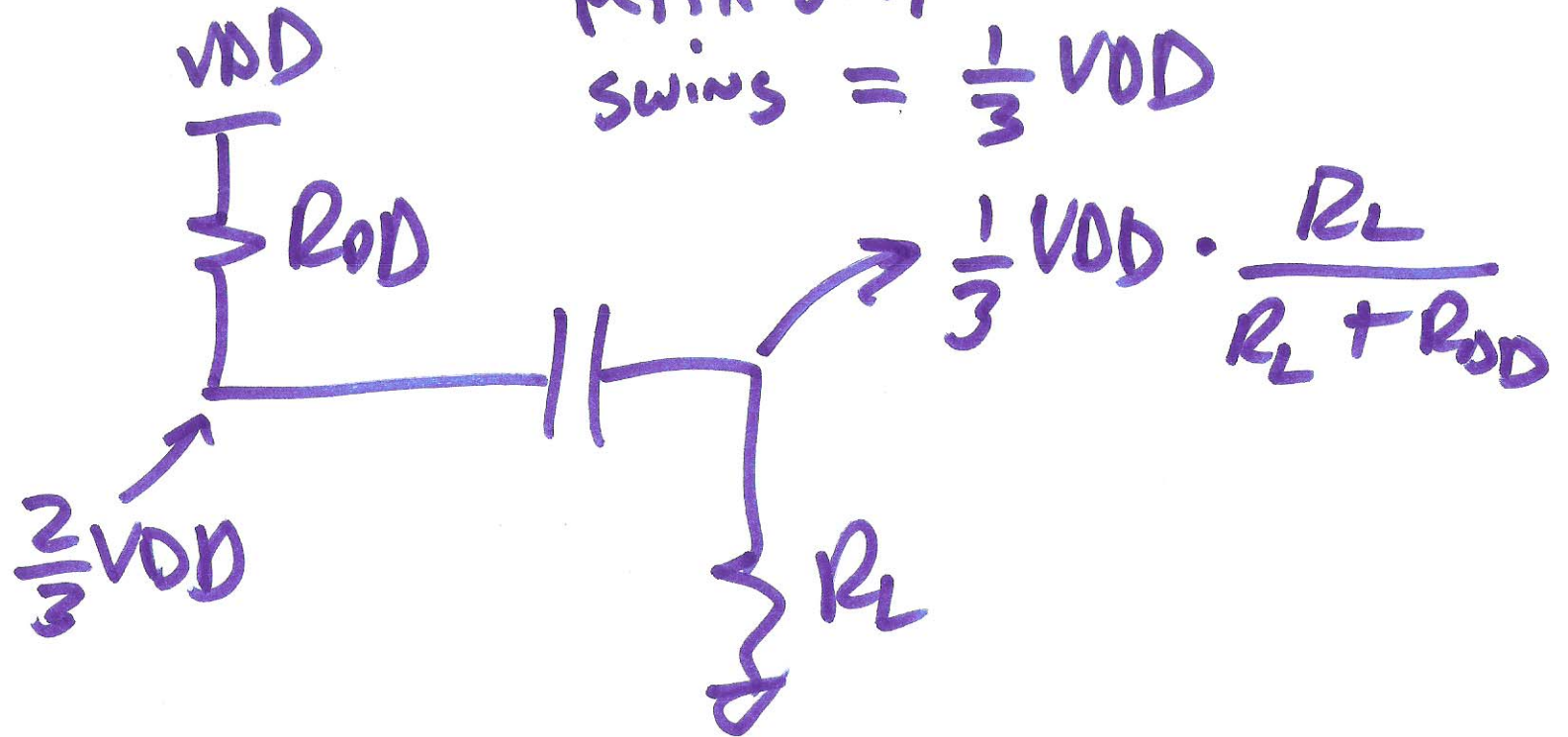

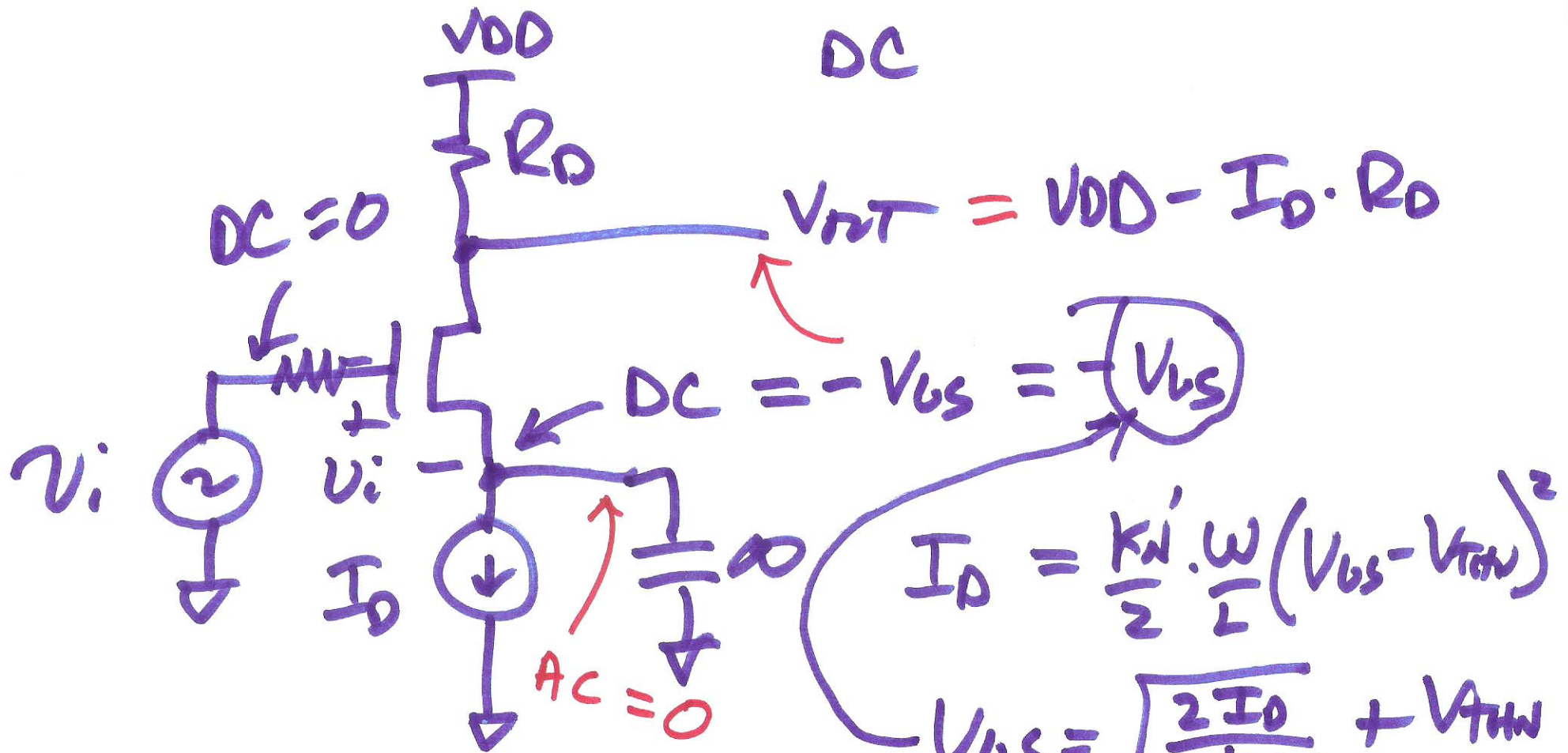

$$R_i = \infty$$

$$R_o = R_D$$


$$g_m = \sqrt{2I_D \cdot k'_n \cdot \frac{W}{L}}$$

$$v_o = -i_d \cdot R_D$$

$$v_i = v_{gs} = \frac{i_d}{g_m}$$

$$\frac{v_o}{v_i} = A_v = -\frac{R_D}{\frac{1}{g_m}}$$

$$= -g_m R_D$$

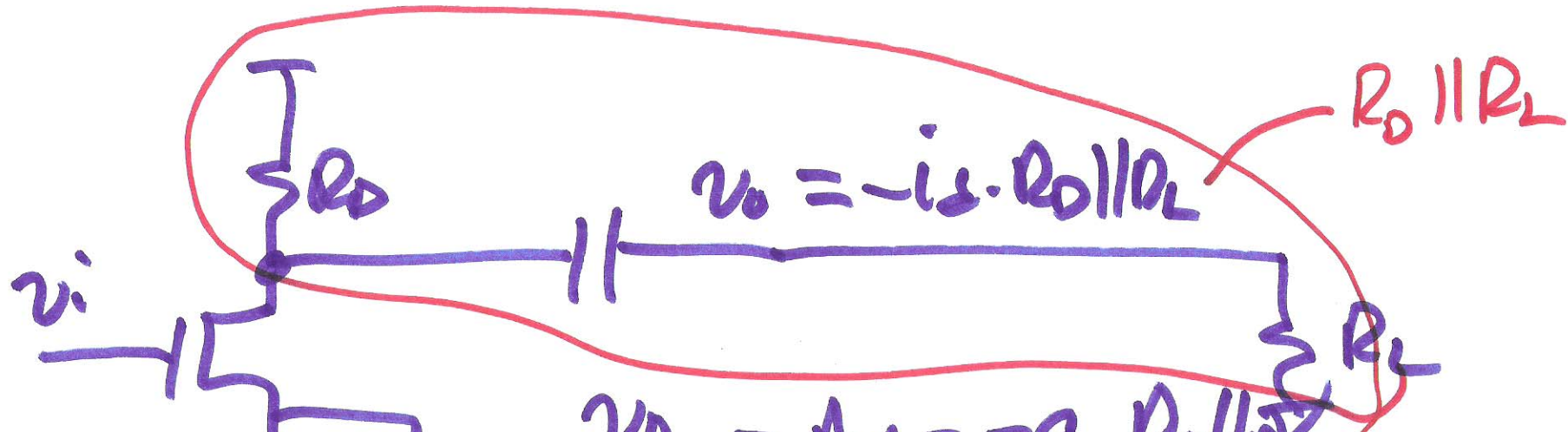


$$\frac{v_o}{v_i} = A_v = -g_m R_D || R_L$$


$$\frac{v_o}{v_i} = -g_m R_D \cdot \frac{R_L}{R_D + R_L}$$


$$A_v = -g_m R_L || R_D$$

$$v_i = v_{gs} = \frac{i_d}{g_m}$$

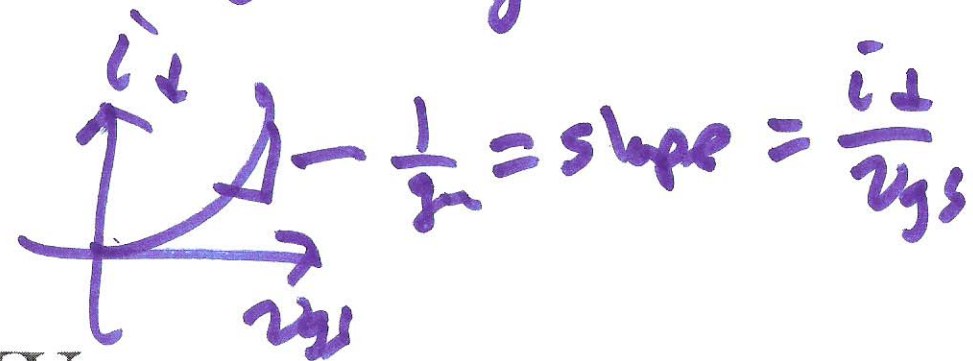

9)

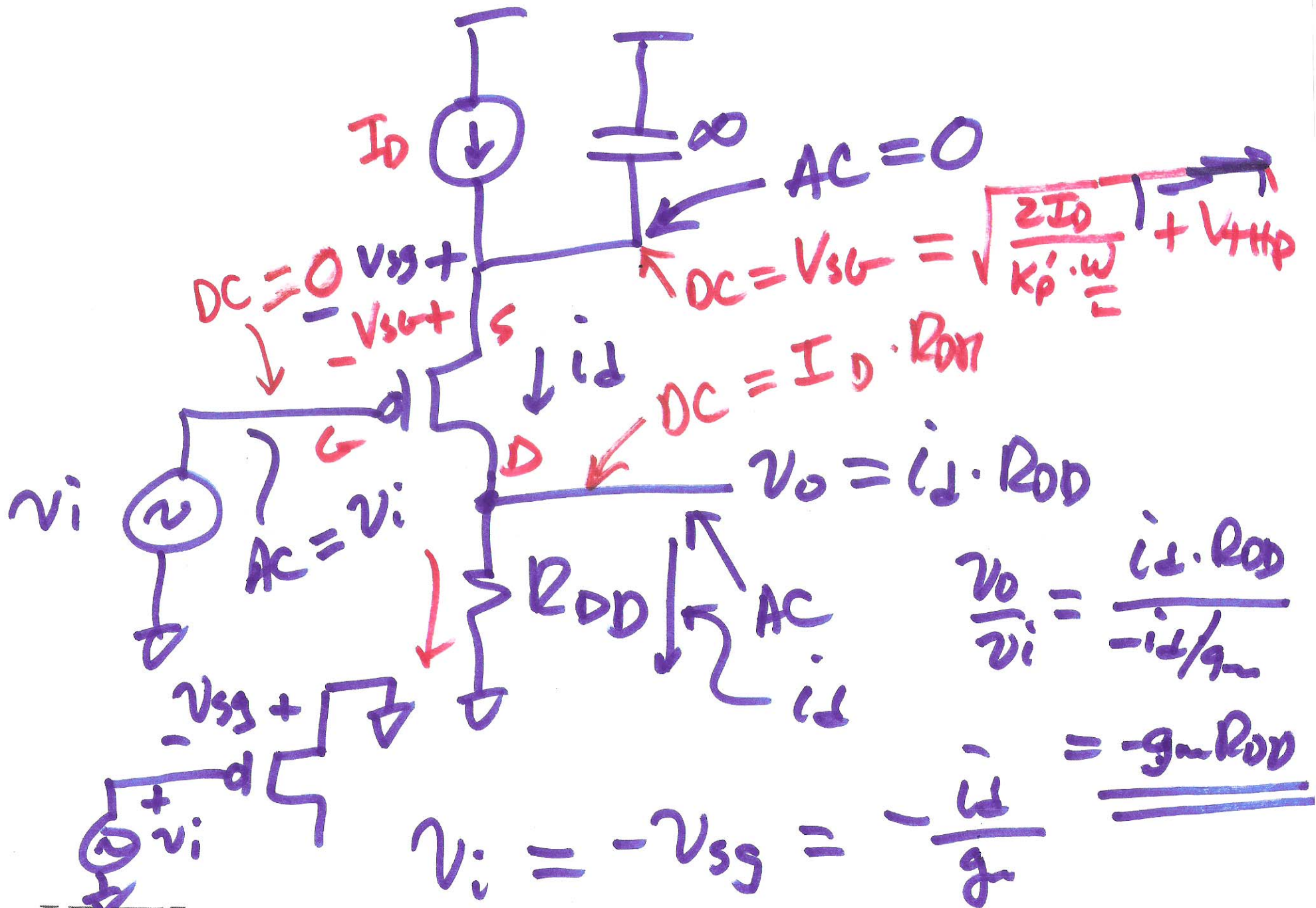

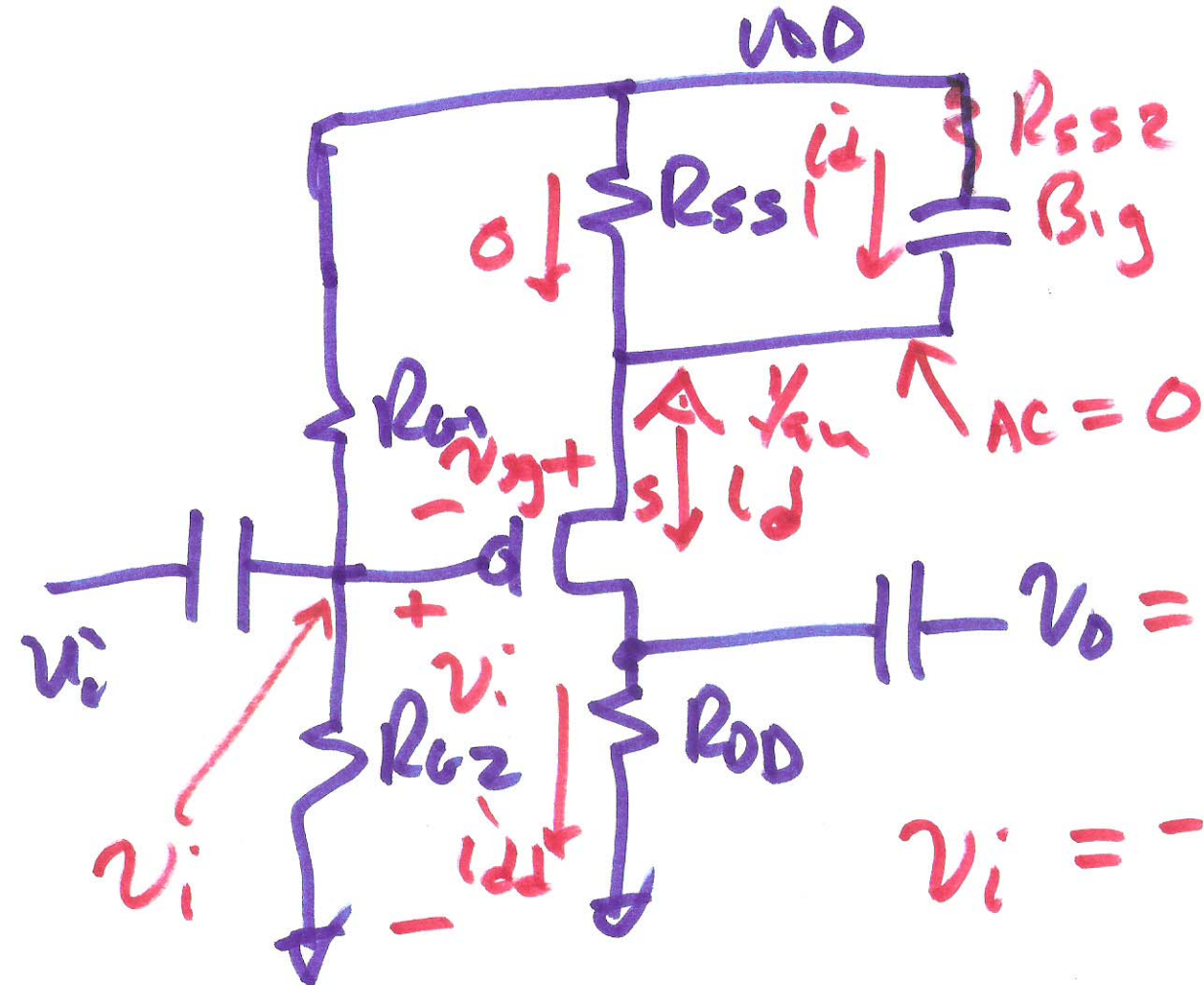

$$\frac{-R_{OD}}{\frac{1}{g_m} + R_{ss1} \parallel R_{ss2}}$$

$$v_o = R_{OD} \cdot i_d$$

$$v_i = -v_{sg} = -\frac{i_d}{g_m}$$

$$\begin{aligned} \frac{v_o}{v_i} &= \frac{R_{OD} \cdot i_d}{-\cancel{i_d} / g_m} \\ &= -g_m R_{OD} \end{aligned}$$