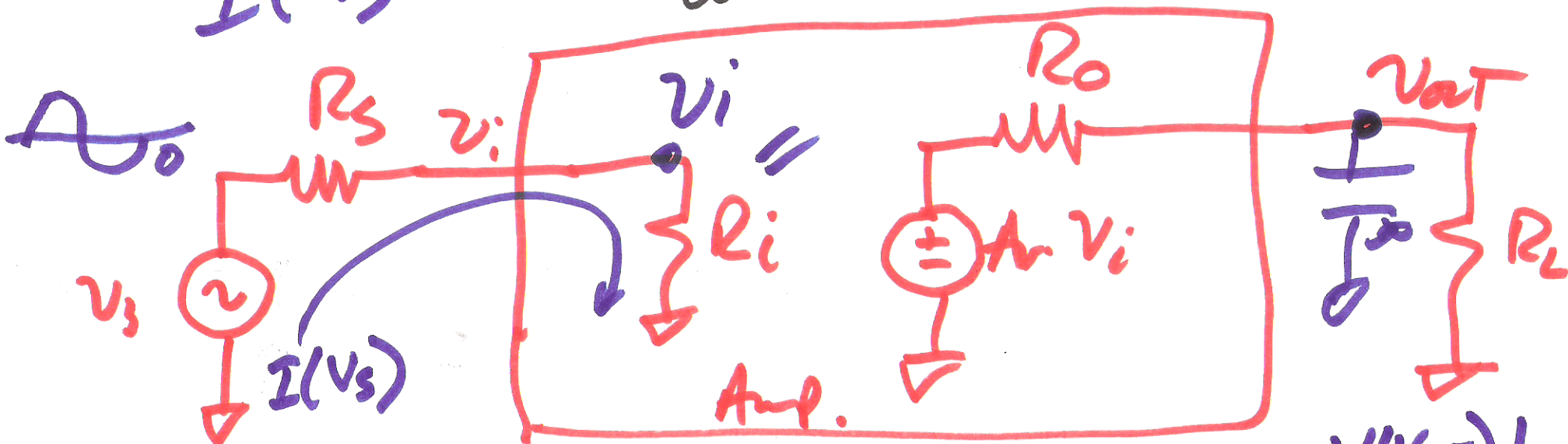


$$R_i = \frac{V(v_i)}{I(V_s)} \quad \text{EE 320}$$

WALK QUIZ

$$R_L \rightarrow \infty \quad v_{out} = A_v v_i$$



$$v_i = v_s \cdot \frac{R_i}{R_i + R_s}, \quad A_v = \frac{v_{out}}{v_i}$$


$$R_o = \frac{V(v_{out})|_{R_L=\infty}}{I(R_L)|_{R_L=\infty}}$$

$$v_{out} = A_v \cdot v_i \cdot \frac{R_L}{R_L + R_o}$$

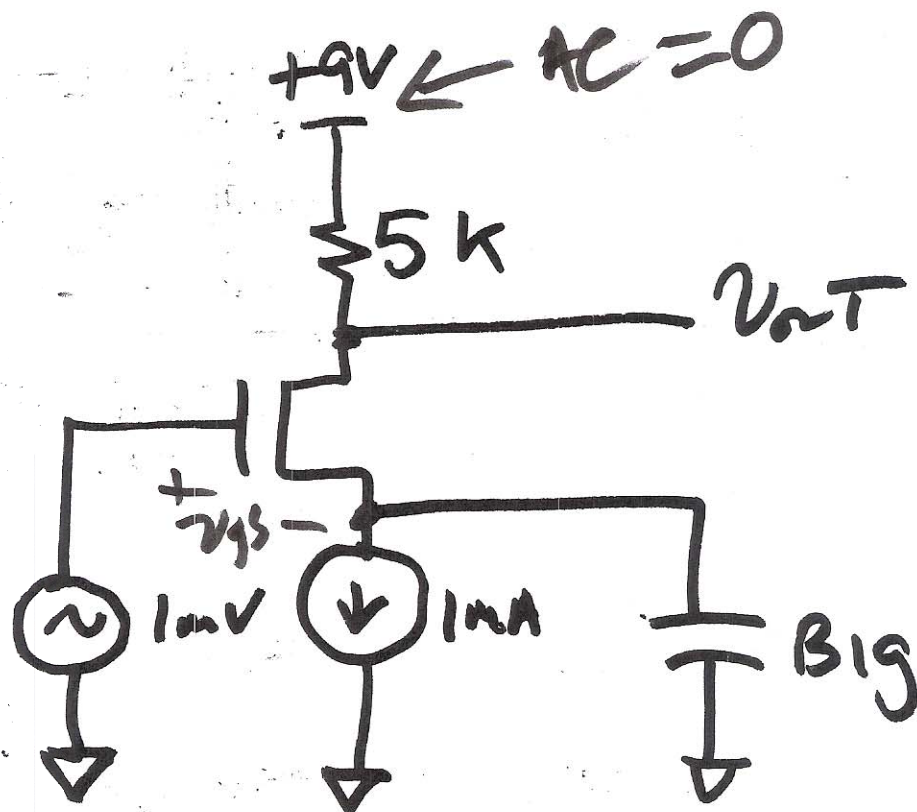Q10 EE 520 MTH 513

For the following determine:

$I_D, i_d, V_{out}, v_{out}$ if $g_m = 1 \text{ mA/V}$



$$I_D = 1 \text{ mA}$$

$$V_{out} = 9 - 5k \cdot 1 \text{ mA} = 4 \text{ V}$$

$$v_{gs} = 1 \text{ mV}$$

$$i_d = g_m v_{gs} = 1 \text{ mA/V} \cdot 1 \text{ mV} = 1 \text{ } \mu\text{A}$$

$$V_{out} = -i_d \cdot 5k$$


$$= -1 \text{ } \mu\text{A} \cdot 5k$$

$$= -5 \text{ mV}$$

$$i_d = 1 \text{ } \mu\text{A}$$

$$\frac{v_{out}}{v_{in}} = -5$$


2)

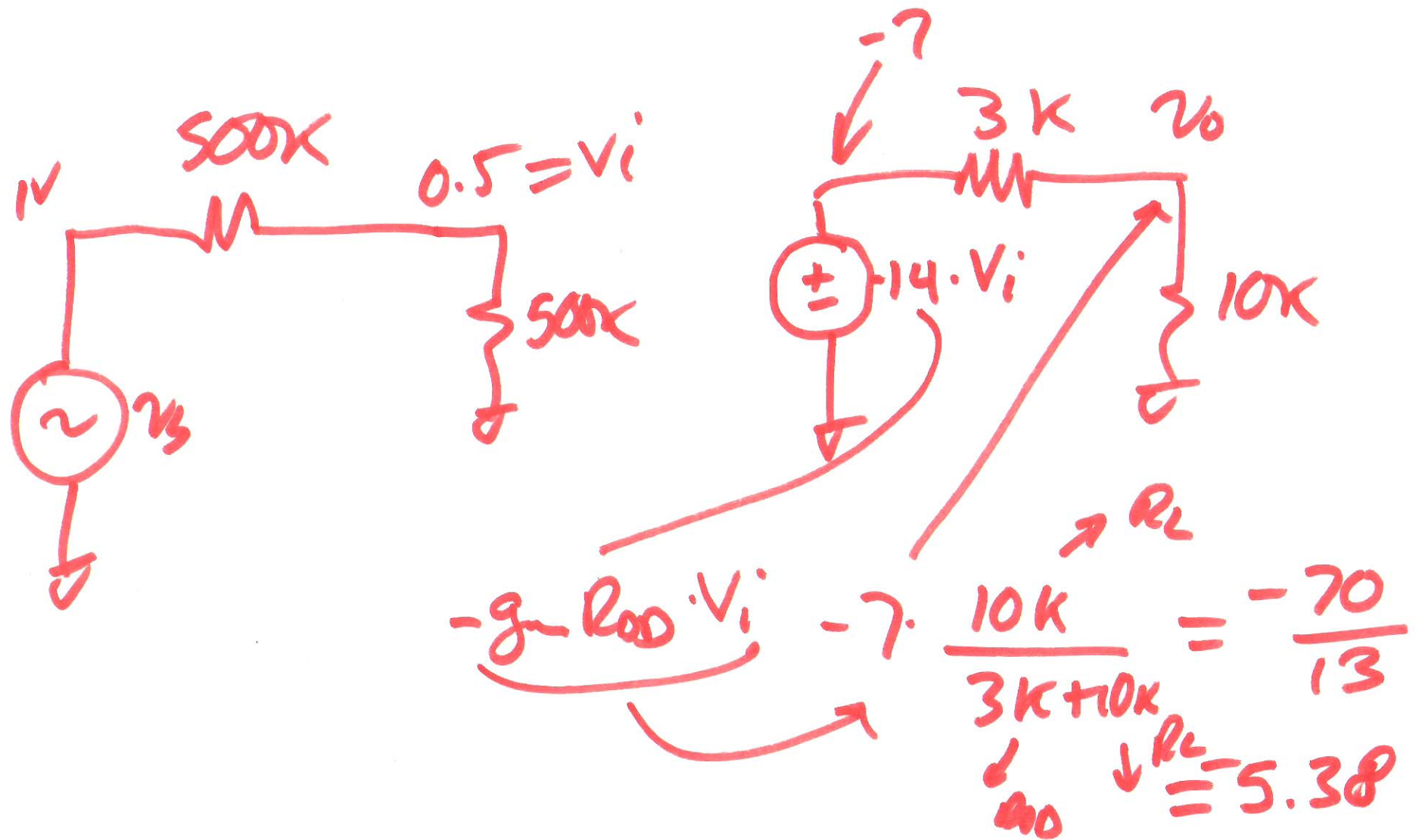

$$V_o = \frac{-g_m V_i \cdot R_{oo} \cdot R_L}{R_{oo} + R_L}$$


$$\frac{V_o}{V_i} = -g_m R_{oo} \parallel R_L$$

3)

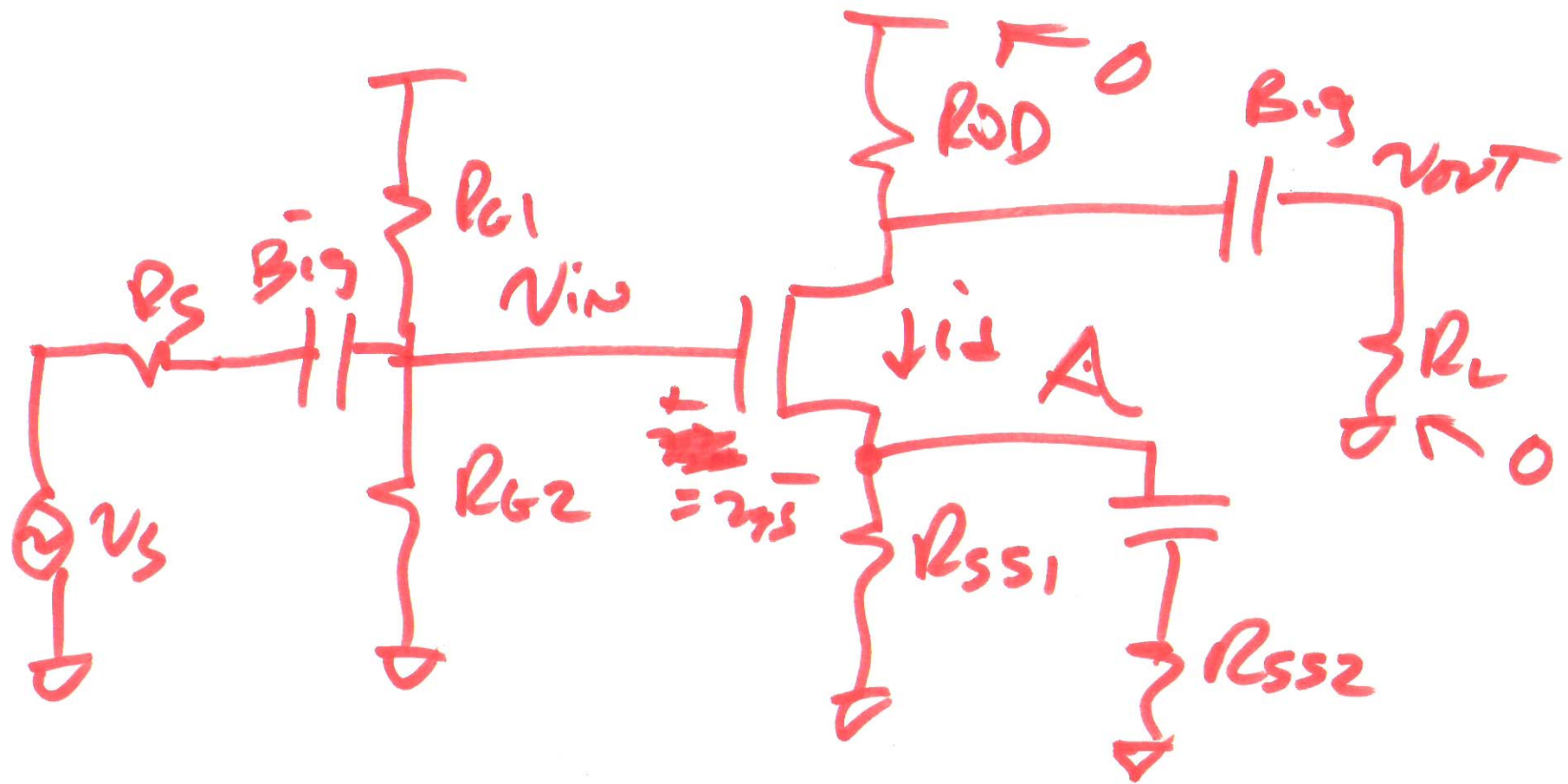


$$\begin{aligned}
 \frac{v_{OUT}}{v_{in}} &= \frac{-i_D \cdot R_L \parallel R_{DD}}{\frac{i_D}{g_m} + i_D \cdot R_{SS1} \parallel R_{SS2} - R_L \parallel R_{DD}} \\
 &= \frac{-R_L \parallel R_{DD}}{\frac{1}{g_m} + R_{SS1} \parallel R_{SS2}}
 \end{aligned}$$

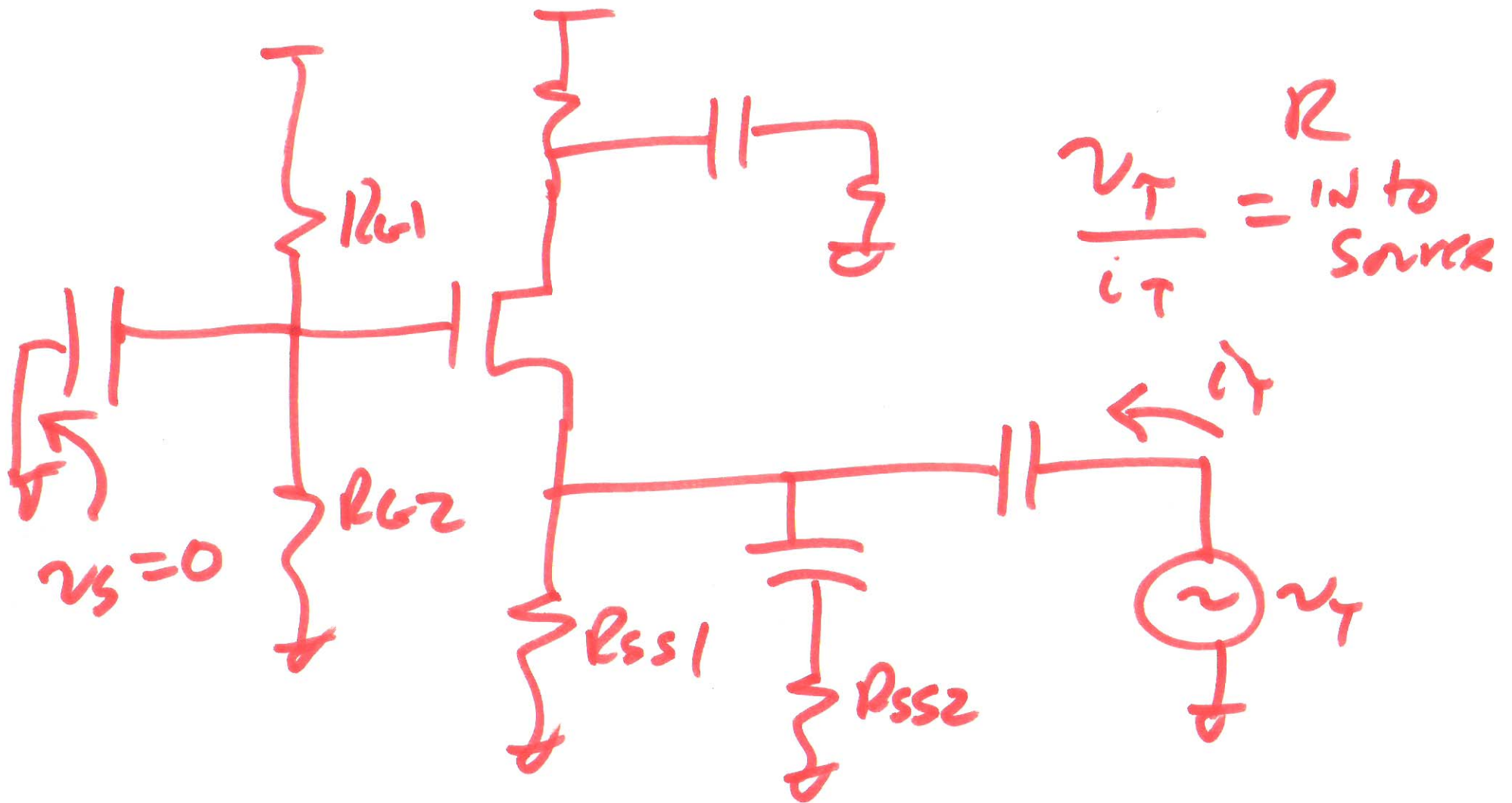v_{gs} → $\frac{i_D}{g_m}$
 i_D source → $R_{SS1} \parallel R_{SS2}$
 i_D drain → $-R_L \parallel R_{DD}$




5)

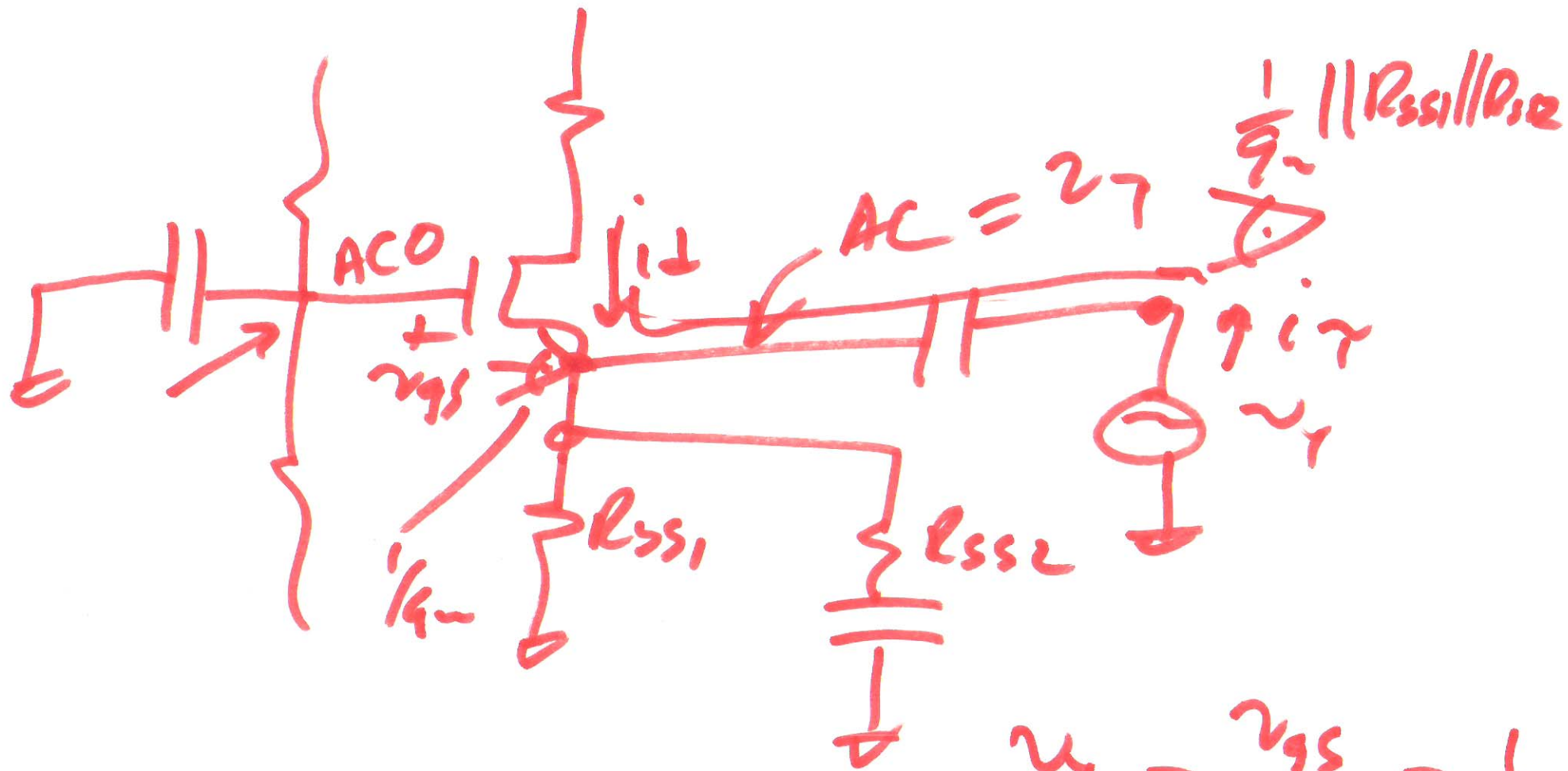

$$v_{gs} = -v_T \quad \frac{v_T}{i_T} = \frac{v_{gs}}{i_d} = \frac{1}{g_m}$$

$$i_d = -i_T$$


6)

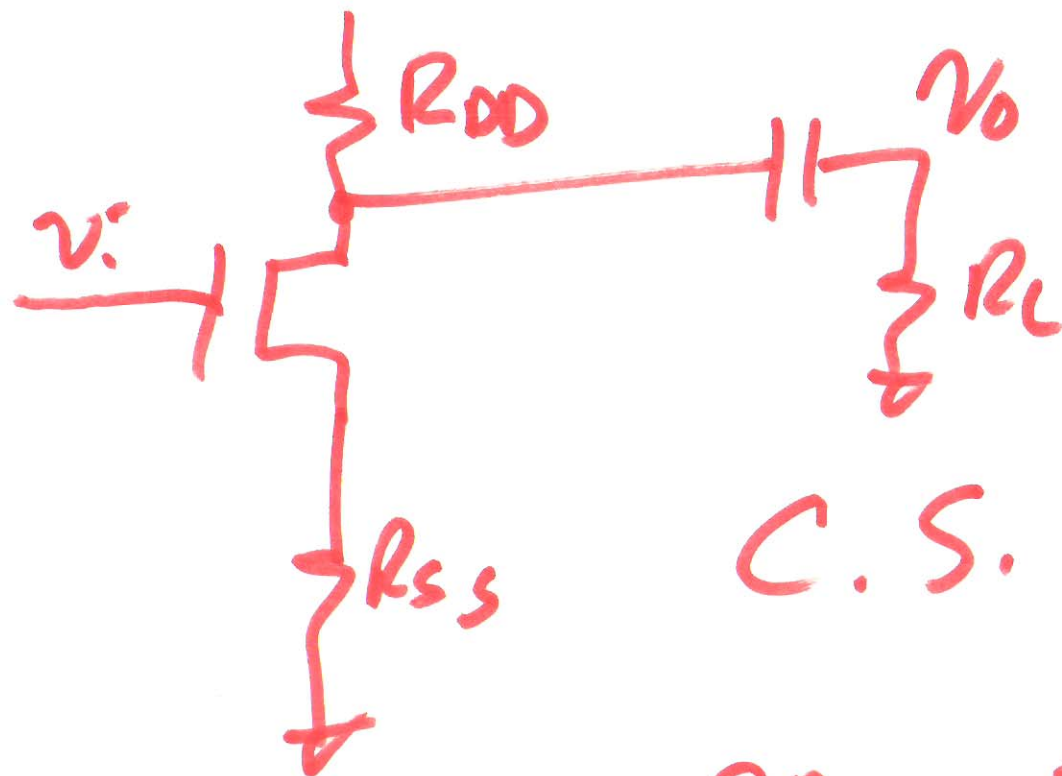

$$\frac{v_o}{v_i} = \frac{-R_{DD} \parallel R_L}{\frac{1}{g_m} + R_{SS}}$$

C.S.

CD = SF

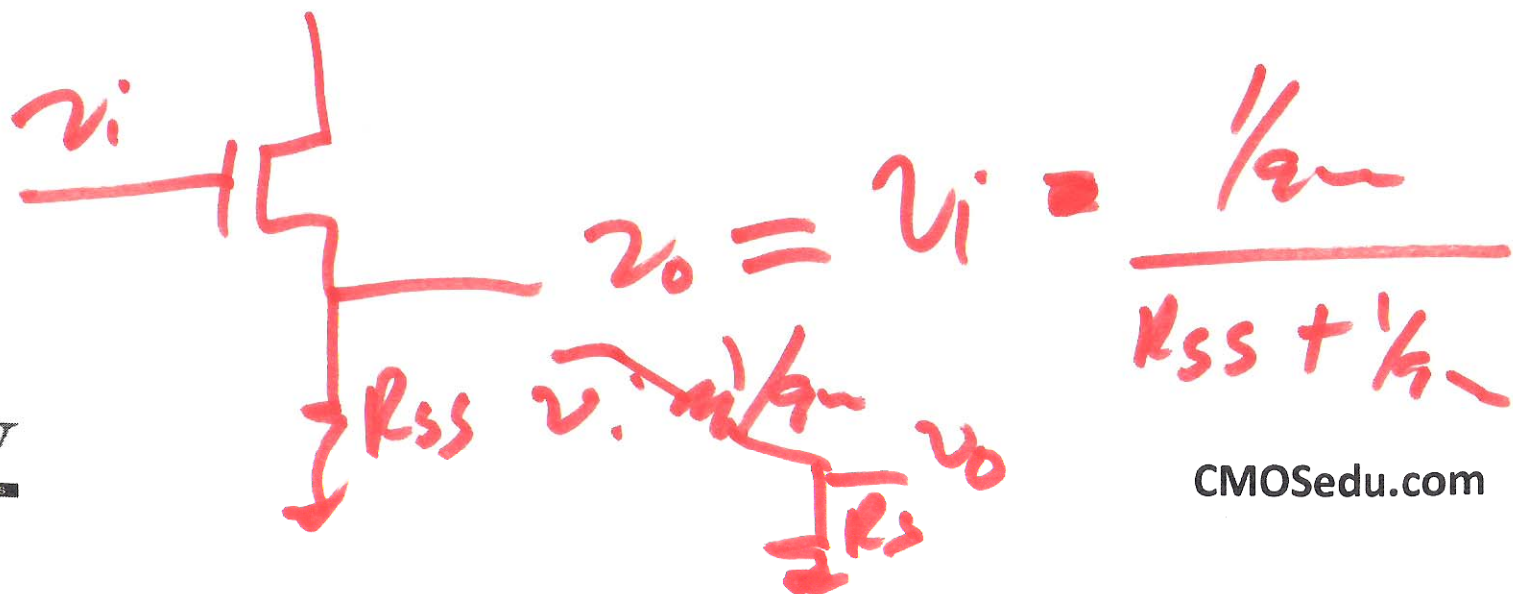

$$v_o = v_i = \frac{\frac{1}{g_m}}{R_{SS} + \frac{1}{g_m}}$$