
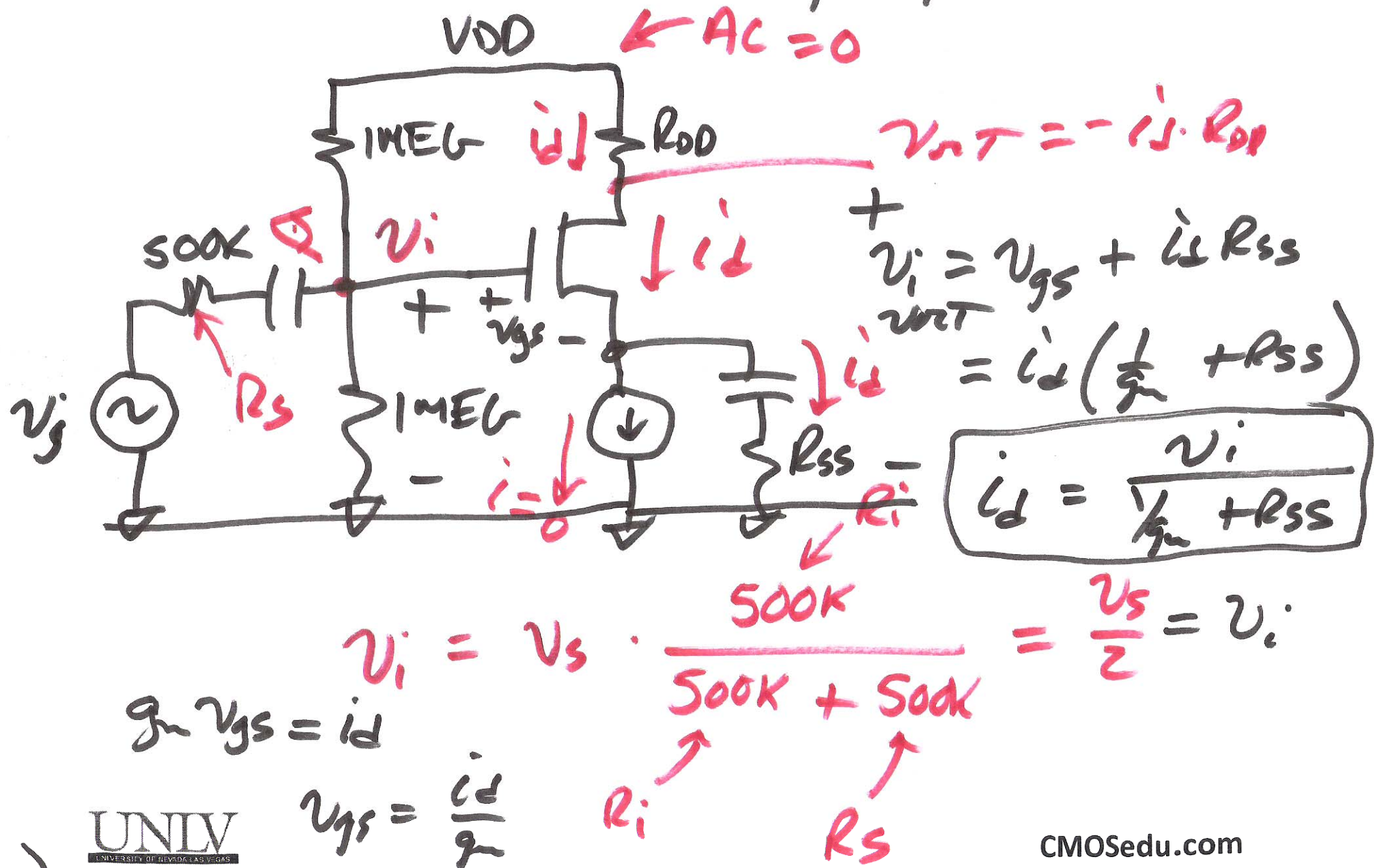


4/15/13

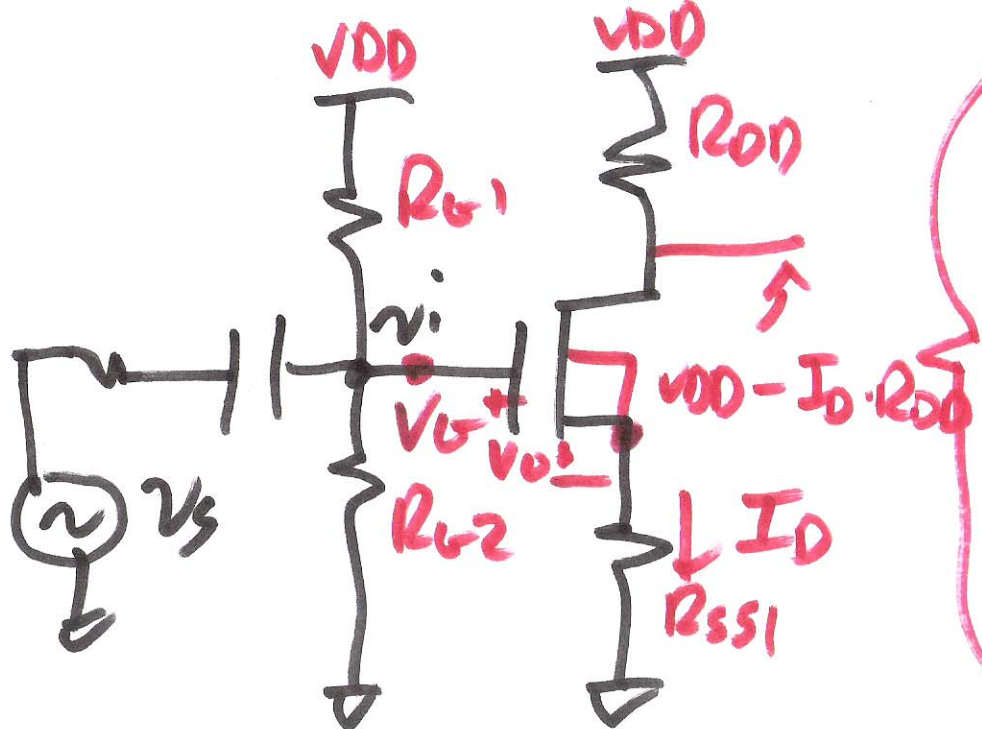



$$V_G = V_{GS} + I_D \cdot R_{SS1}$$


$$I_D = \frac{K'_n}{2} \cdot \frac{W}{L} (V_{GS} - V_{THN})^2$$


$$V_{GS} = \sqrt{\frac{2 I_D}{K'_n \cdot \frac{W}{L}}} + V_{THN}$$

$$V_G = \frac{V_{DD} \cdot R_{G2}}{R_{G1} + R_{G2}}$$




MISTAKE

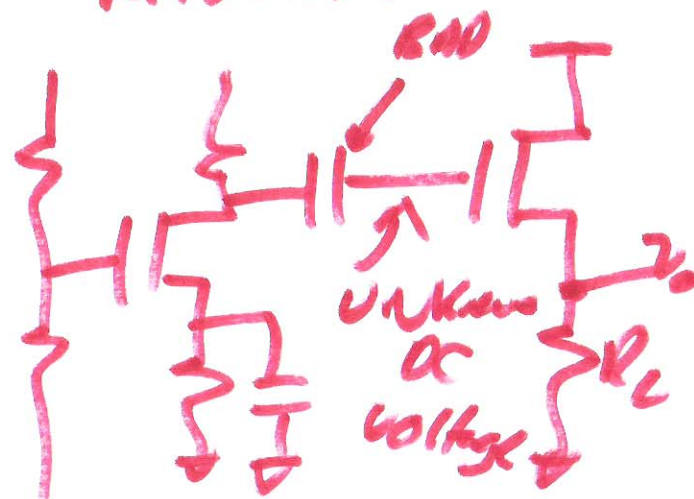


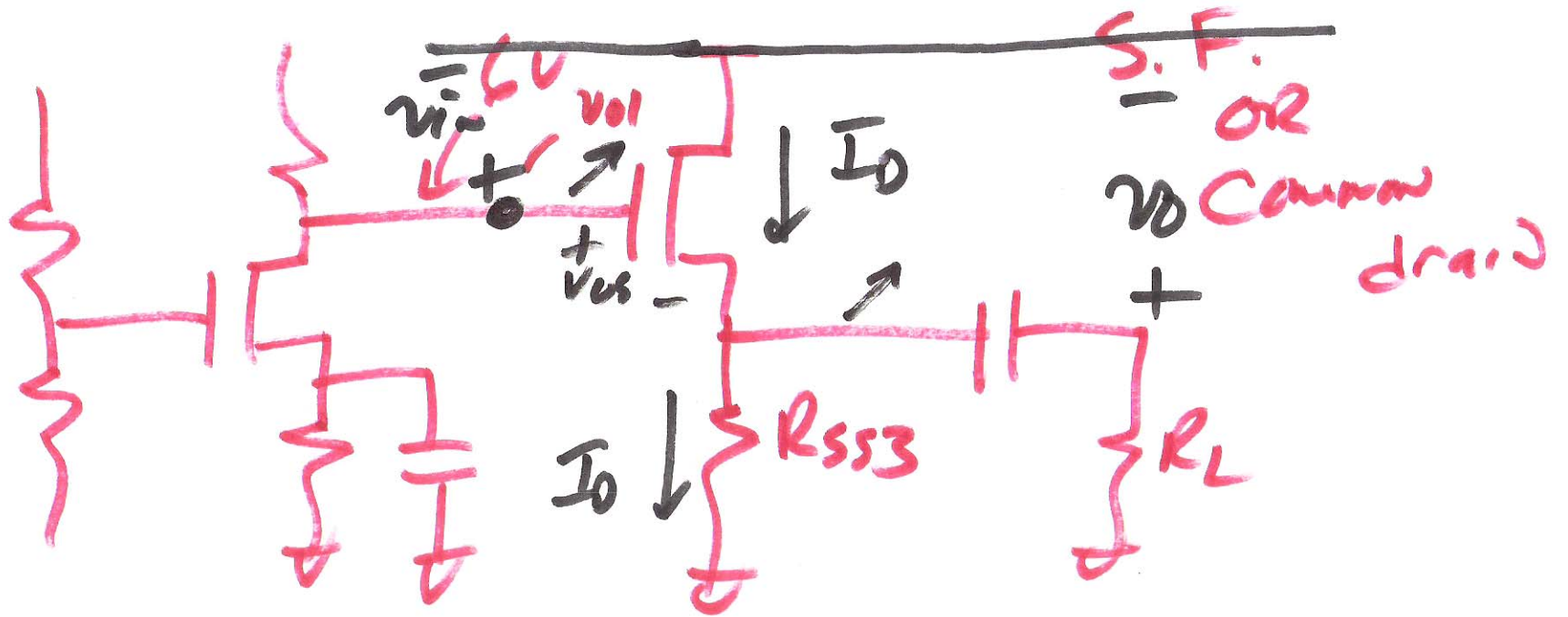

$$V_{gs} = V_{gs} + I_D \cdot R_{SS3}$$

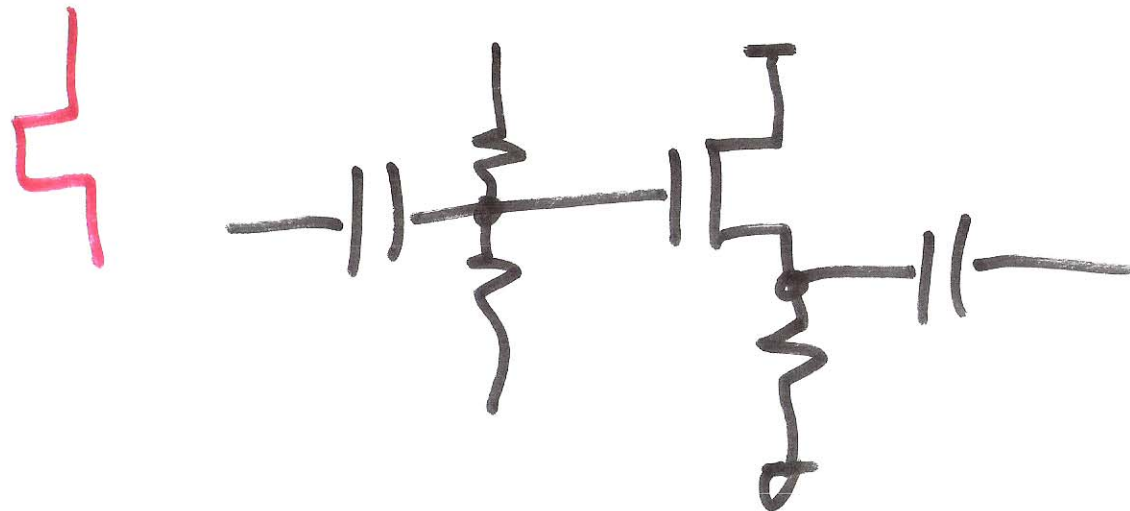

3)


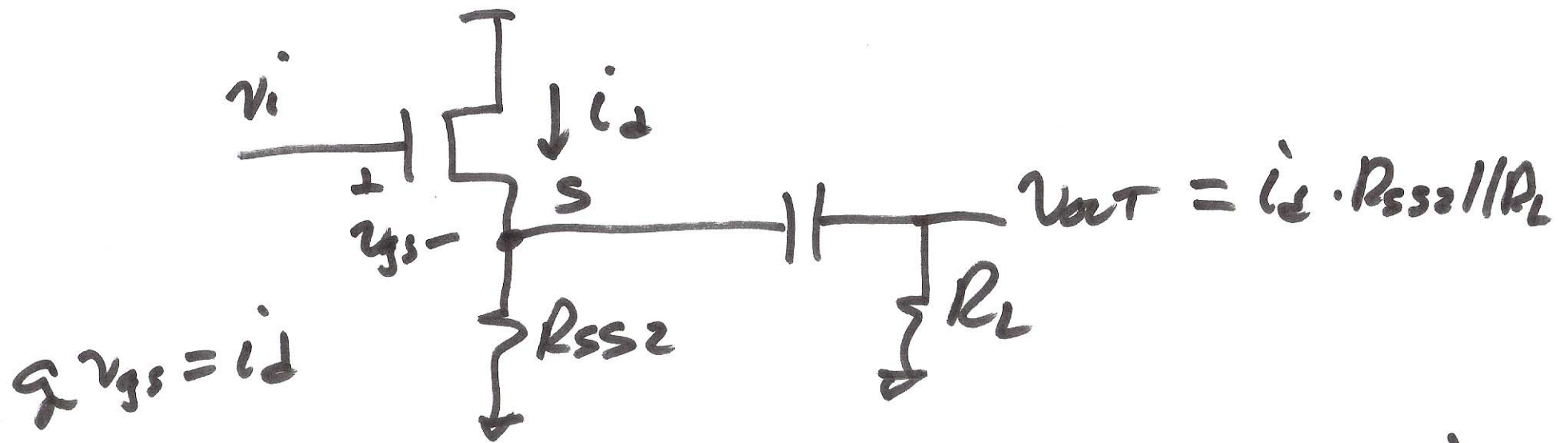


$$\begin{aligned}
 v_i &= v_{GS} + i_d (R_{SS2} \parallel R_L) \\
 &= i_d \left(\frac{1}{g_m} + R_{SS2} \parallel R_L \right) \\
 \frac{v_{OUT}}{v_i} &= \frac{R_{SS2} \parallel R_L}{\frac{1}{g_m} + R_{SS2} \parallel R_L}
 \end{aligned}$$

$$\frac{1}{g_m} \ll R_{SS2} \parallel R_L$$

$$\frac{v_{OUT}}{v_i} \approx 1$$

4)

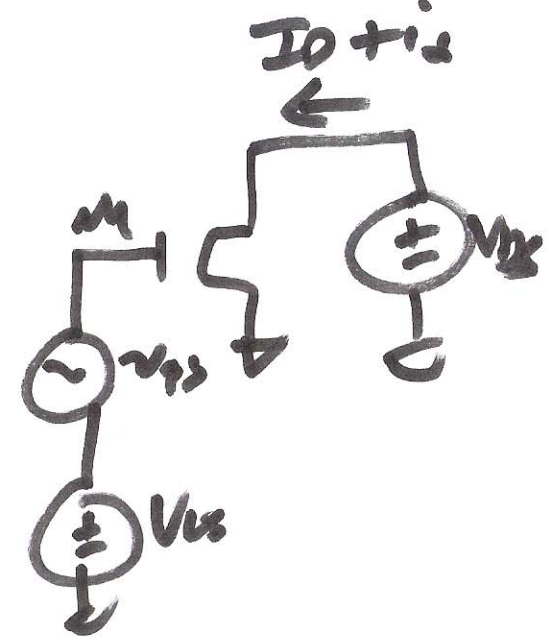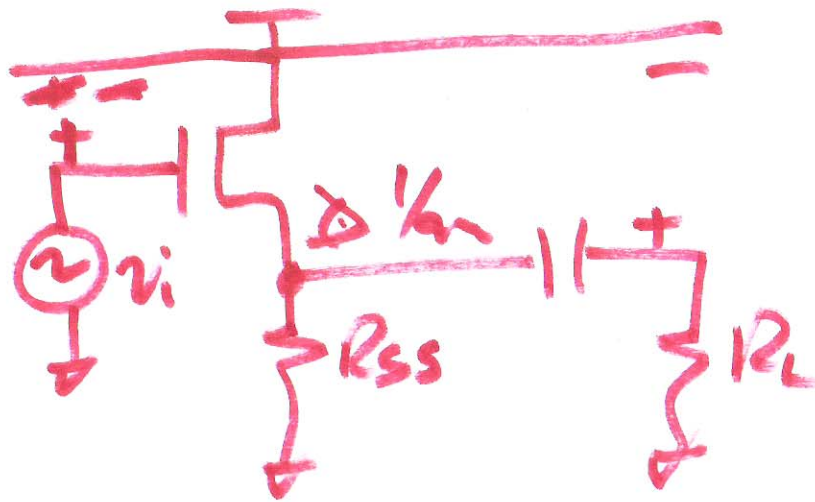


AC ground

$$g(-v_T) = -i_T$$

$$g v_{gs} = i_d$$

$$v_{gs} = -v_T$$

$$i_d = -i_T$$

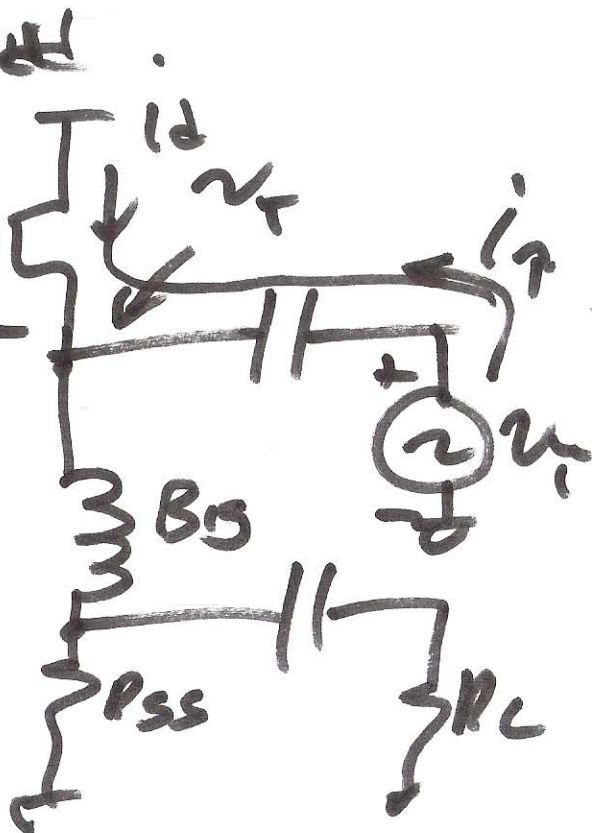


$$I_D + i_d = \frac{k_n W}{L} v_{gs}$$

$$R_{in} = \frac{v_T}{i_T} = \frac{1}{g_m}$$

$$V_{DS} + v_{gs} - v_{TTH}$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

c)

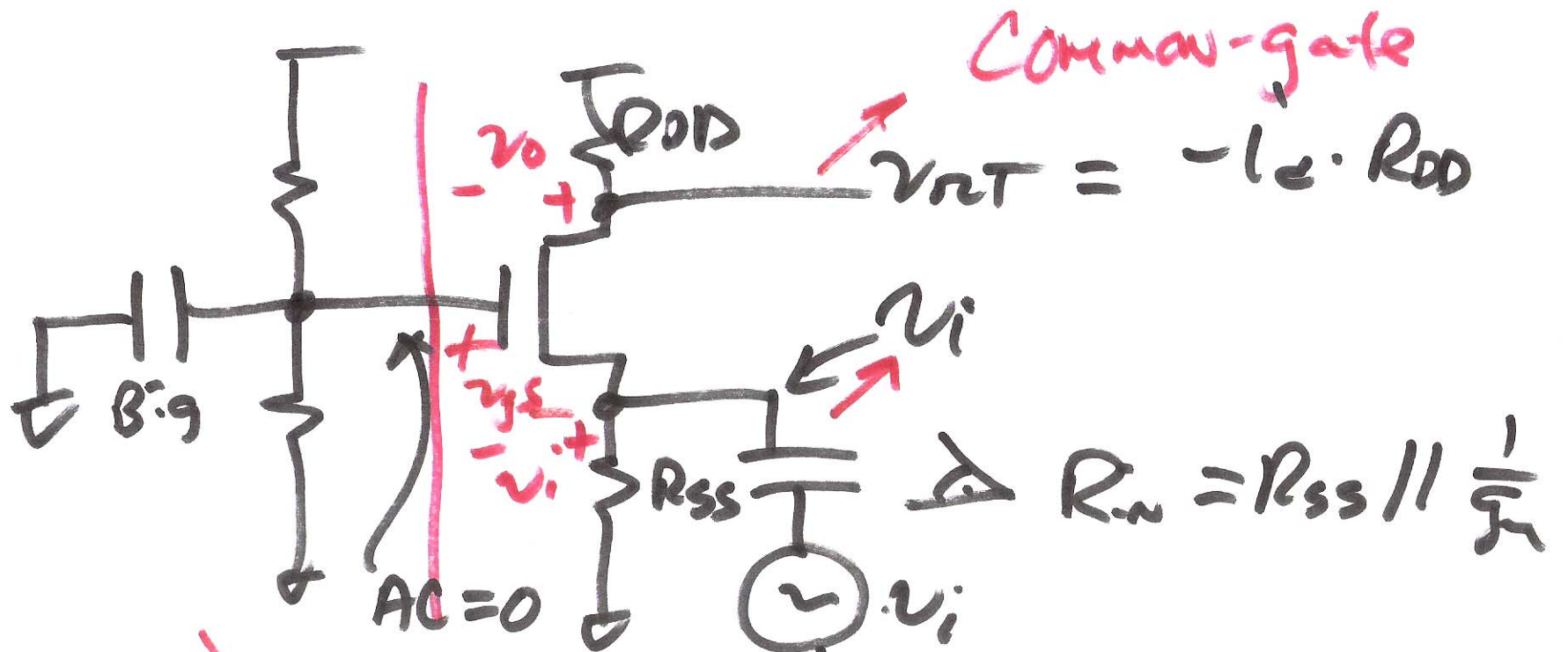


$g_m v_{gs} = i_c$

$v_{gs} = -v_i = \frac{-v_o}{g_m R_{OD}}$

$\frac{v_o}{v_i} = \frac{-i_c \cdot R_{OD}}{-i_c / g_m} = g_m R_{OD}$

$\frac{V}{I} = g_m R_{OD}$

Transimpedance
Resistance

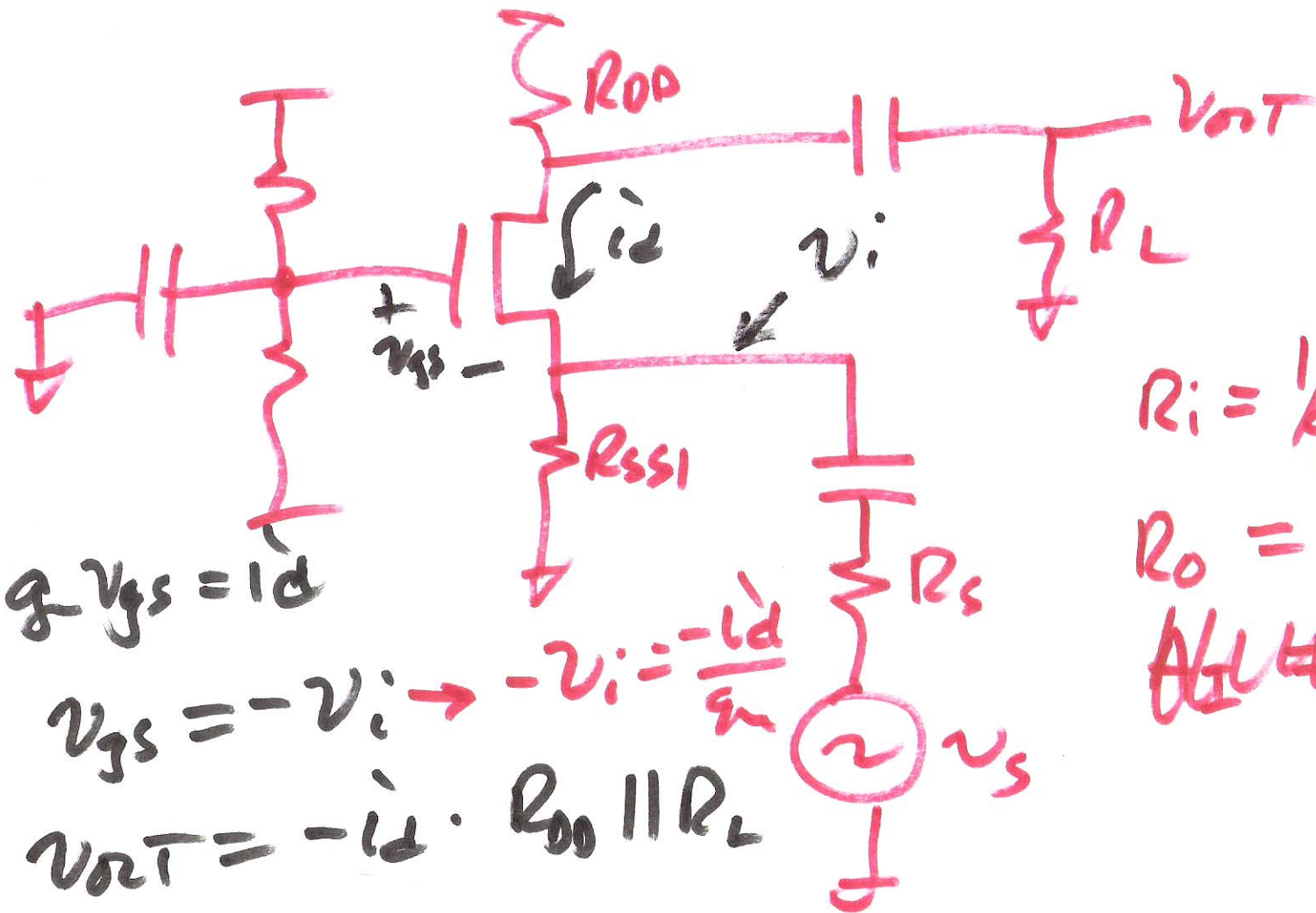

$$g_m v_{gs} = i_d$$

$$v_{gs} = -v_i \rightarrow$$

$$v_{OUT} = -i_d \cdot R_{OD} \parallel R_L$$


$$\frac{v_{OUT}}{v_i} = \frac{-i_d \cdot R_{OD} \parallel R_L}{-i_d \cdot \frac{1}{g_m}} = \frac{R_{OD} \parallel R_L}{\frac{1}{g_m}}$$

$$v_i = v_s \cdot \frac{R_{SS1} \parallel \frac{1}{g_m}}{R_{SS1} \parallel \frac{1}{g_m} + R_S}$$

$$R_i = \frac{1}{g_m} \parallel R_{SS1}$$

$$R_o = R_{OD}$$

ALL

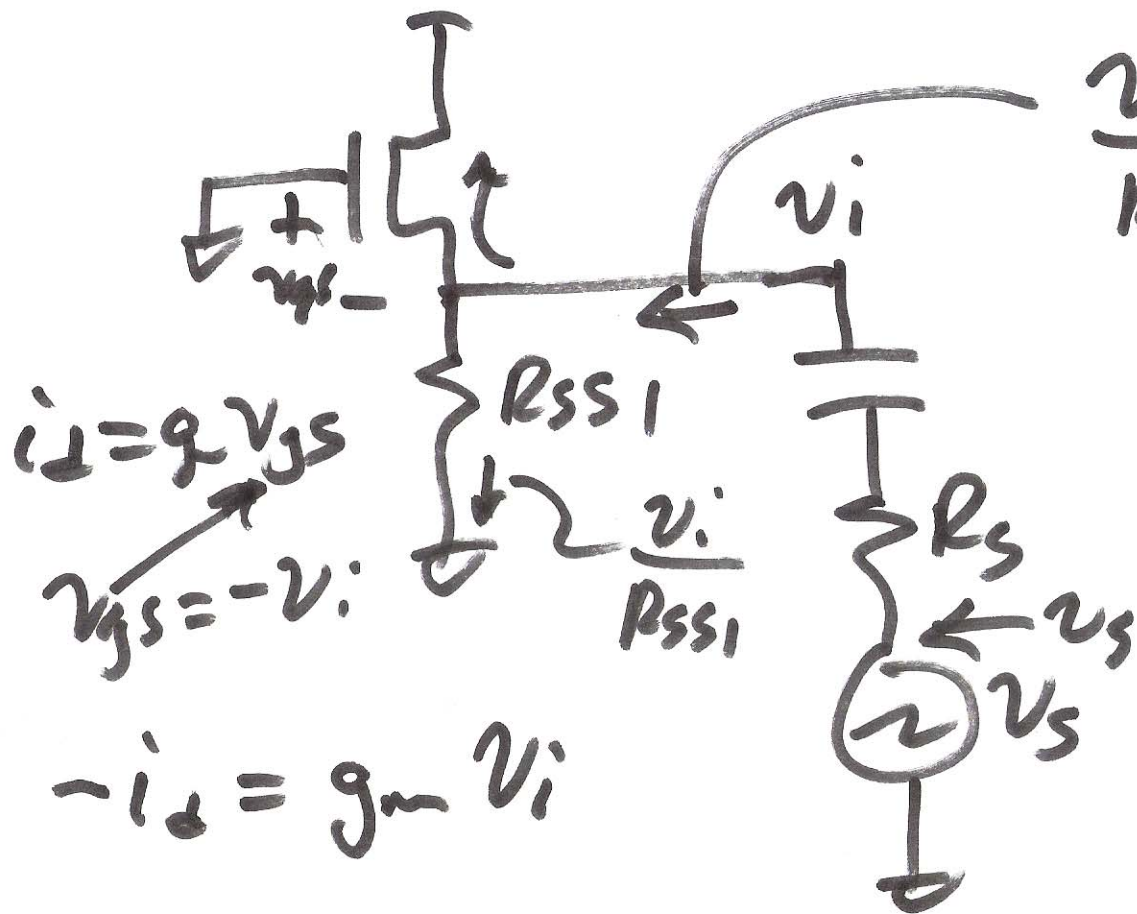

$$\frac{v_i}{R_{ss1}} + (-i_d) = i_{in}$$


$$\frac{v_i}{R_{ss1}} + \frac{v_i}{1/g_m} = i_{in}$$

$$v_i = i_{in} \cdot R_{ss1} \parallel 1/g_m$$

$$i_{in} = \frac{v_s - v_i}{R_s}$$

$$v_i = v_s \cdot \frac{R_{ss1} \parallel 1/g_m}{R_{ss1} \parallel 1/g_m + R_s}$$

9)

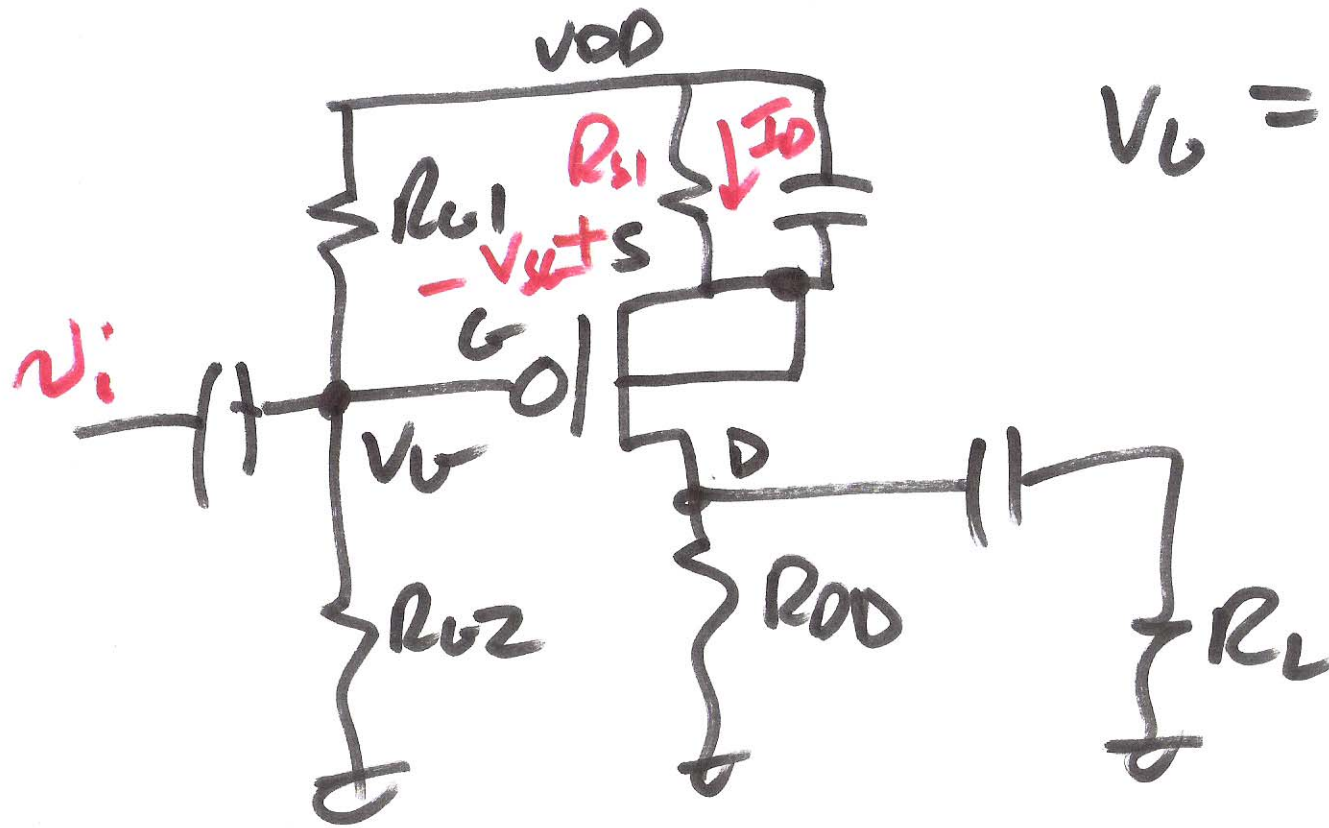


$$V_G = \frac{R_{G2}}{R_{G2} + R_{G1}} \cdot V_{DD}$$

$$V_{DD} - I_0 \cdot R_{S1} - V_{SG} = V_G$$

$$I_0 = \frac{K_p'}{2} \cdot \frac{W}{L} (V_{SG} - V_{THP})^2$$


$$g_m = \sqrt{2 I_0 \cdot K_p' \cdot \frac{W}{L}}$$

10)

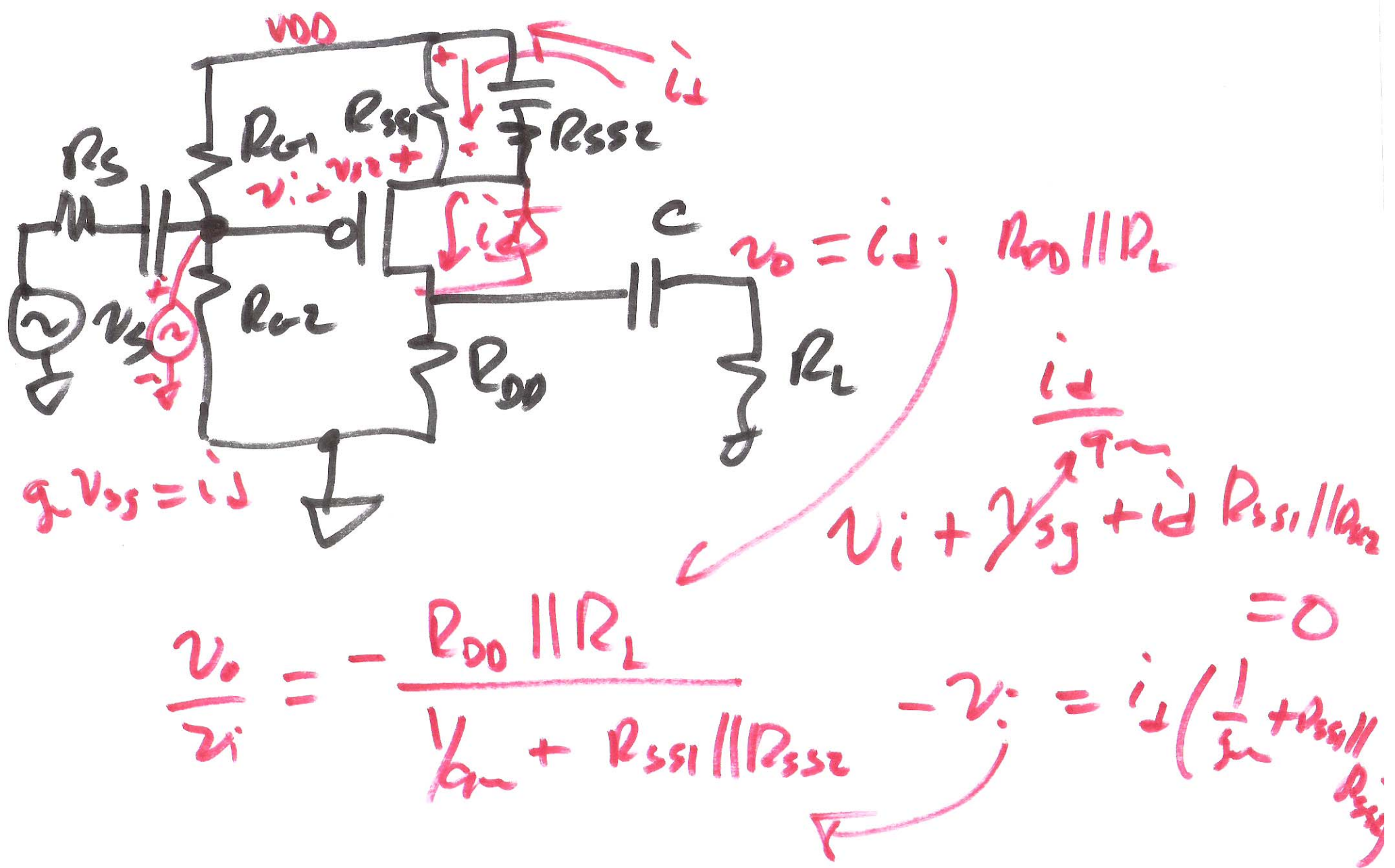

$$\frac{v_o}{v_i} = - \frac{R_{D0} \parallel R_L}{\frac{1}{g_m} + R_{ss1} \parallel R_{ss2}}$$

11)

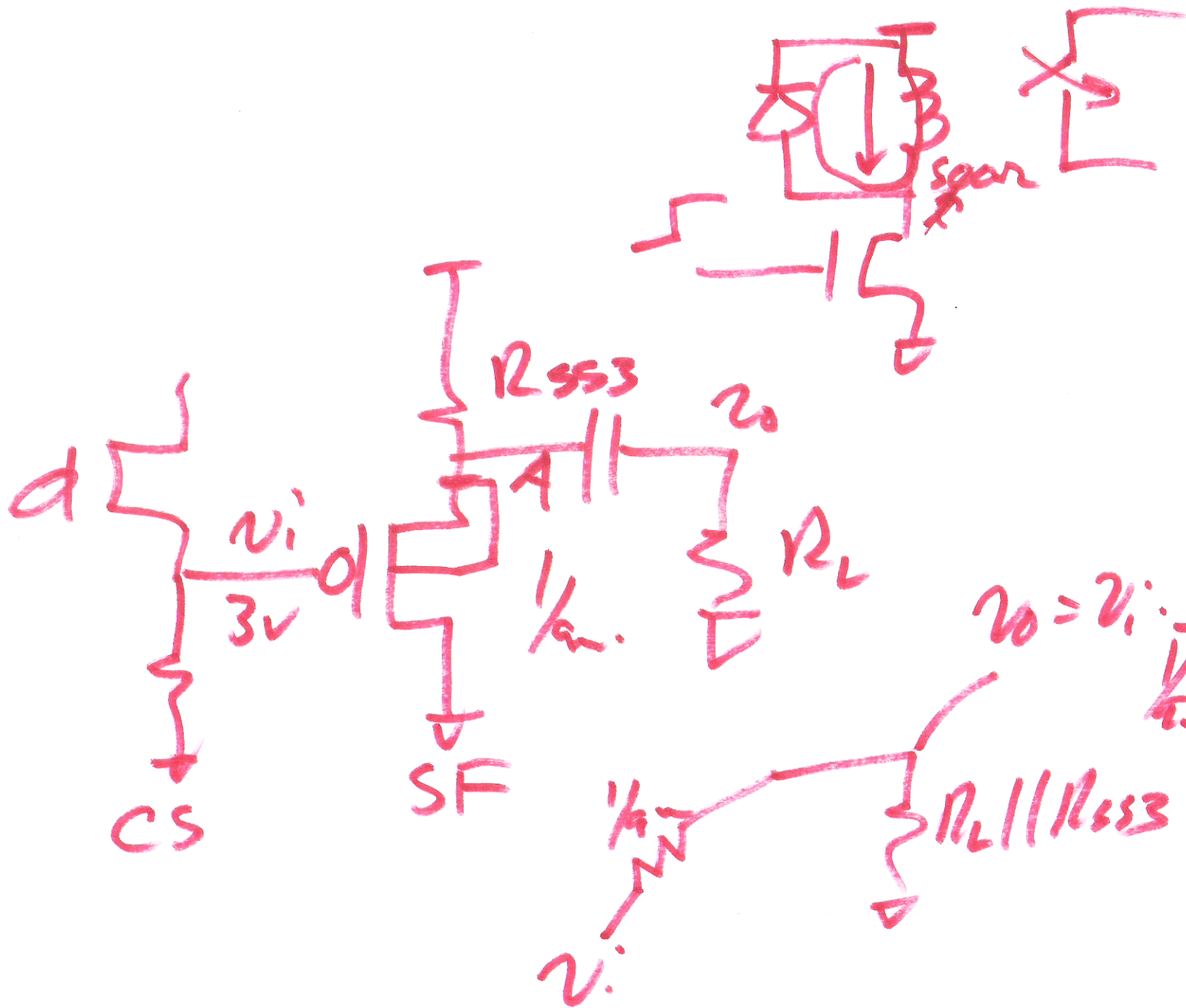

$$v_o = v_i \cdot \frac{R_{eff}}{R_{eff} + R_{ss3}}$$

