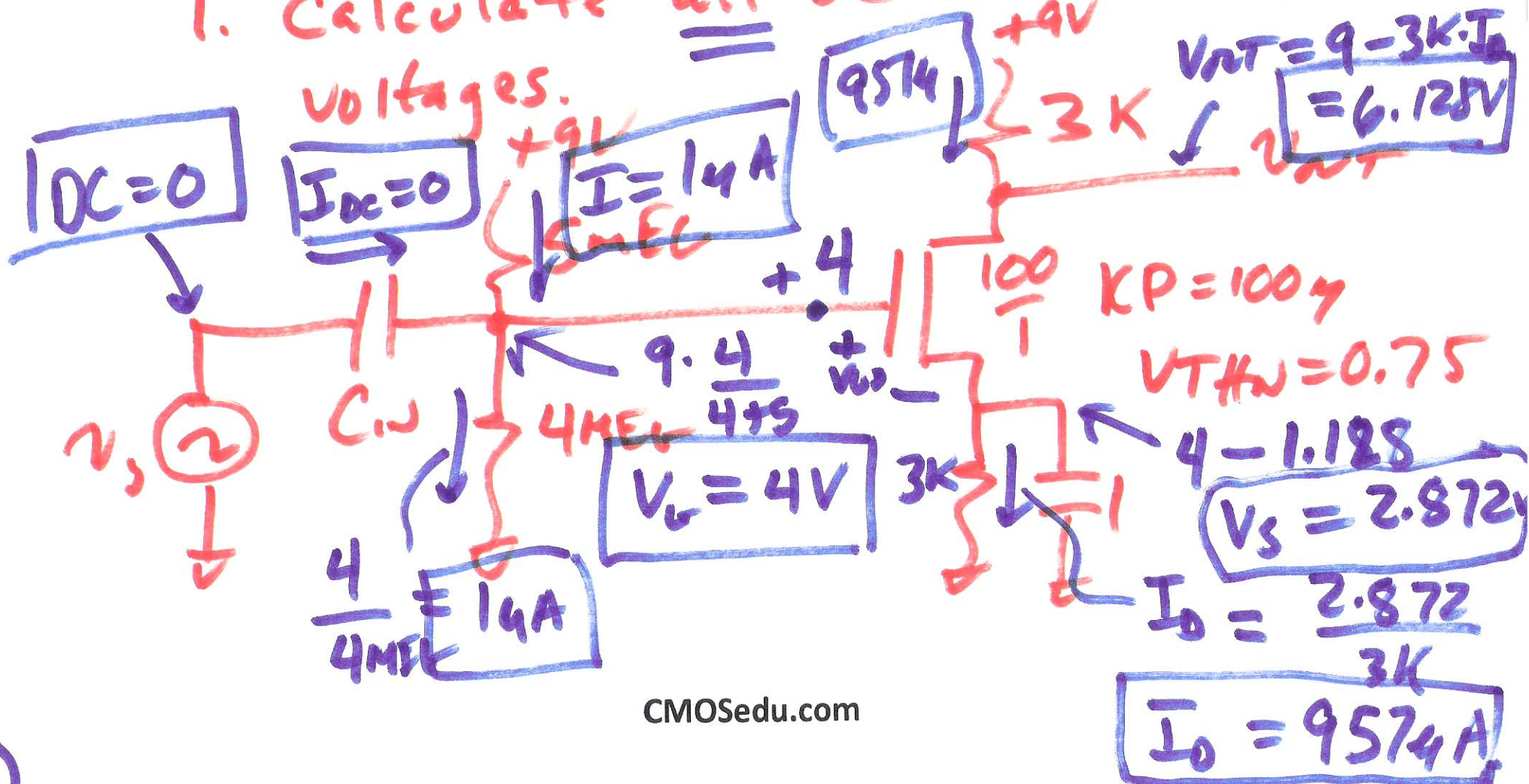


EE 320 Intro. to Electronics

4/24/13 Lecture 23

TEST #1

1. Calculate all DC currents & voltages.



$$V_G = 4 = V_{GS} + I_D \cdot 3k$$

$$I_D = \frac{\mu_n'}{2} \cdot \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$I_D = \frac{100\mu}{2} \cdot \frac{100}{1} (V_{GS} - 0.75)^2$$

$$I_D = 5 \frac{mA}{V^2} (V_{GS} - 0.75)^2$$

$$I_D = 5mA (V_{GS}^2 - 1.5V_{GS} + 5625)$$

$$I_D = 5mA V_{GS}^2 - 7.5mV_{GS} + 2.8125m$$

$$4 = V_{GS} + 3(5V_{GS}^2 - 7.5V_{GS} + 2.8125)$$

$$4 = V_{GS} + 15V_{GS}^2 - 22.5V_{GS} + 8.4375$$

$$0 = 15V_{GS}^2 - 21.5V_{GS} + 4.4375$$

$$V_{GS}^2 - 1.433V_{GS} + 0.2958$$

$$V_{GS} = \frac{1.433 \pm \sqrt{2.053 - 4(0.2958)}}{2}$$


$$V_{GS} = \frac{1.433 \pm 0.9326}{2}$$

$$V_{GS} = \frac{1.433 + 0.9326}{2} = 1.1828V$$

43)

2.) $\frac{v_{in}}{v_s} = ?$ $\frac{v_{out}}{v_{in}} = ?$

$$\frac{v_{in}}{v_s} = 1$$

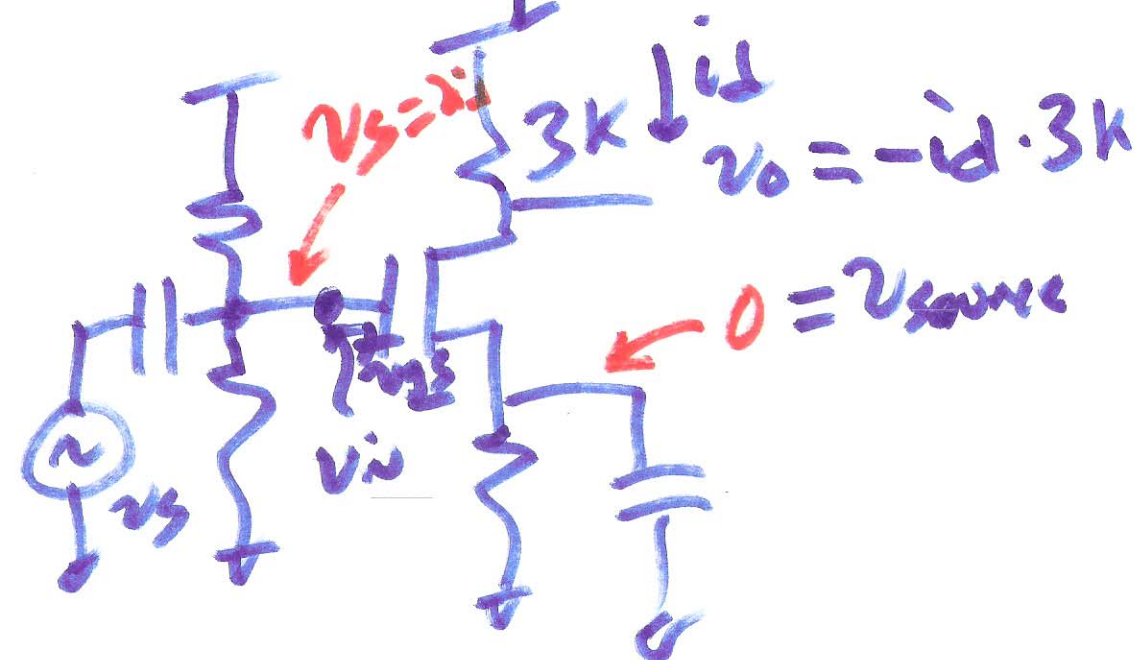

$$g_m = k_n' \cdot \frac{W}{L} (V_{GS} - V_{TH})$$

$$= 100\mu \cdot \frac{100}{1} (1.1825 - 0.75)$$

$$g_m = 4.328 \frac{mA}{V}$$

$$\frac{v_{out}}{v_{in}} = \frac{-i_d \cdot 3k}{i_d / g_m} = -g_m \cdot 3k$$

$$\frac{v_{out}}{v_{in}} = -4.328 \cdot 3$$

$$\frac{v_{out}}{v_{in}} = -12.98$$

$$i_d = g_m \cdot v_{gs}$$

$$i_d = v_{gs} \cdot g_m$$

$$i_d = g_m \cdot v_{in}$$

$$i_d = g_m v_s$$

4)

3.) Calculate All DC currents & voltages



5)

$$9 - \frac{133}{66.5} (V_{SG}^2 - 7V_{SG} + 12.25) - V_{SG} - 2.5 = 0$$

$$9 - 66.5 V_{SG}^2 + 465.5 V_{SG} - 814.625 - V_{SG} - 2.5 = 0$$


$$-66.5 V_{SG}^2 + 464.5 V_{SG} - 808.125 = 0$$

$$V_{SG}^2 - 6.985 V_{SG} + 12.15 = 0$$

$$V_{SG} = \frac{6.985 \pm \sqrt{48.79 - 4(12.15)}}{2}$$

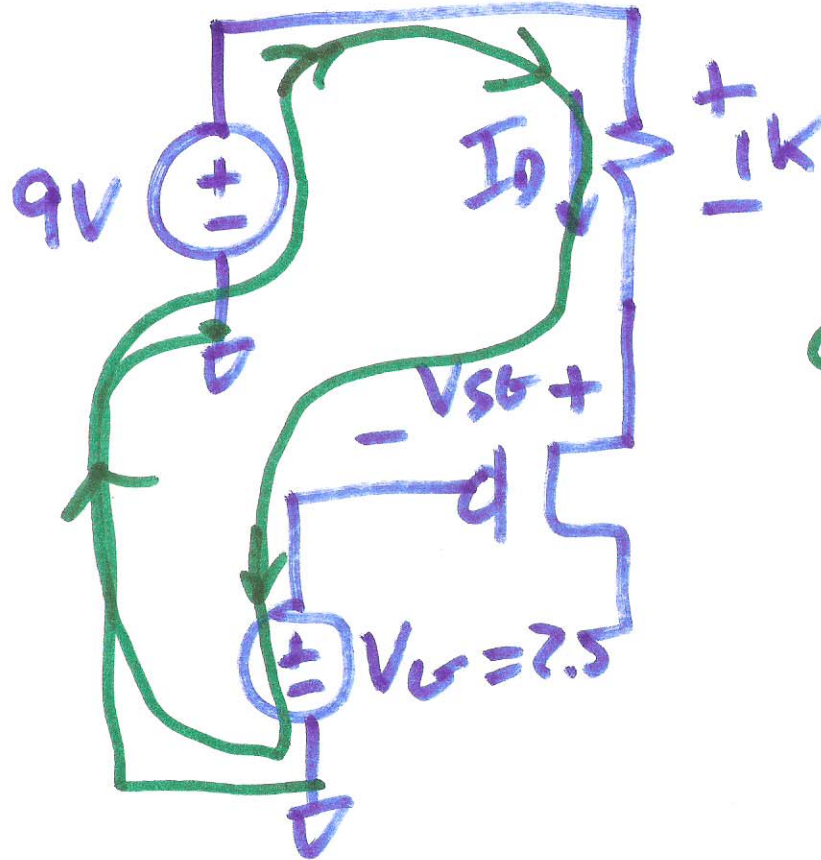48.6

$$3.71V = V_{SG} = \frac{6.985 \pm .435}{2}$$



$$9 - I_D 1k - V_{SG} - 2.5 = 0$$

6)

$$I_0 = \frac{9 - 6.21}{1k} = \underline{\underline{2.79mA}}$$


4) Calculate v_{out}/v_i

$$v_{in} + v_{sg} = 0$$

$$v_{in} = -v_{sg}$$

$$g_m = 0.133 (3.71 - 3.5)$$

$$g_m = 27.9 \mu A/V$$

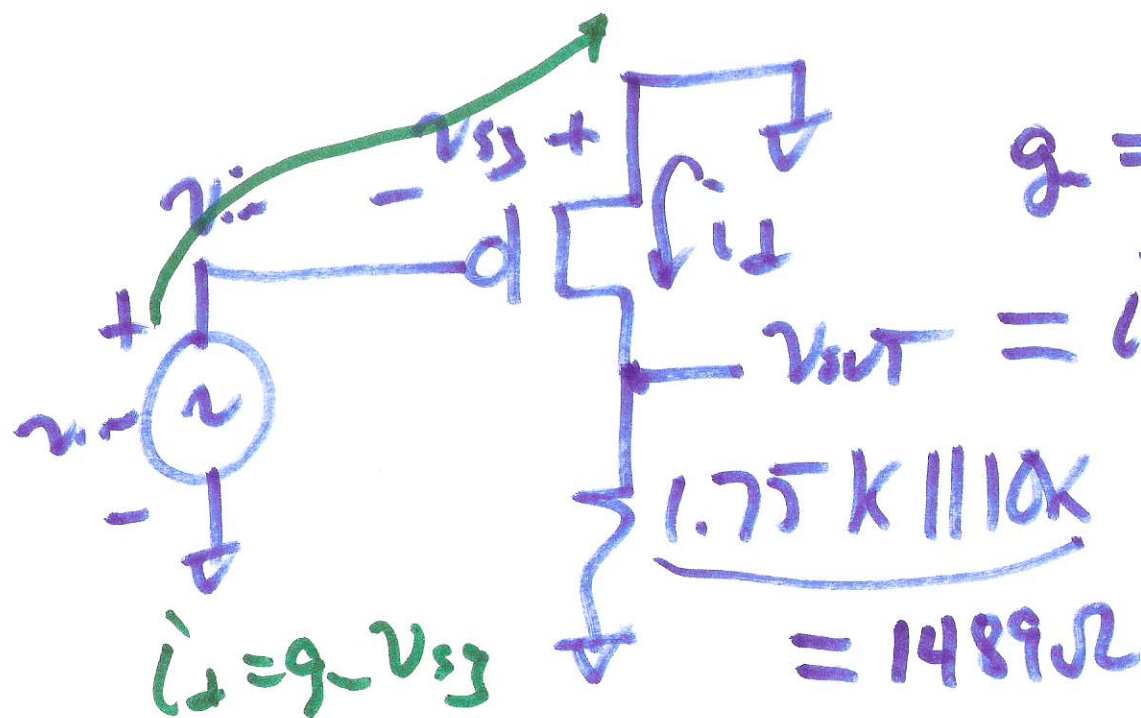

$$v_{out} = i_d \cdot 1489$$


$$\frac{v_o}{v_i} = \frac{i_d \cdot 1489}{-i_d / 27.9 \mu A}$$

$$\frac{v_o}{v_i} = 1.489 \cdot 27.9$$

$$\underline{\underline{-41.54V}}$$

7)

5) Calculate v_{out}/v_{in}

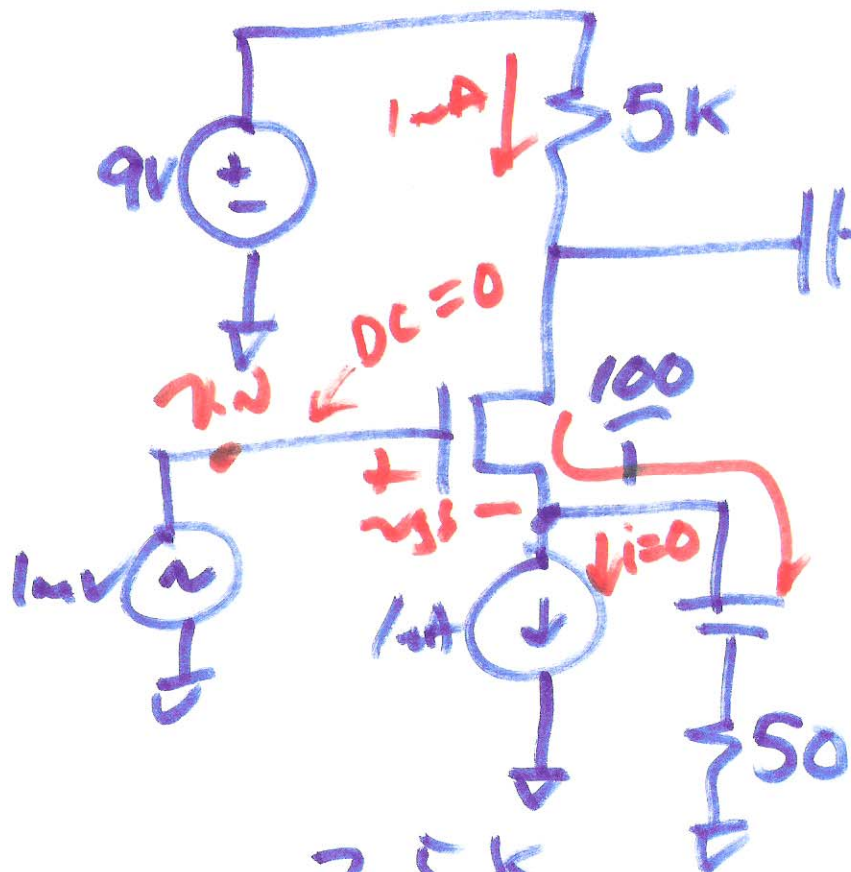

$$g_m = \sqrt{2 \cdot 1 \mu A \cdot 100 \mu \cdot \frac{100}{1}}$$

$$= \sqrt{2 \cdot I_0 \cdot K_p' \cdot \frac{W}{L}}$$

$$= \sqrt{2 \cdot 10^{-6} \cdot 100 \mu \cdot \frac{100}{1}}$$

$$g_m = 4.47 \text{ mA/V}$$

$$V_{TH} = 0.75$$

$$K_P = 100 \mu$$

$$\frac{v_o}{v_{in}} = \frac{-\cancel{g_m} \cdot 5k \parallel 5k}{\cancel{g_m} \cdot 5k + \cancel{g_m} \cdot 50}$$


$$\frac{v_o}{v_{in}} = \frac{-2.5k}{\frac{1}{4.47 \text{ mA/V}} + 50}$$

$$= \frac{-2.5k}{224 + 50}$$

$$= -9.12 \frac{V}{V}$$

CMOSedu.com

8)

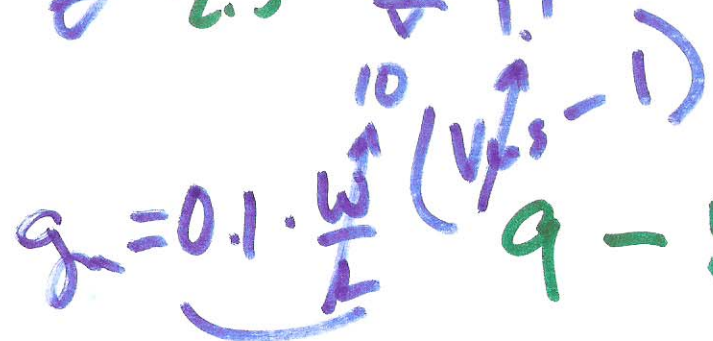

$$V_{SG} = 1.1V$$

$$9 - 500V_{SG}^2 + 1000V_{SG} - 500 - V_{SG} - 2.5 = 0$$

$$-500V_{16}^2 + 999V_{16} - 493.5 = 0$$

$$V_{SG}^2 - 1.998V_{SG} + 0.987 = 0$$

$$V_{SG} = \frac{1.998 \pm \sqrt{3.992 - 3.948}}{2}$$

$$9 - 1k \cdot I_D - V_{SG} - 2.5 = 0$$


$$I_D = \frac{0.1}{2} \cdot \frac{10}{1} (V_{SG} - 1)^2$$

$$= 0.5 (V_{SG}^2 - 2V_{SG} + 1)$$

$$I_D = 0.5 V_{SG}^2 - V_{st} \pm \frac{1}{2}$$

9)

$$v_{sg} \cdot g = i_d$$

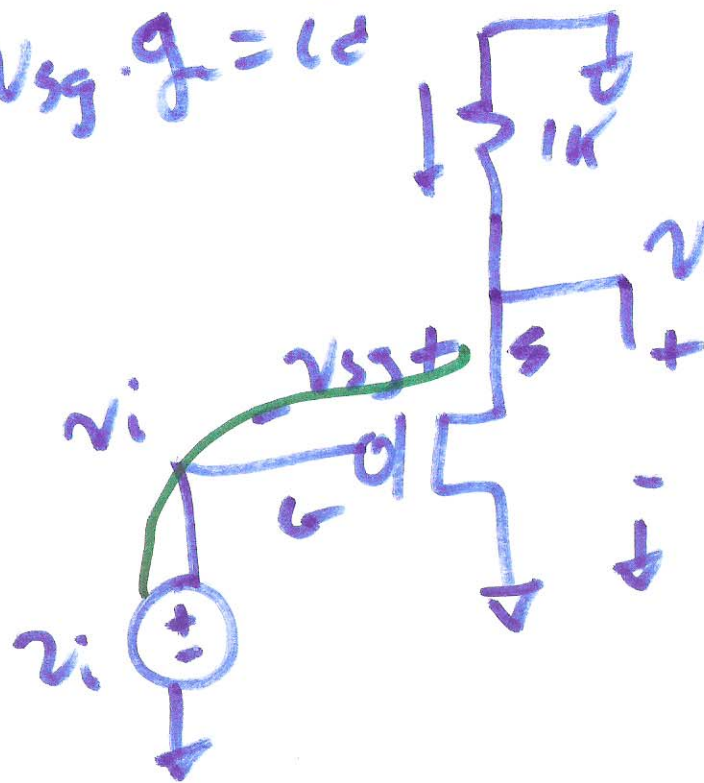

$$v_{dT} = -i_d \cdot 1k$$


$$v_i + v_{sg} = v_{dT}$$

$$\frac{v_{dT}}{v_i} = \frac{-i_d \cdot 1k}{-i_d \left(\frac{1}{g} + 1k \right)}$$

$$= \frac{1k}{\frac{1}{.1} + 1k}$$

$$= \frac{1k}{1.01k} = .99V$$

7)

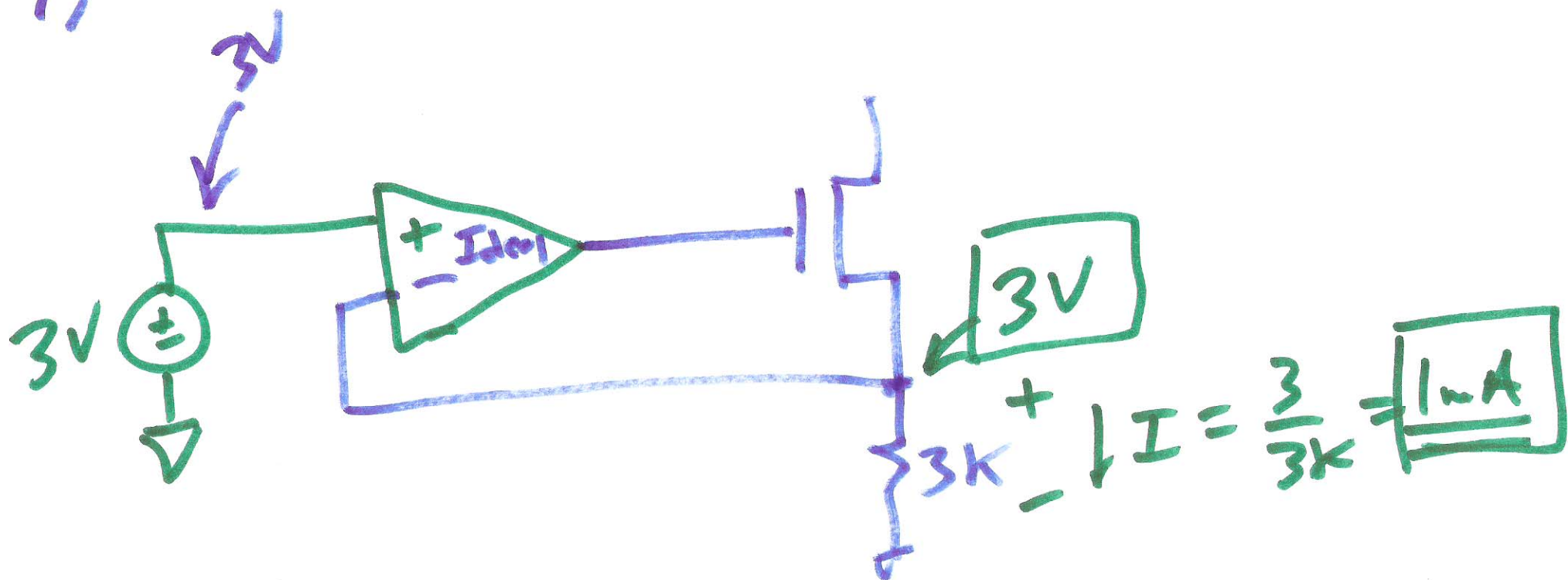

11)