

EE 320 Intro to Electronics

5/1/13

Lecture 25

logic MOSFET
great

Analog lower g_m
But high
input $R \leftarrow$ good

* Digital *

COST $\uparrow$



CMOS $\rightarrow$ Complementary MOS
p - AND n

BJT
good - doesn't scale
well
also has stored
charge
high g_m
low input R - not
good

* Analog *

BiCMOS

BJT's
CMOS

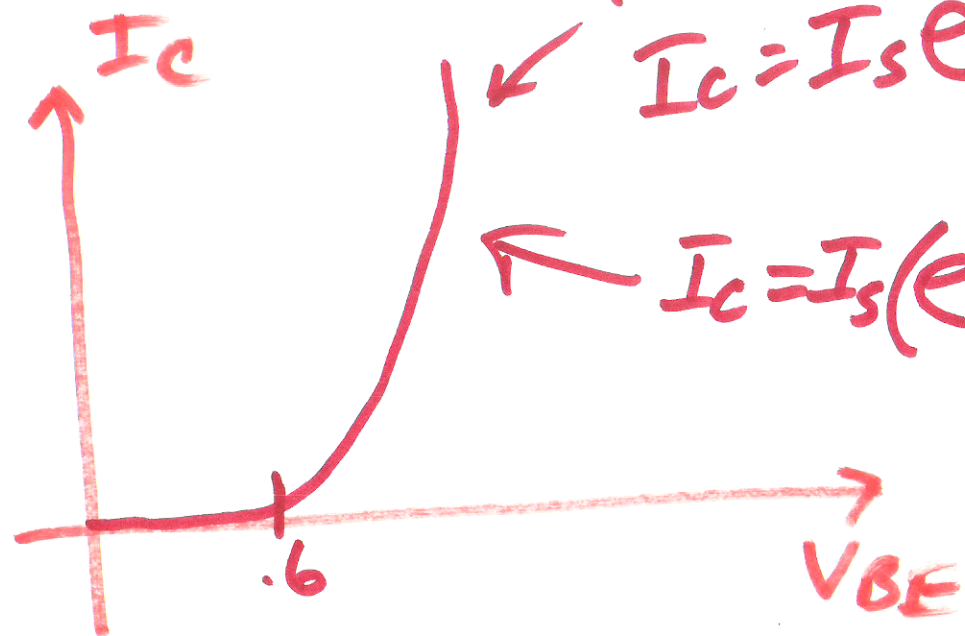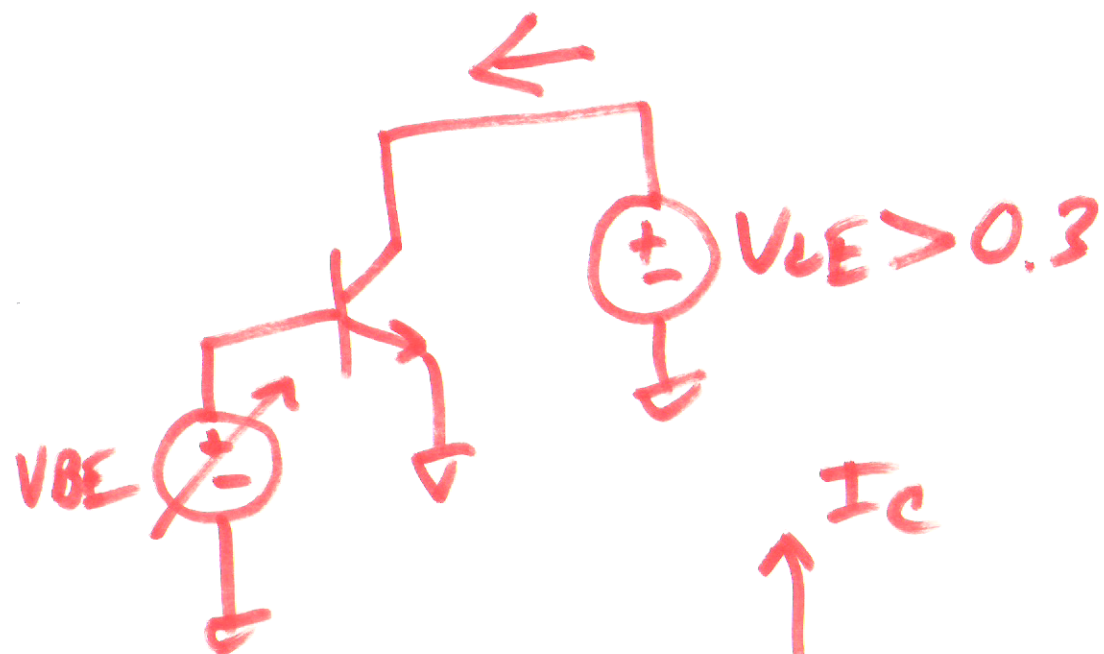

turned on V_{BE}/V_T

$$I_C = I_S e^{V_{BE}/V_T}$$



$$I_C = I_S (e^{V_{BE}/V_T} - 1)$$

$$V_T = \frac{kT}{q}$$

$$= 25 \text{ mV @ room temp}$$

derive g_m
 $\leftarrow I_c + i_c$

$$i_c = g_m v_{be}$$

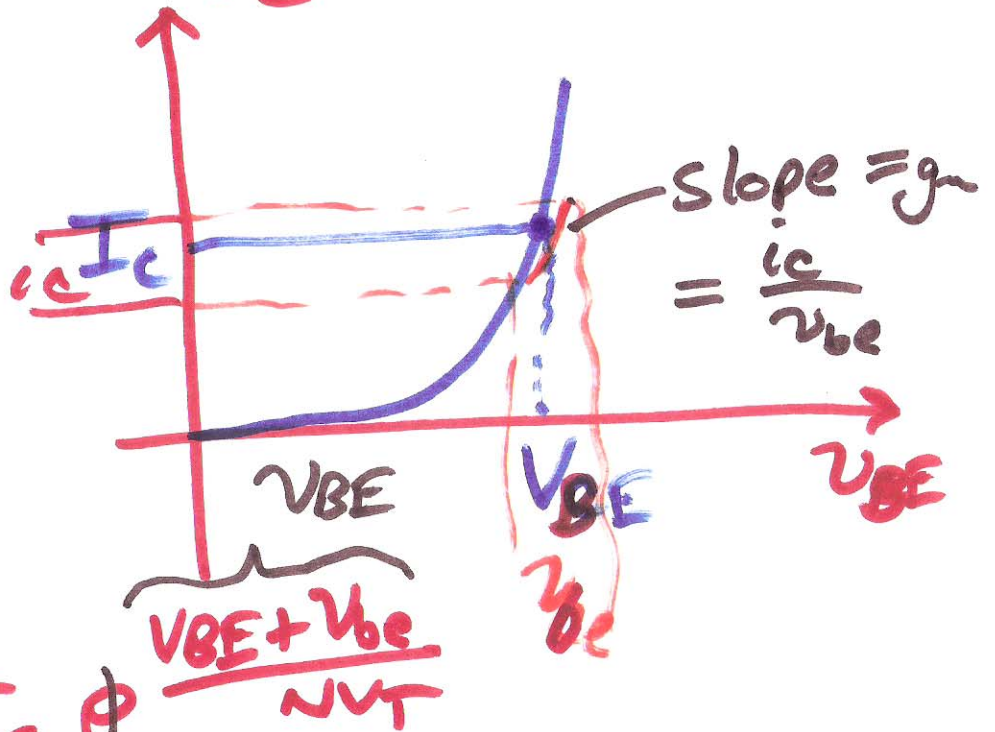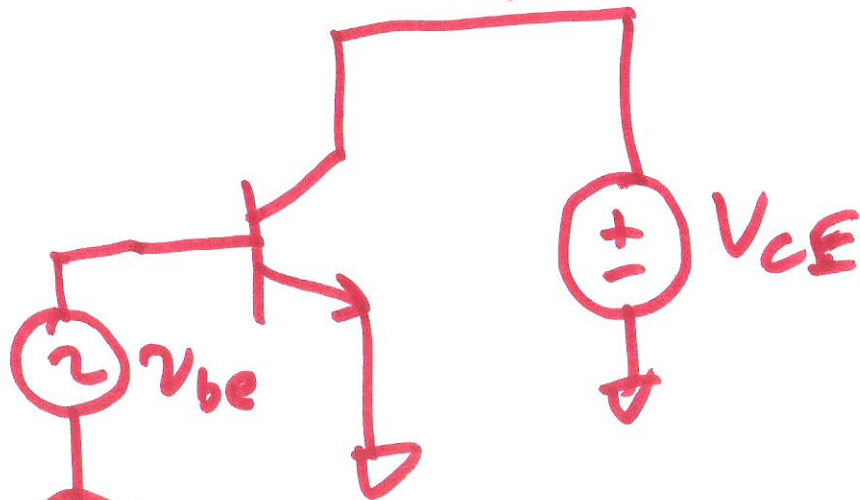

$$g_m = \frac{\delta i_c}{\delta v_{BE}} = \frac{\delta i_c + I_c}{\delta v_{BE}} = \frac{\delta I_s e^{\frac{V_{BE} + v_{be}}{NVT}}}{\delta v_{BE}} \bigg|_{\substack{I_c = \text{CONST} \\ V_{BE} = \text{CONST}}}$$

$$\left. \frac{\delta i_c}{\delta V_{BE}} \right|_{\substack{I_C = \text{CONST} \\ V_{BE} = \text{CONST}}} = \frac{\delta}{\delta V_{BE}} I_s e^{V_{BE}/N V_T}$$

$$= \frac{I_s}{N V_T} e^{V_{BE}/N V_T} \frac{\delta V_{BE}}{\delta V_{BE}}$$


$$= \frac{i_c}{N V_T} \approx \frac{I_C}{N V_T}$$

$i_c \ll I_C$

↑ AC ↑ DC

$$g_m = \frac{I_C}{N V_T}$$

final exam
😊

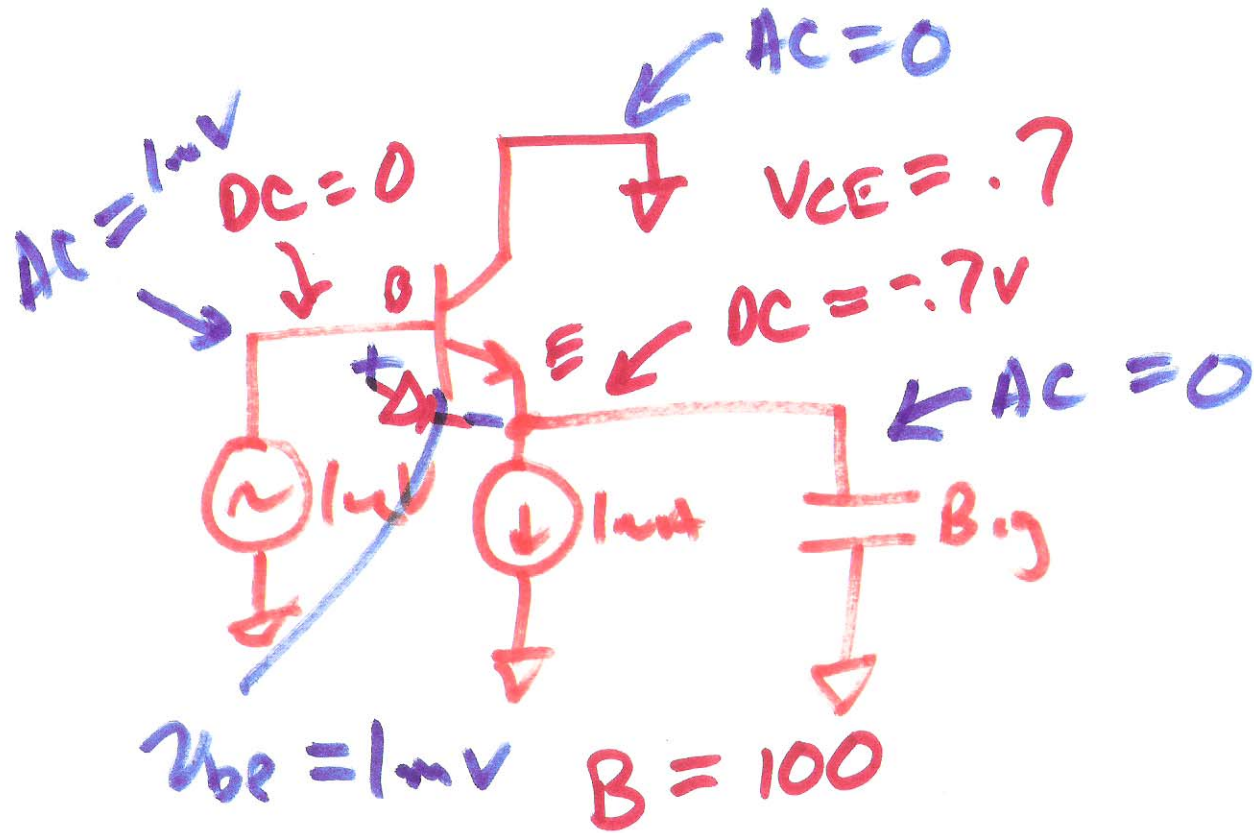

$$g_m = \frac{I_C}{V_T} = \frac{1mA}{25mV} = 40 \frac{mA}{V}$$


$$i_c = g_m v_{be} = g_m \cdot 1mV = 40 \mu A$$

1.04mA

1mA

96mA

$$i_c = 40 \mu A$$

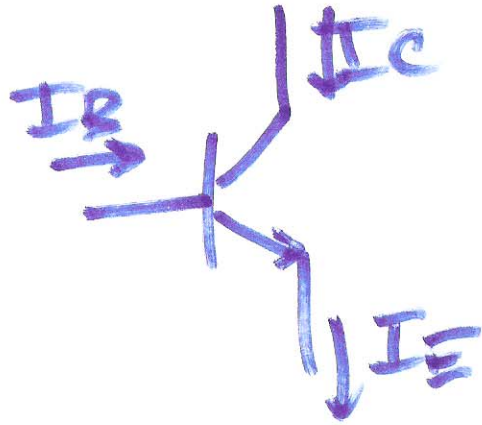

$$\alpha I_E = I_C$$

$$I_C + I_B = I_E$$

$$\alpha I_C + \alpha I_B = I_C$$

$$\frac{\alpha}{1-\alpha} \cdot I_B = I_C$$


$$\beta \cdot I_B = I_C$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$100 - 100\alpha = \alpha$$

$$\alpha = \frac{100}{101} = .99$$

b)

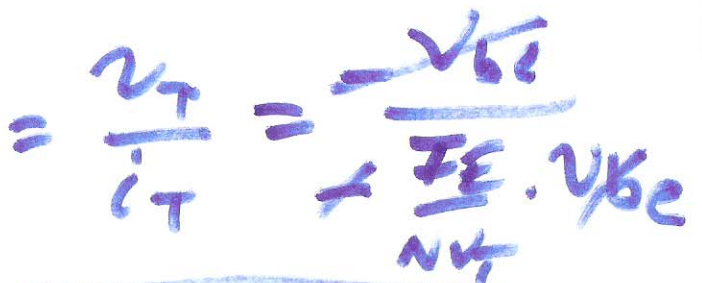

$$g_m = \frac{I_c}{V_T}$$

$$i_c = g_-(-v_T) = g_-v_{be}$$

$$\alpha i_e = q v_{be} \rightarrow i_e = -i_r = \frac{q}{\alpha} \cdot v_{be}$$

$$V_{be} \frac{I_E}{n V_T} \ll \frac{I_C}{\alpha \cdot n V_T} \cdot V_{be}$$



$$r_e = \frac{NVT}{I_E} = \frac{25mV}{1mA} = 25\Omega$$

$$101 \cdot 25\Omega = 2525$$


$$r_e \approx \frac{1}{g_m} = \frac{NVT}{I_C}$$

$$r_{be} = \frac{NVT}{I_B}$$

$$= (\beta + 1) \cdot r_e$$

$$I_B \cdot \beta = I_C \quad I_B \cdot \beta + I_B$$

$$I_B(\beta + 1) = I_E = I_C + I_B$$

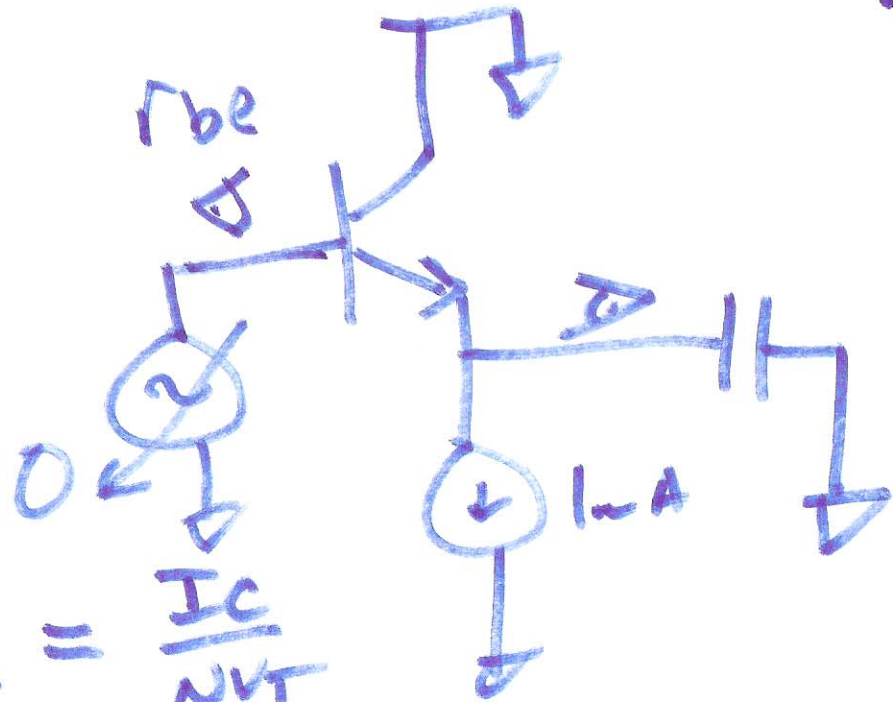


$$g_m = \frac{I_C}{NVT}$$

$$r_e = \frac{NVT}{I_E}$$

$$r_{be} = \frac{NVT}{I_B}$$

8)

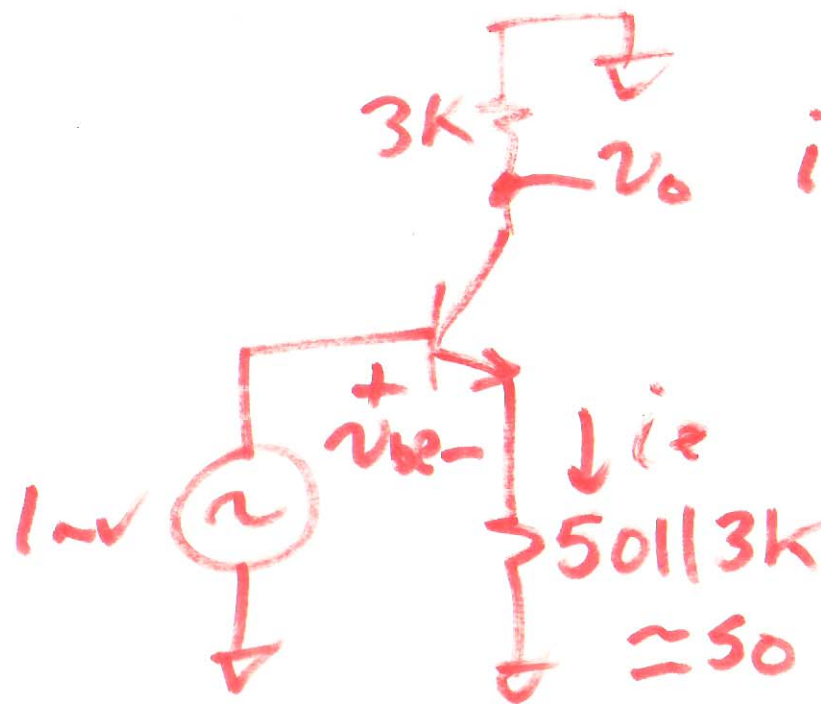

$$i_c = g_m v_{be}$$

$$v_o = -i_c \cdot 3k$$

$$v_i = v_{be} + i_e \cdot 50$$

$$\frac{i_c}{g_m}$$

$$\frac{v_o}{v_i} = \frac{-3k}{\frac{1}{g_m} + 50} = \frac{-3k}{75} \approx \underline{\underline{40}}$$

$$r_o \approx$$

$$g_m = 40 \frac{A}{V}$$

$$\frac{1}{g_m} = 25 \Omega$$

CE Amp

9)