

Transistor
= transfer
resistance

Lecture 26

$$[(\beta+1)r_e]^{-1} = r_{be}^{-1} = \frac{I_B}{NVT} \quad r_e^{-1} = \frac{I_E}{NVT}$$

$$g = \frac{I_C}{NVT}$$

$$I_C + I_B =$$


$$I_E$$

$$I_E \alpha = I_C$$



$$I_C = \beta \cdot I_B$$

current gain

$$I_B(\beta+1) = I_E$$

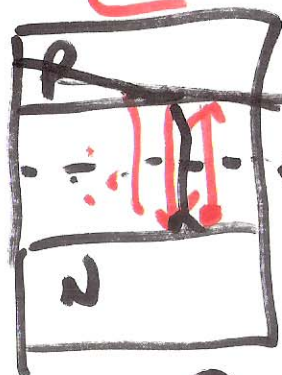

metallurgical junction

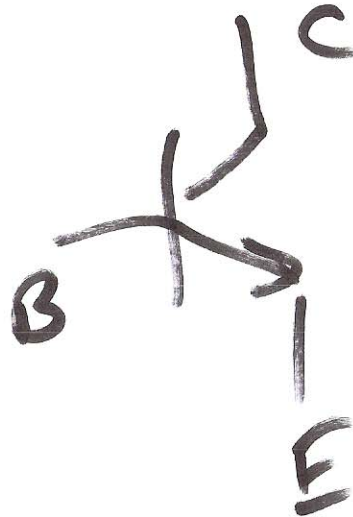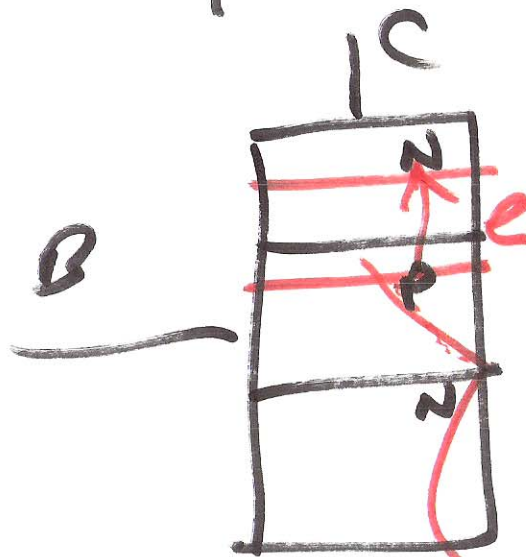


$$\beta = 100$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{100}{101} = .99$$

test
pnp-equiv.

$$V_B = 0$$

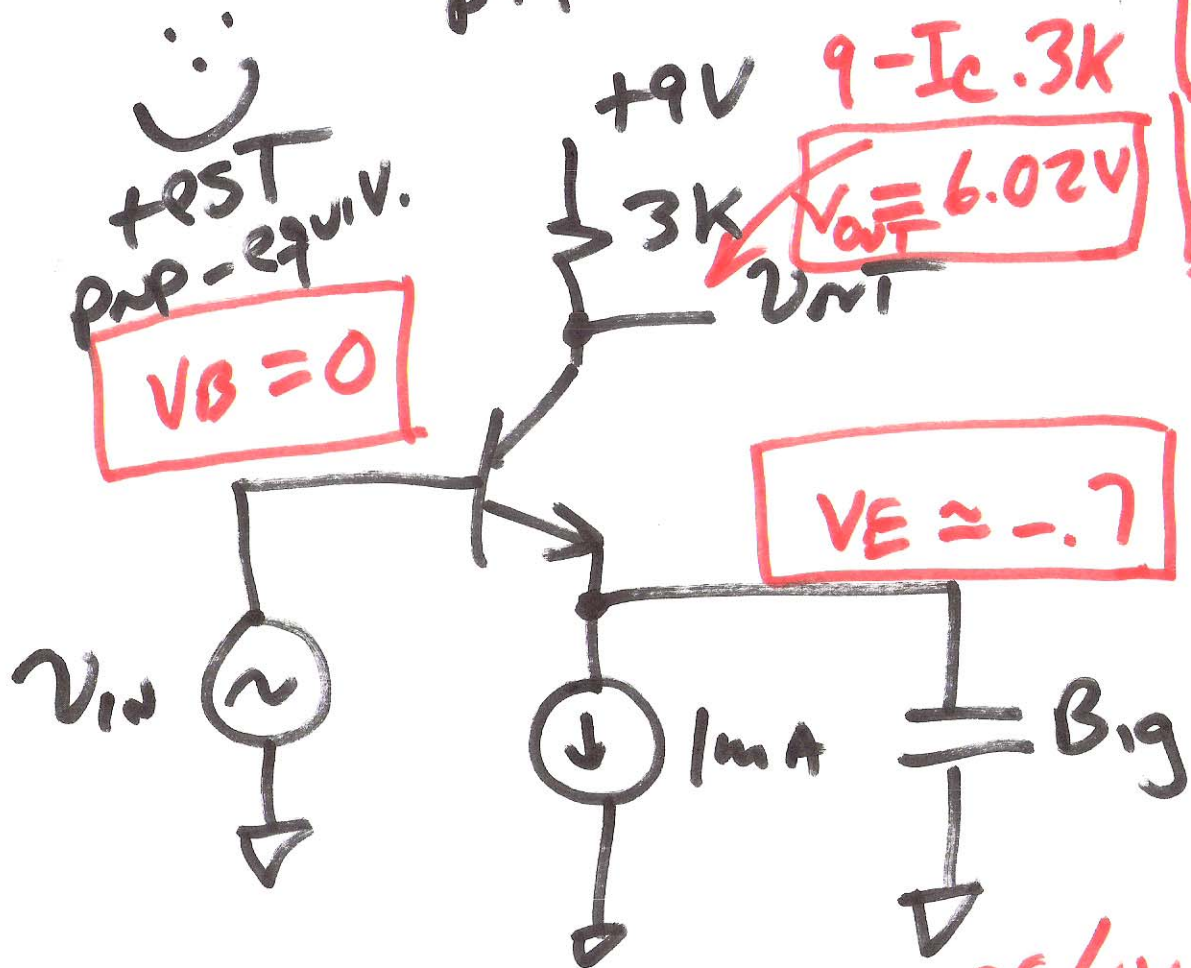

$$9 - I_C \cdot 3k$$

$$V_{out} = 6.02V$$

$$I_E = 1mA$$

$$I_C = 990\mu A$$

$$I_C = \alpha I_E$$

$$I_B = \frac{I_C}{\beta}$$


$$I_B = 9.9\mu A \approx 10\mu A$$

$$I_B = \frac{I_E}{\beta + 1}$$

$$I_C = I_S e^{\frac{V_{BE}}{NVT}}$$

$$V_{BE} = NVT \ln \frac{I_C}{I_S}$$

2)

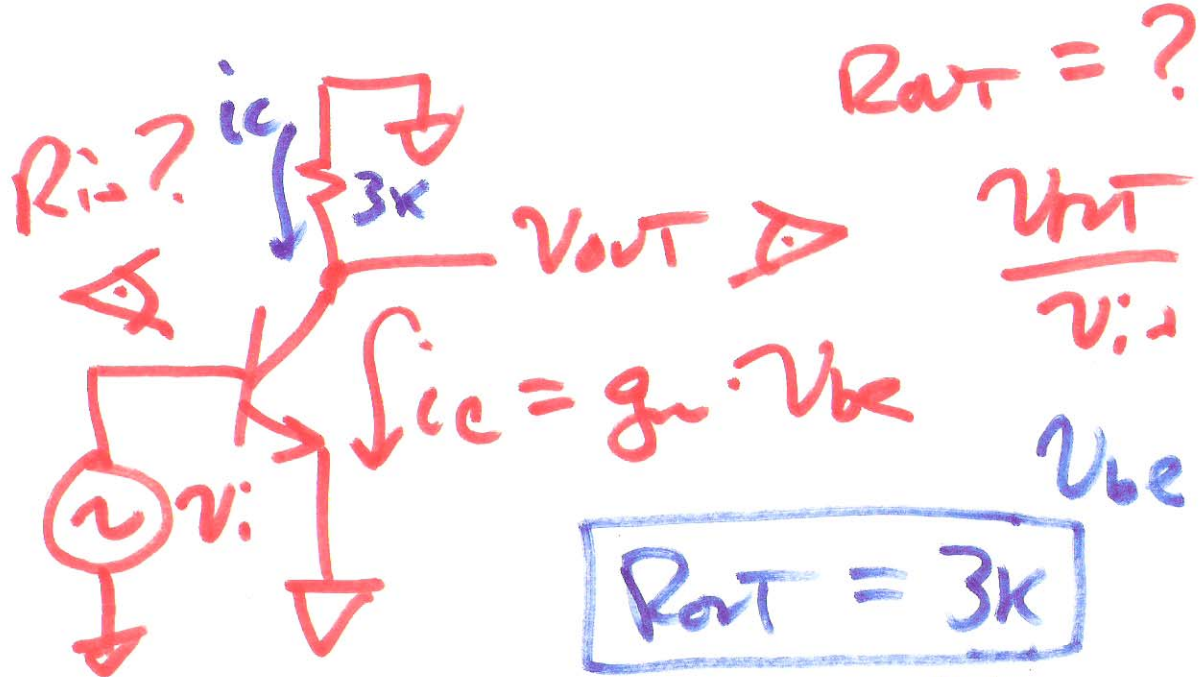

$$\frac{v_{out}}{v_i} = \frac{-i_c \cdot 3k}{v_{be}} \quad R_{in} = \frac{NVT}{I_B \cdot 25}$$

$$= \frac{-i_c \cdot 3k}{i_c / g_m} \quad R_{in} = 2.5k\Omega$$

$$= \frac{-3k}{1/g_m} = -g_m \cdot 3k = -40 \cdot 3 = -120 \frac{V}{V}$$

CMOSedu.com

ΔV

ΔI

$\Delta V = 0$

$\frac{\Delta V}{\Delta I} = \infty$

ΔV

ΔI


$\Delta V = 0$

$\frac{\Delta V}{\Delta I} = 0$

$g_m = \frac{1mA}{25mV} = 40 \frac{mA}{V}$

$-120 \frac{V}{V}$

3)

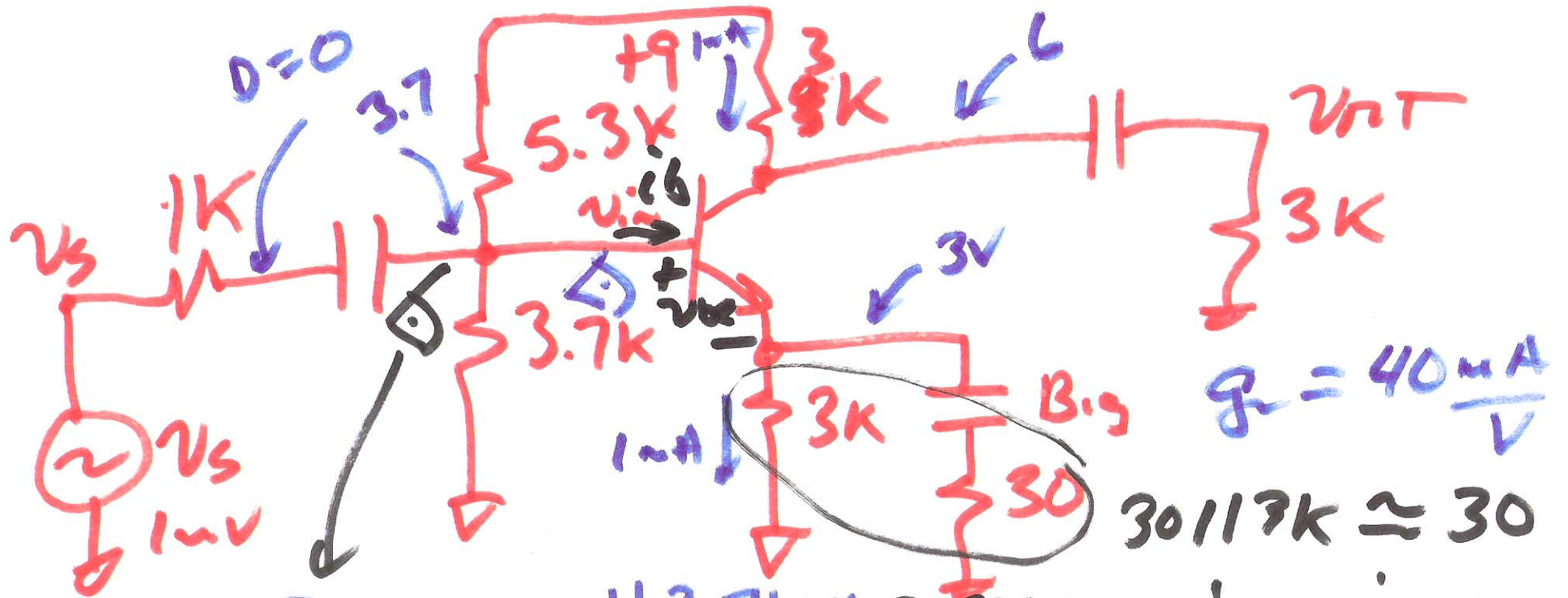

$$R_{in} = 5.3k \parallel 3.7k \parallel 5.53k$$

$$\approx 1.4k$$

$$v_i = v_{be} + i_e \cdot 3k \parallel 30$$


$$i_c = i_b \cdot \beta$$

$$i_e = (\beta + 1) i_b$$


$$v_i = \frac{i_c}{g_m} + i_e \cdot 30$$

$$\frac{v_i}{i_b} = R_{in \text{ to base}} = i_b \left(\frac{\beta}{g_m} + (\beta + 1) \cdot 30 \right)$$
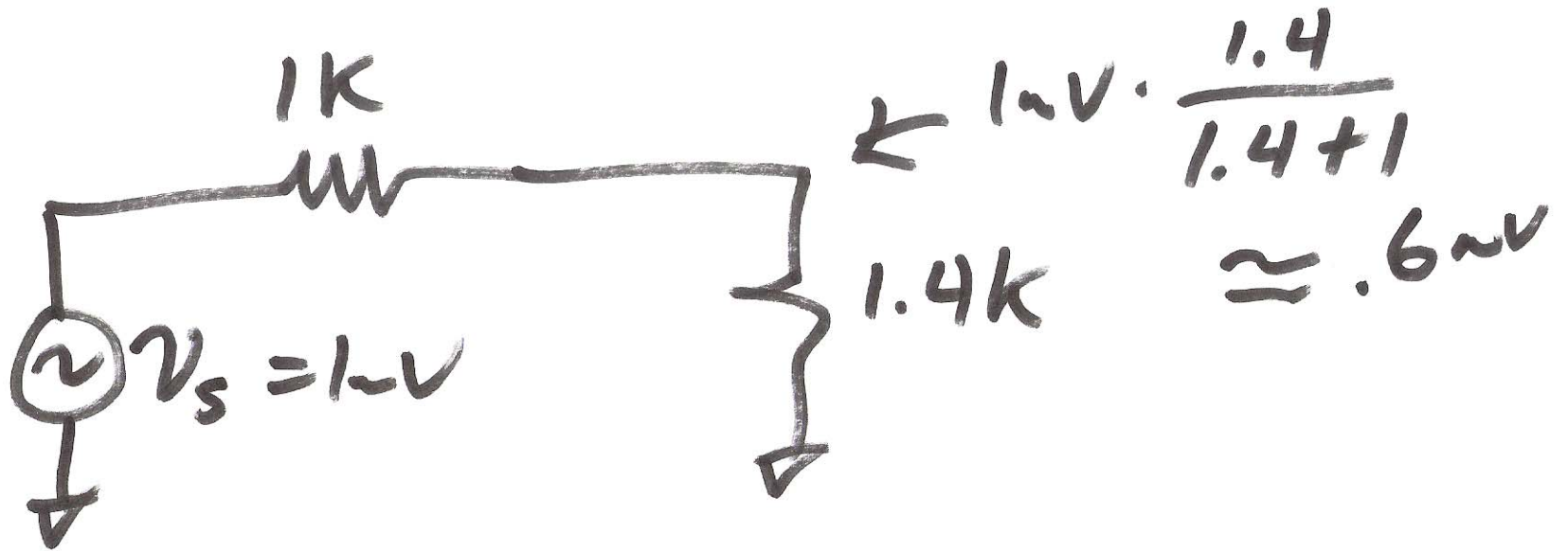
$$\begin{aligned}
 R_{into\ base} &= \frac{100}{.040} + 101(30) \\
 &= 2.5k + 3030 \\
 &= 5.53k
 \end{aligned}$$



5)

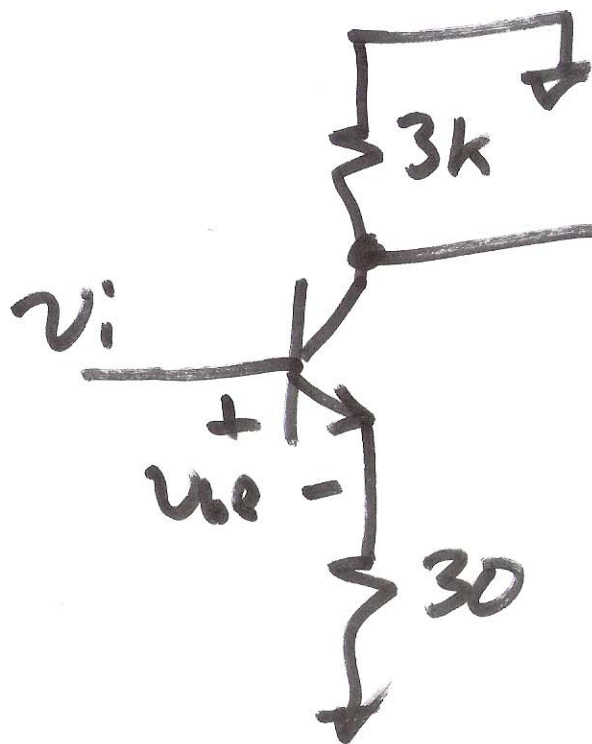

$$v_o = -i_c \cdot 1.5k$$

$$i_c / g_m$$


$$v_i = v_{be} + i_c \cdot 30$$

$$\frac{v_o}{v_i} = \frac{-1.5k}{\frac{1}{g_m} + 30}$$


$$= \frac{-1.5}{55} \boxed{\approx -27}$$

6)

Common-Emitter + 9V

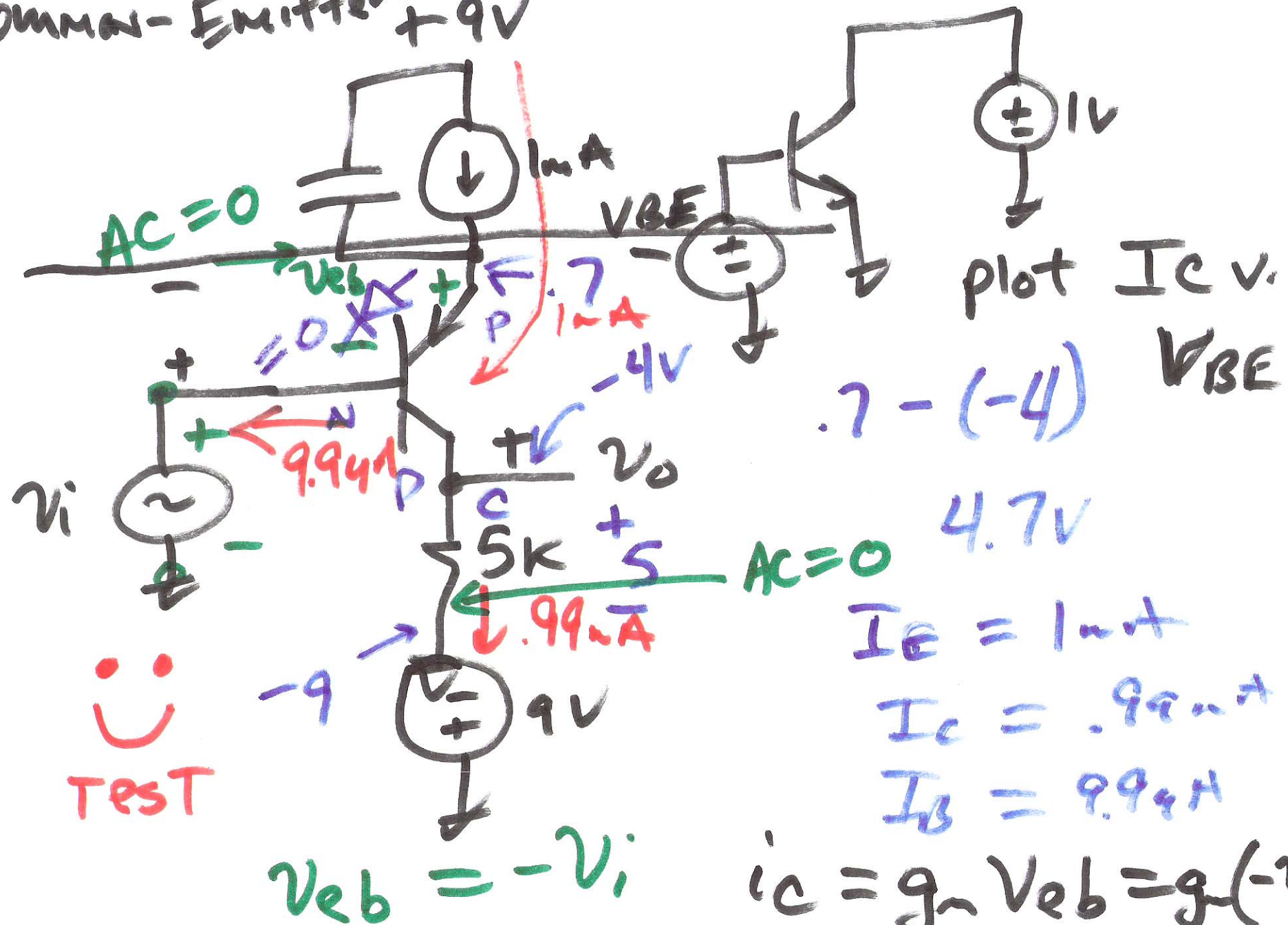

7)

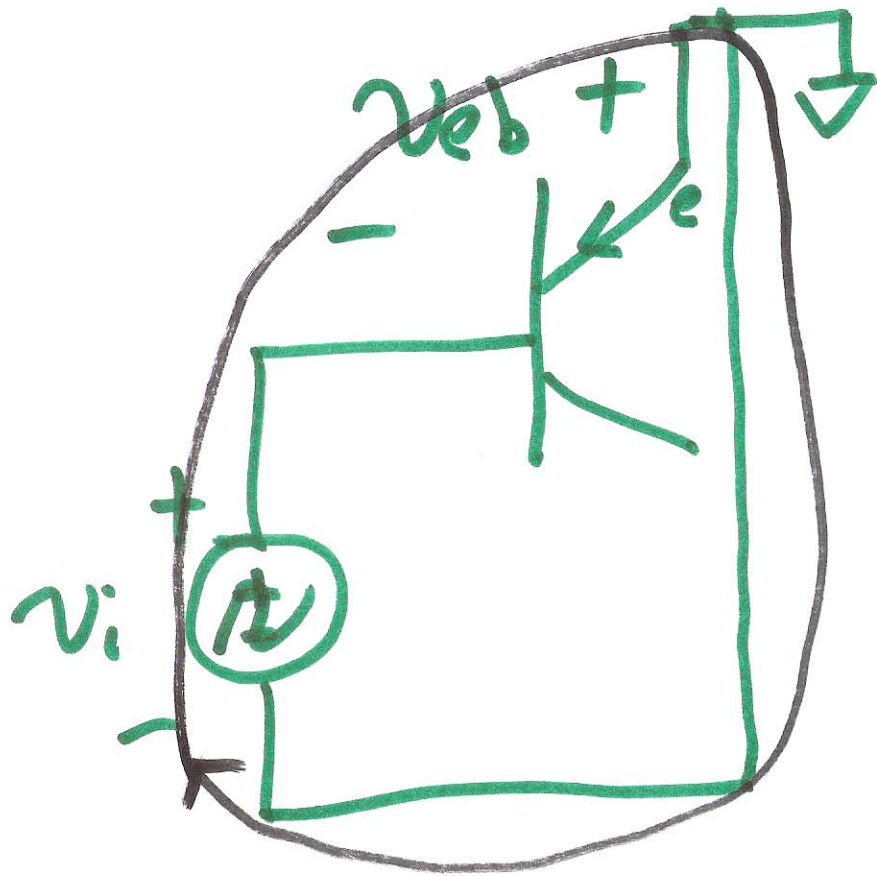

$$v_i + v_{eb} = 0$$


$$v_i = -v_{eb}$$

$$\frac{v_o}{v_i} = \frac{g_c \cdot 5k}{-i_c / g_m}$$

$$= -g_m \cdot 5k$$

8)

Common Collector

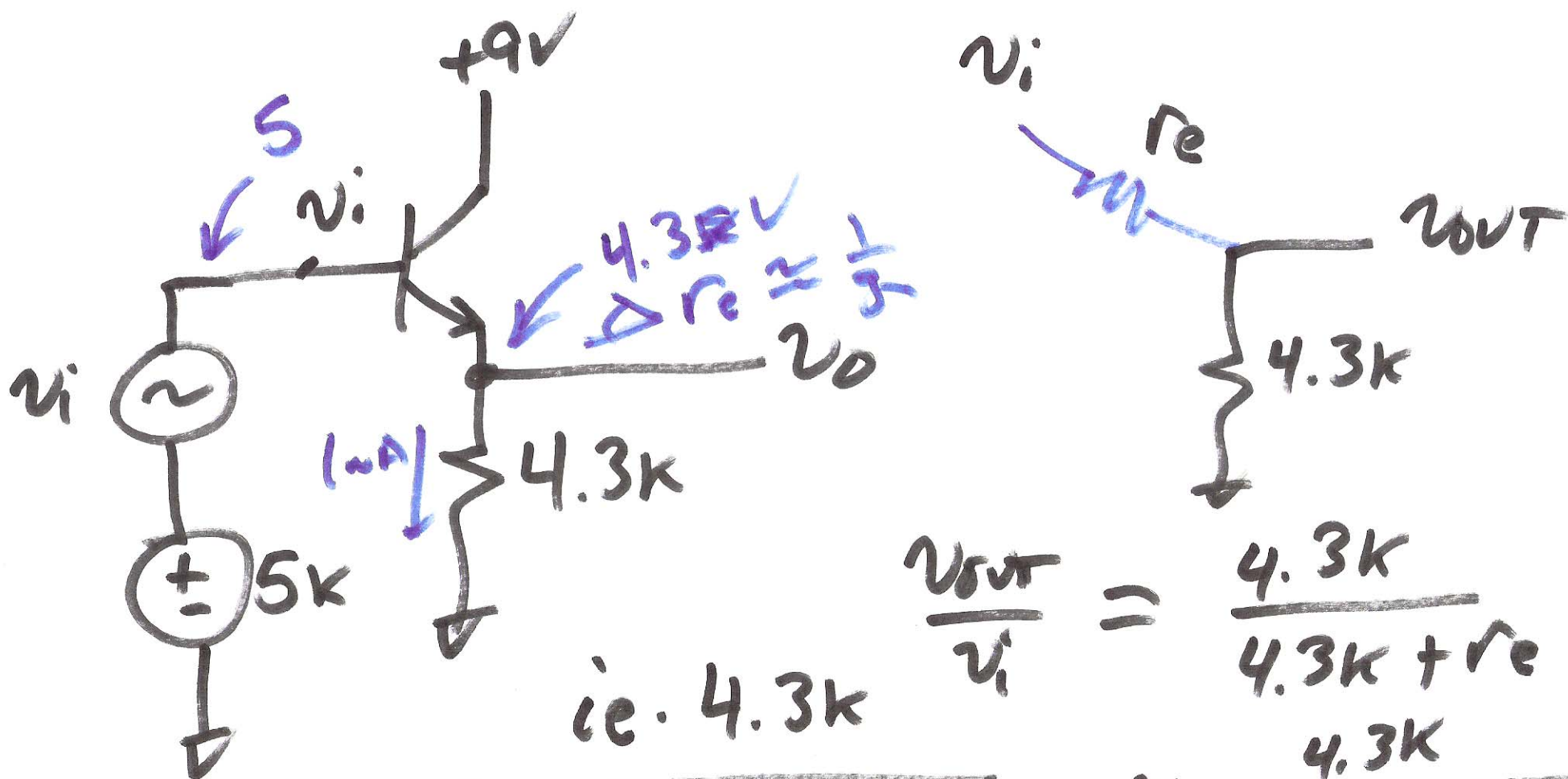

$$\frac{v_o}{v_i} = \frac{i_e \cdot 4.3k}{v_{be} + i_e \cdot 4.3k} \approx \frac{4.3k}{4.3k + r_e}$$

$$v_{be} = \frac{i_c}{g_m} = \frac{\alpha i_e}{g_m} = \frac{i_e}{r_e}$$

$$\frac{v_o}{v_i} = \frac{4.3k}{4.3k + \frac{1}{g_m}} \approx \frac{4.3k}{4.3k + \frac{1}{5}} \approx \frac{4.3k}{4.3k + 0.2k} \approx \frac{4.3k}{4.5k} \approx 0.95$$

9)

