

EE 320

Lecture 3

1/30/2013


Ideal op-Amp

open loop gain $\rightarrow A_{OL} = \infty$
NO CURRENT into + or - terminals


Real op-AMPS

finite op-Amp A_{OL}
input-referred offset
 $\rightarrow$ GAIN. BW = f_{UN}

finite A_{OL}

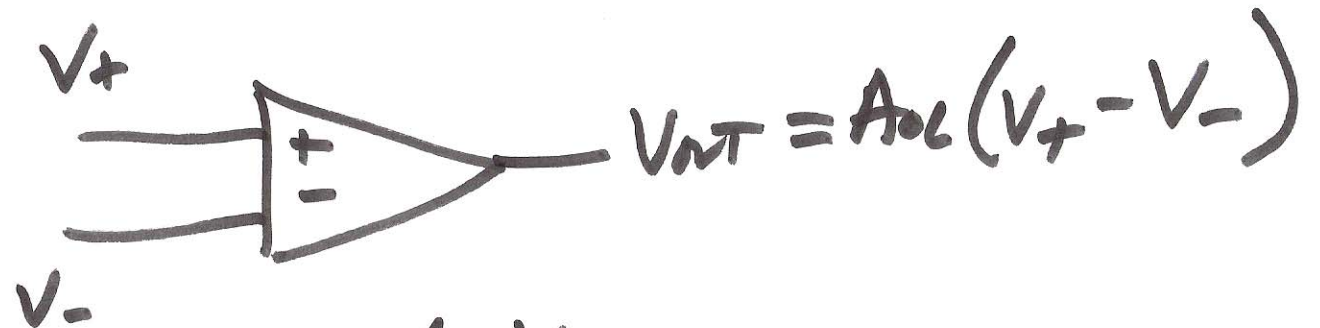

$$V_+ \neq V_-$$


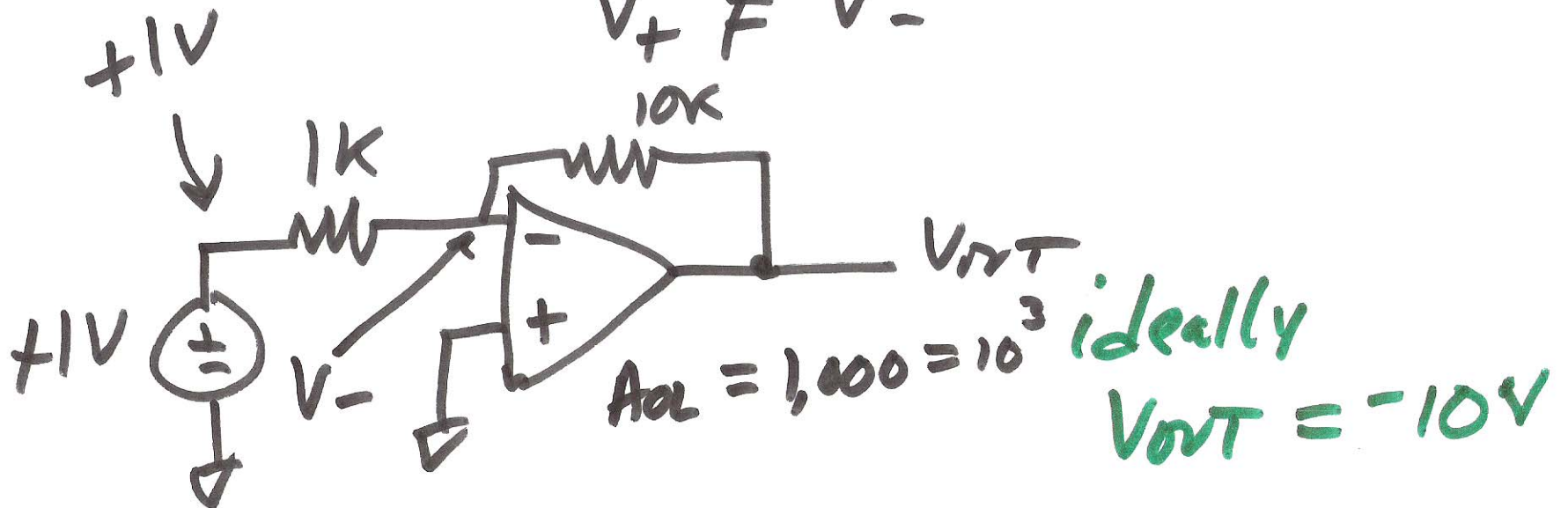


$$\frac{1 - V_-}{1K} = \frac{V_- - V_{out}}{10K}$$

$$V_{out} = 10^3(0 - V_-)$$

$$V_- = -\frac{V_{out}}{10^3}$$

ideally $V_{out} = -10V$

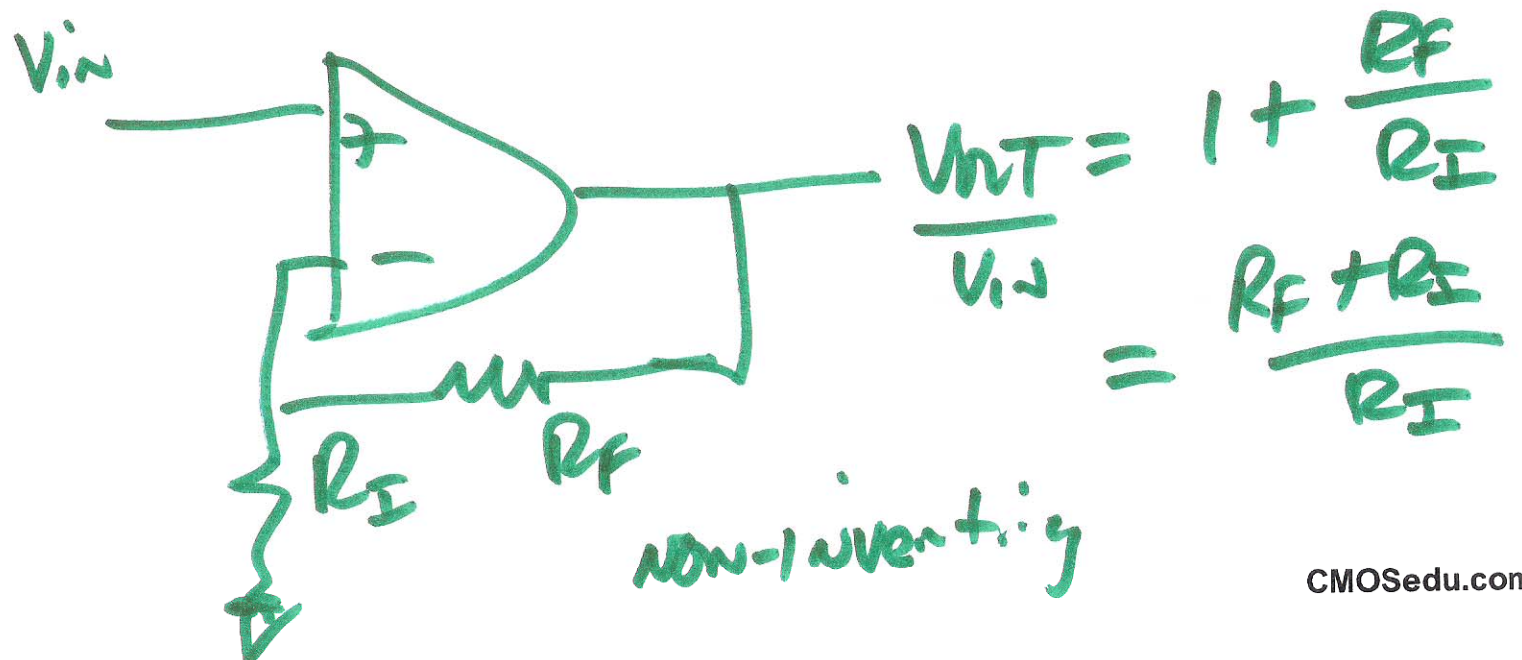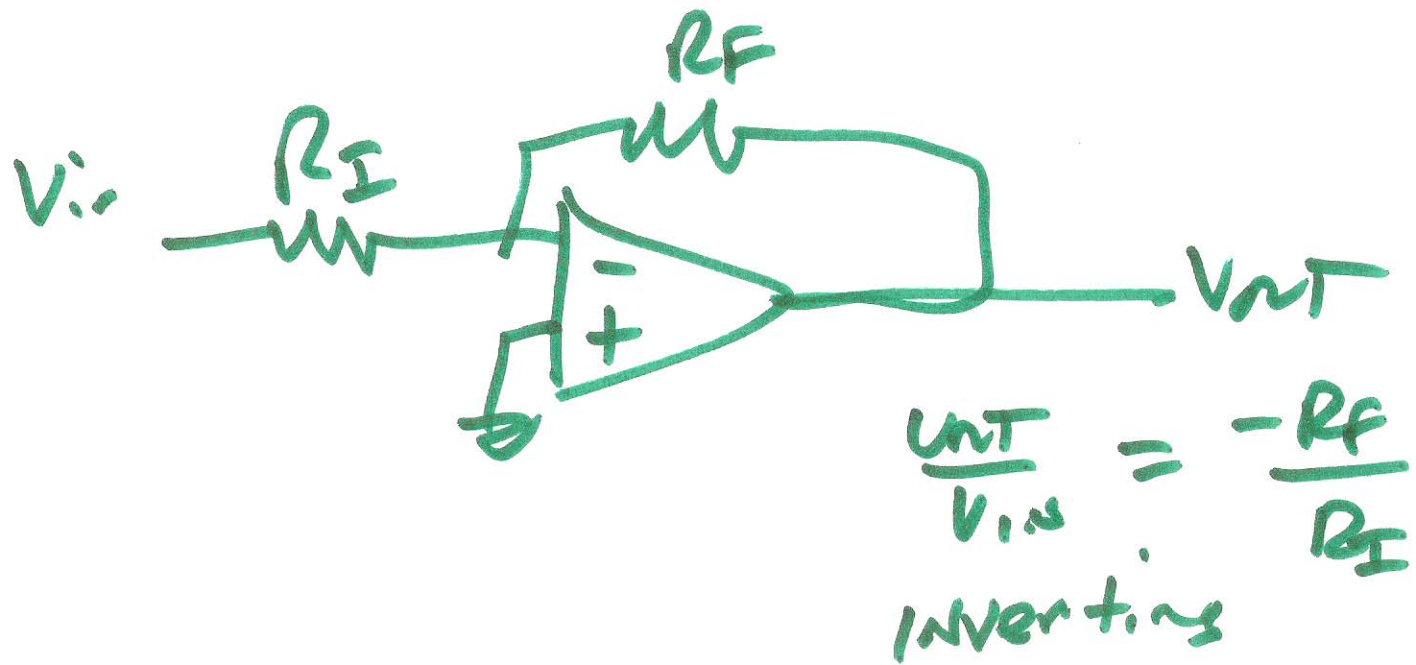

3)



$$10 \left(1 - \left(-\frac{V_{out}}{10^3} \right) \right) = \frac{-V_{out}}{10^3 \cdot 10^2} \cdot \frac{V_{out}}{10^3}$$

$$10 + \frac{V_{out}}{10^2} = -V_{out} \left(\frac{1}{10^3} + 1 \right)$$


$$10 = -V_{out} \left(1 + \frac{1}{10^2} + \frac{1}{10^3} \right)$$

$$V_{out} = \frac{-10}{1.011} = \underline{\underline{-9.891}}$$

offset voltage

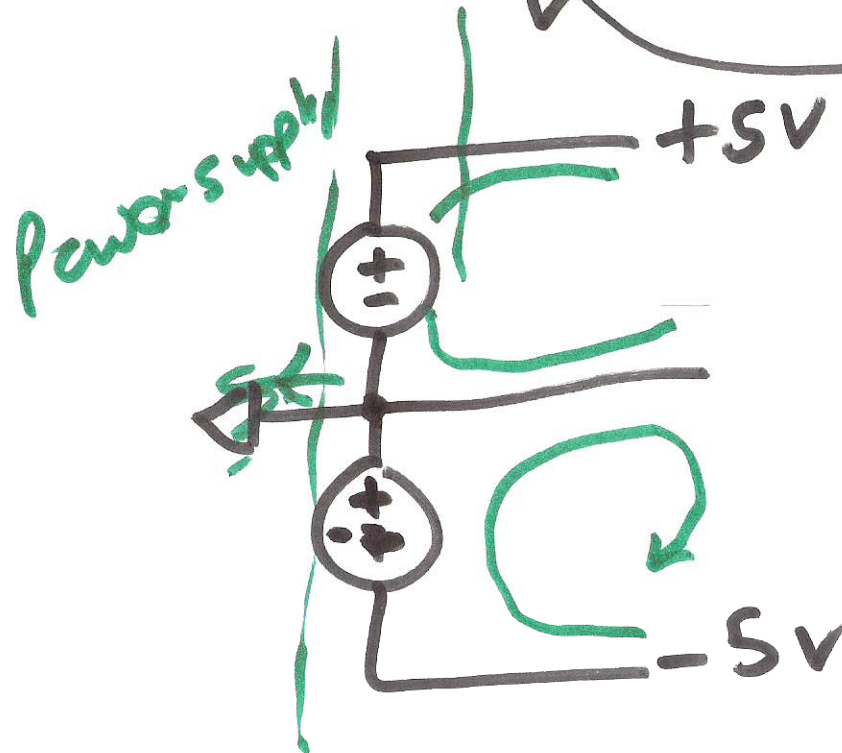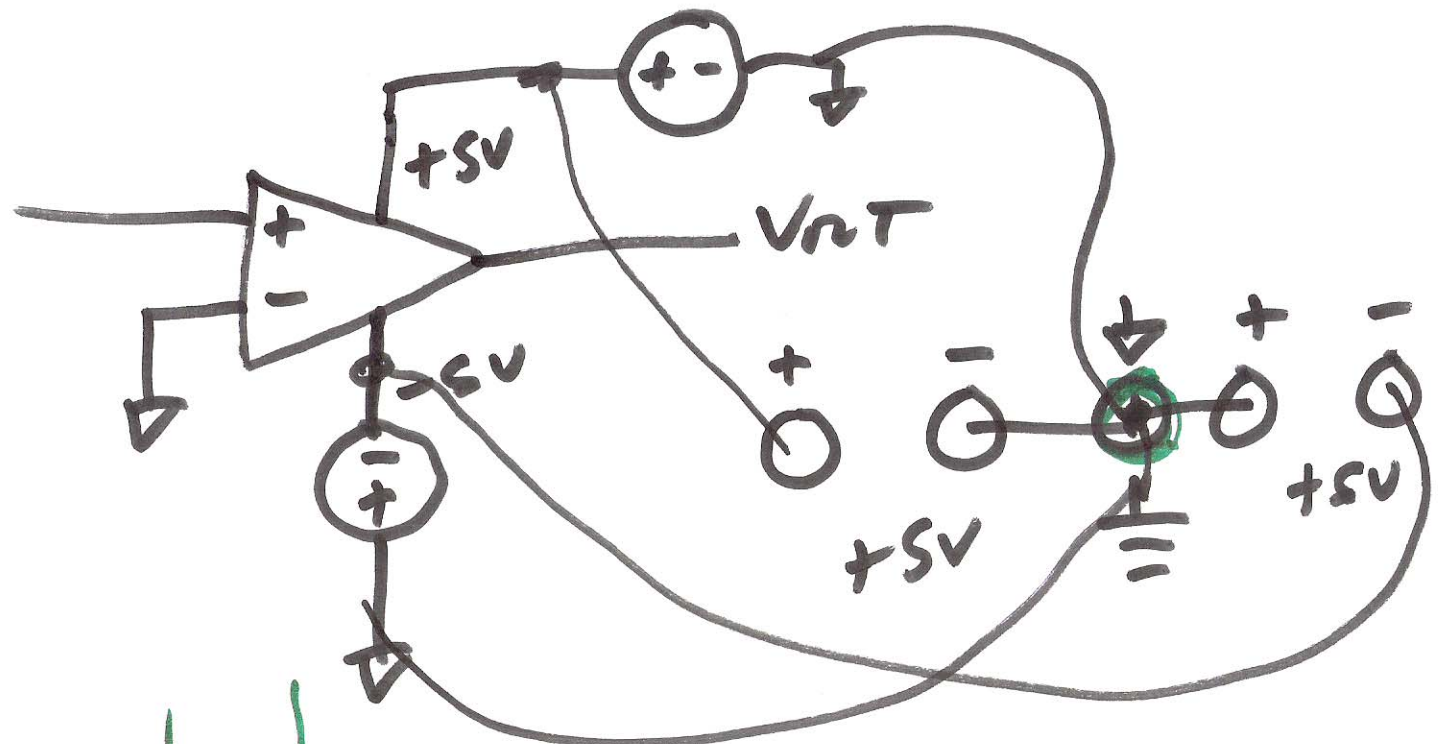


Offset Voltage

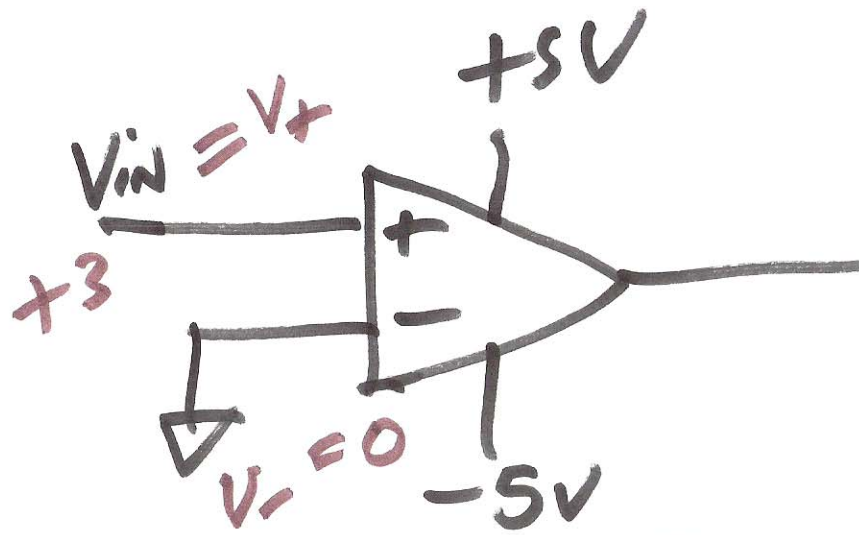

$$V_{out} = A_{OL} \cdot (V_+ - V_-)$$


$$V_{out} = 10^3 (-3 - 0)$$

$$V_{out} = 10^3 (3 - 0)$$

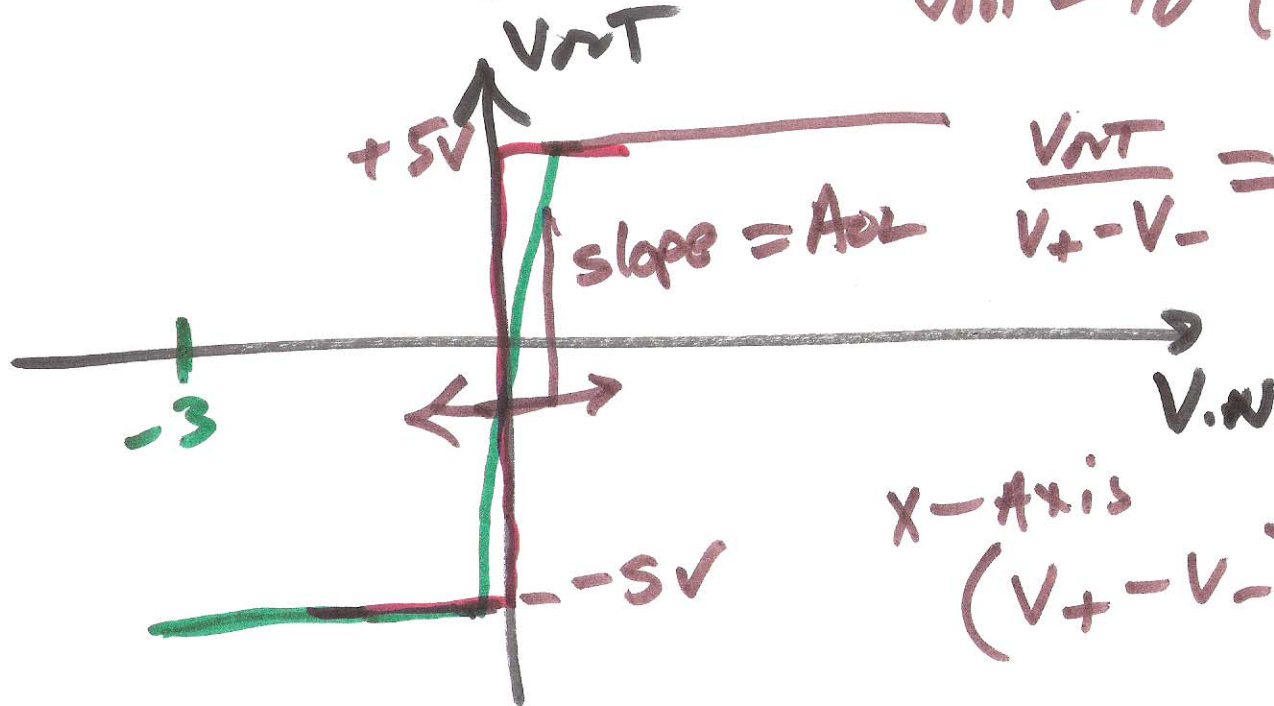


$$\frac{V_{out}}{V_+ - V_-} = A_{OL}$$

X -axis
 $(V_+ - V_-)$



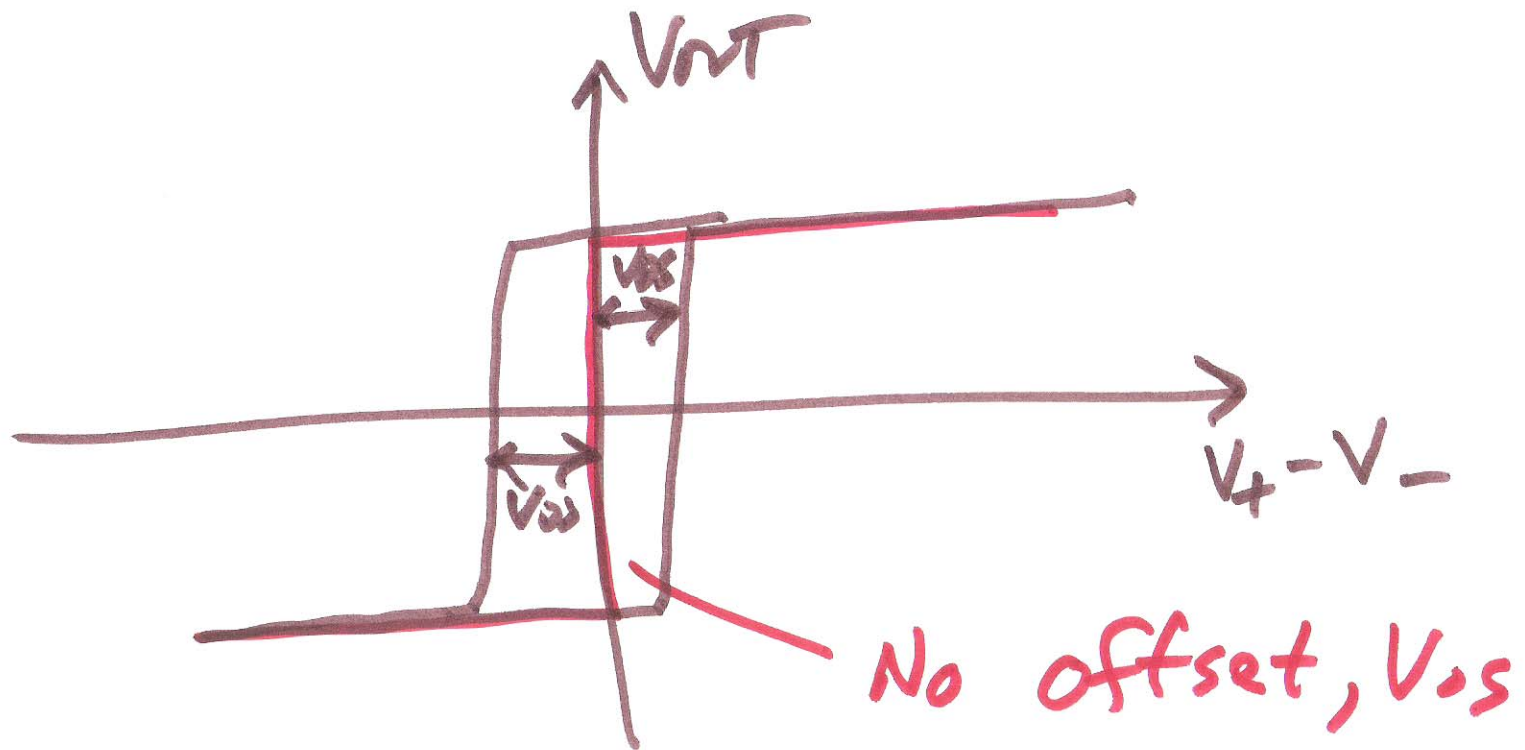


WAY we model offset


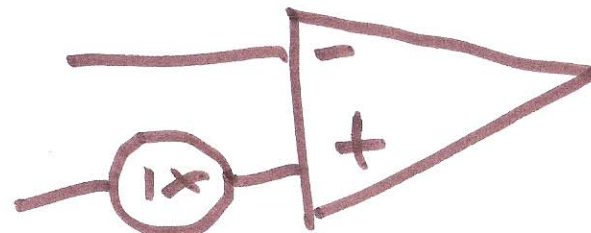



V_{os} can be neg. or pos.

$$V_{OS} = +10\text{mV}$$

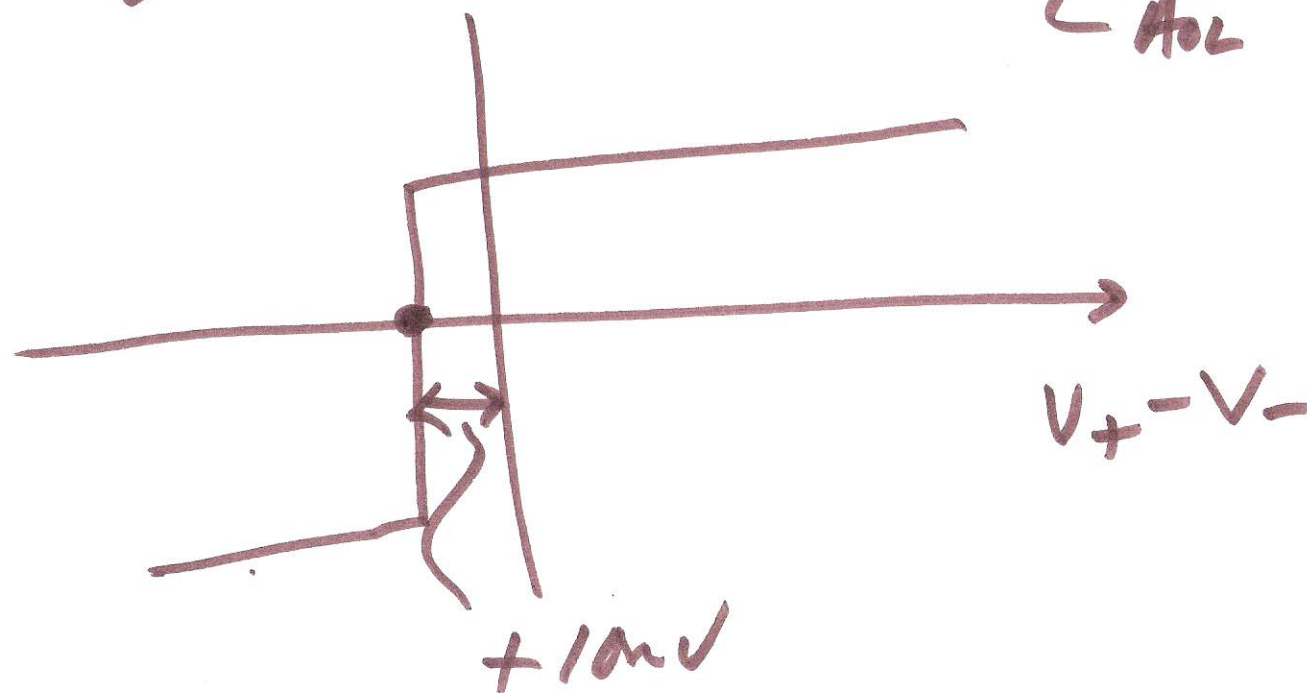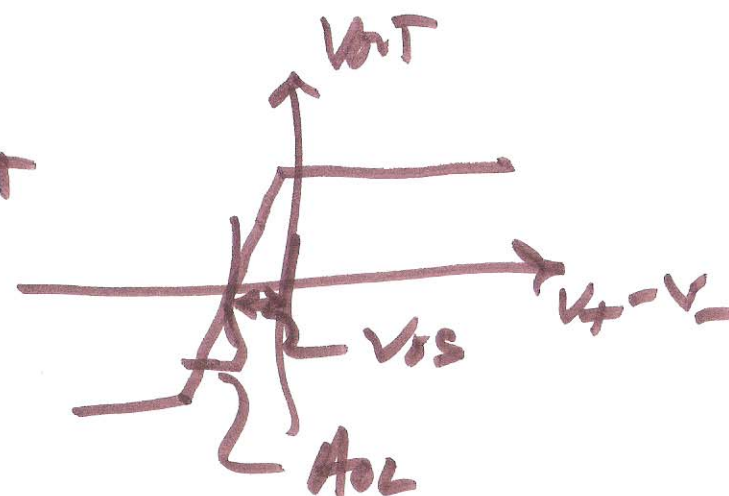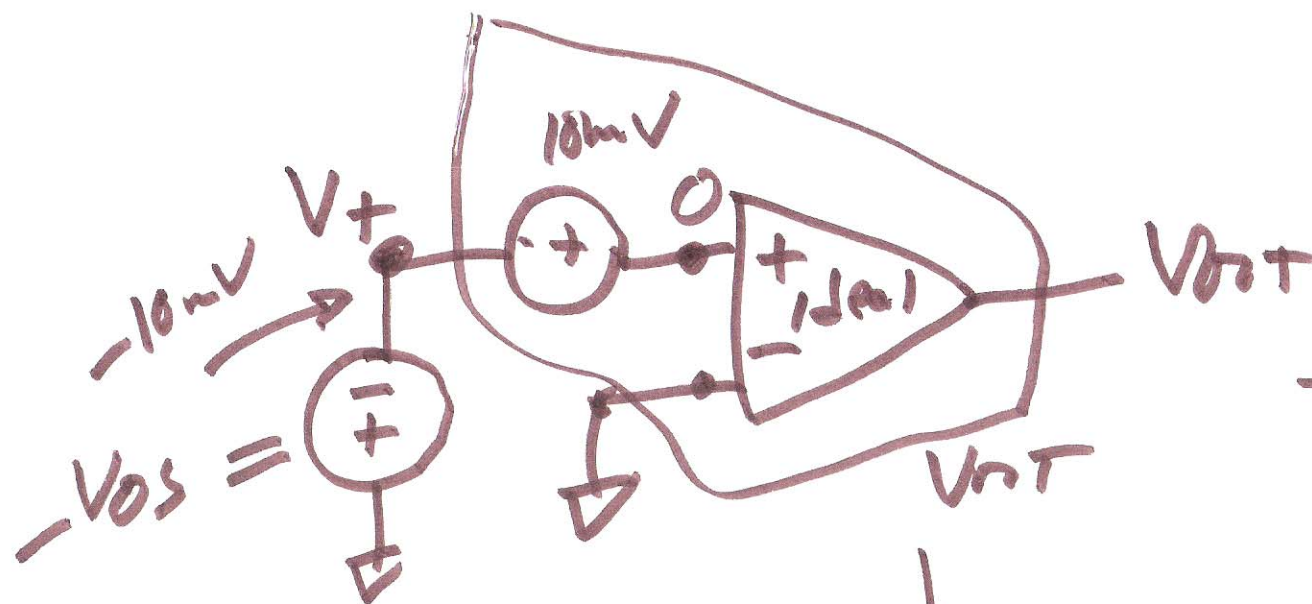


8)

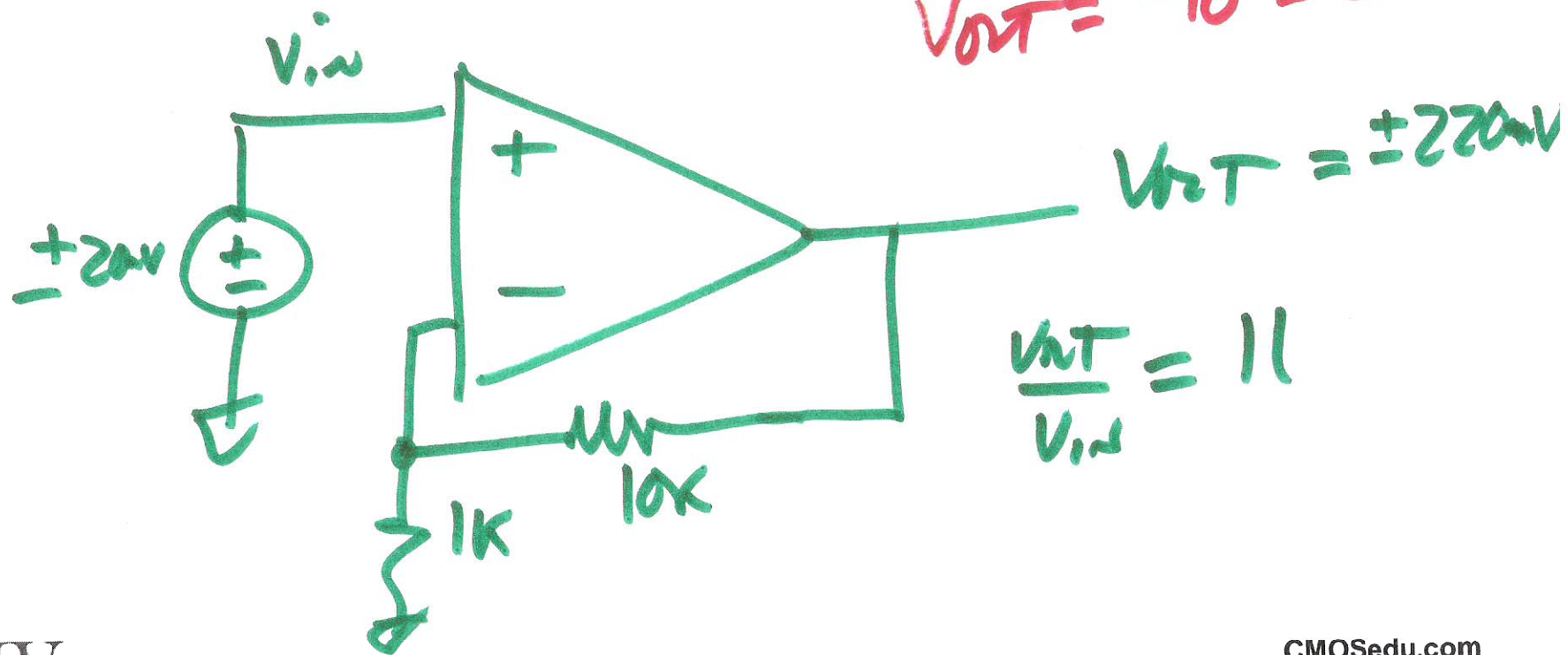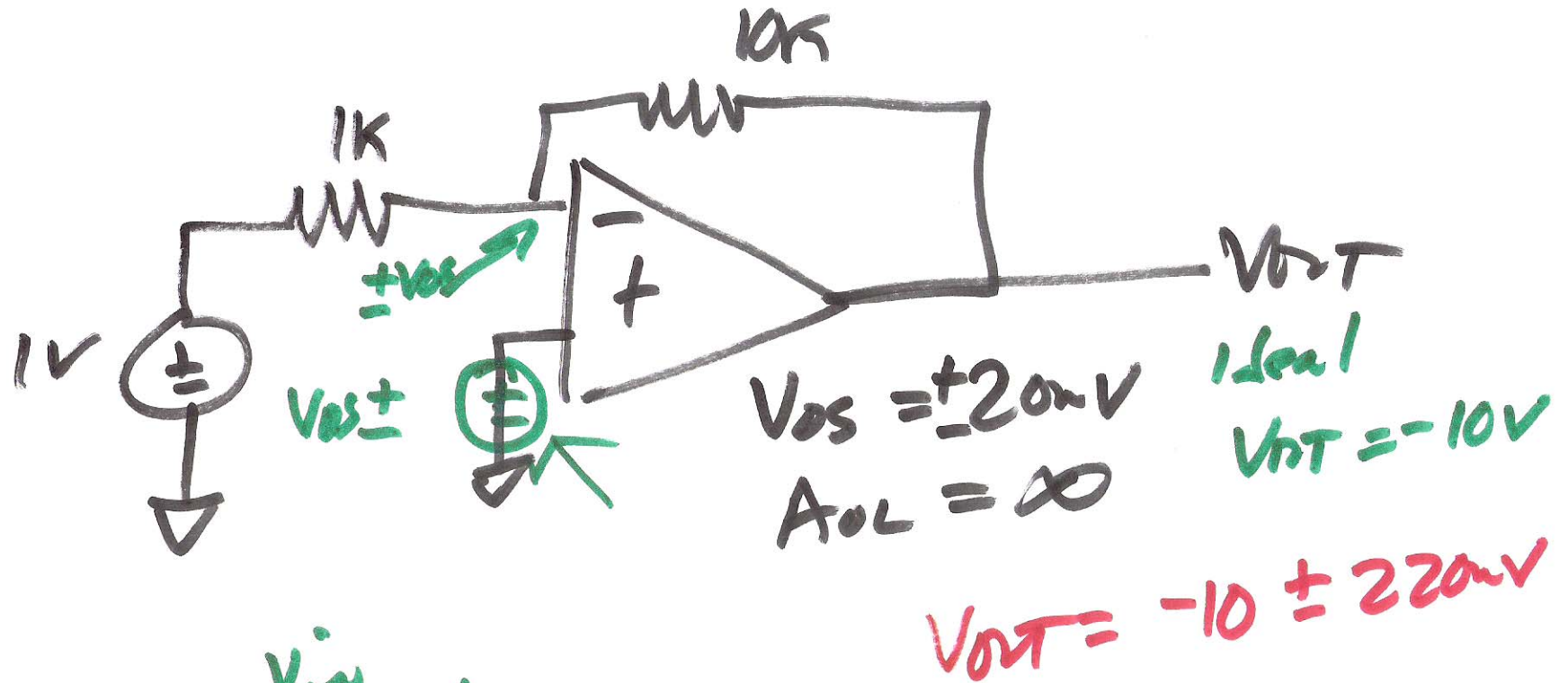

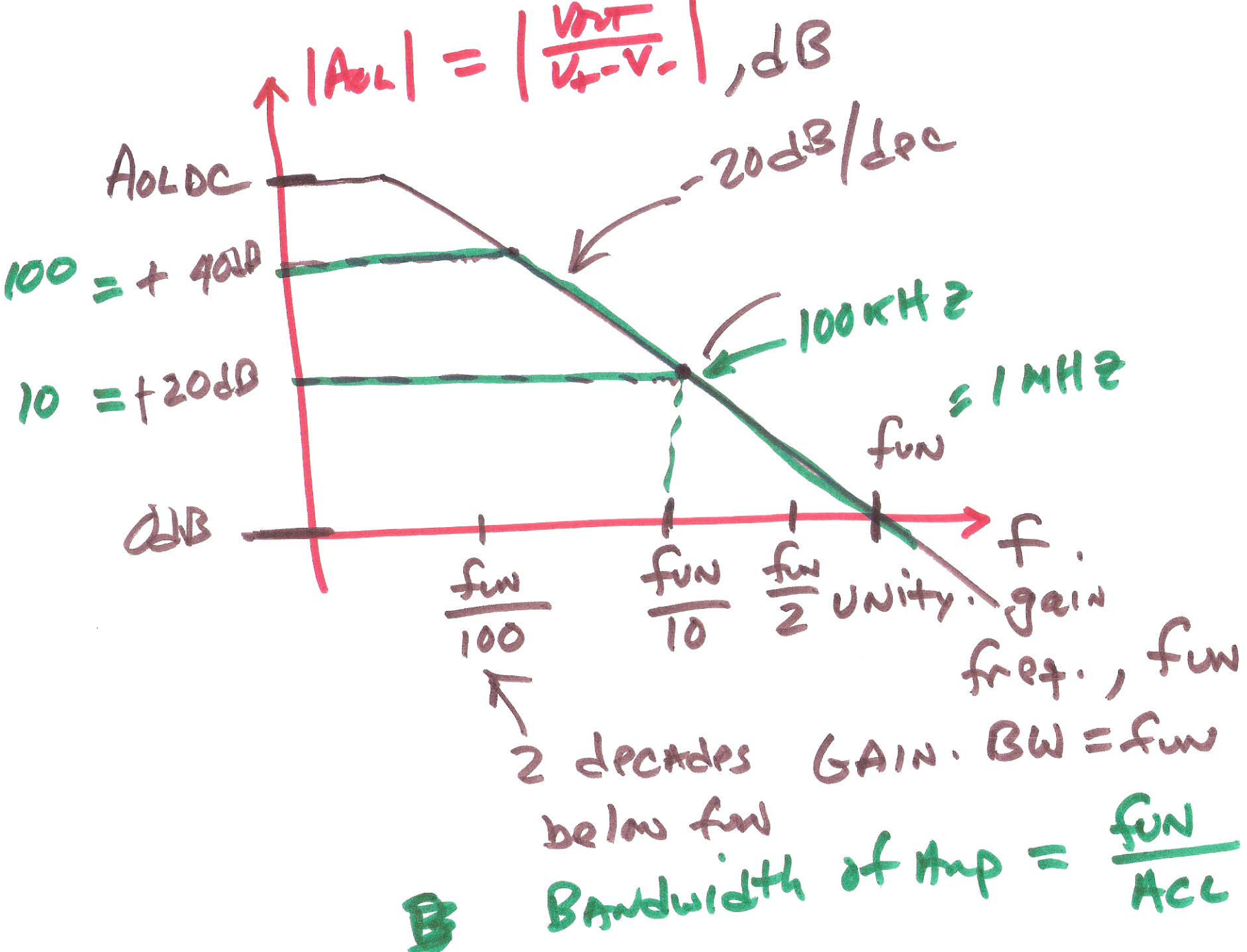

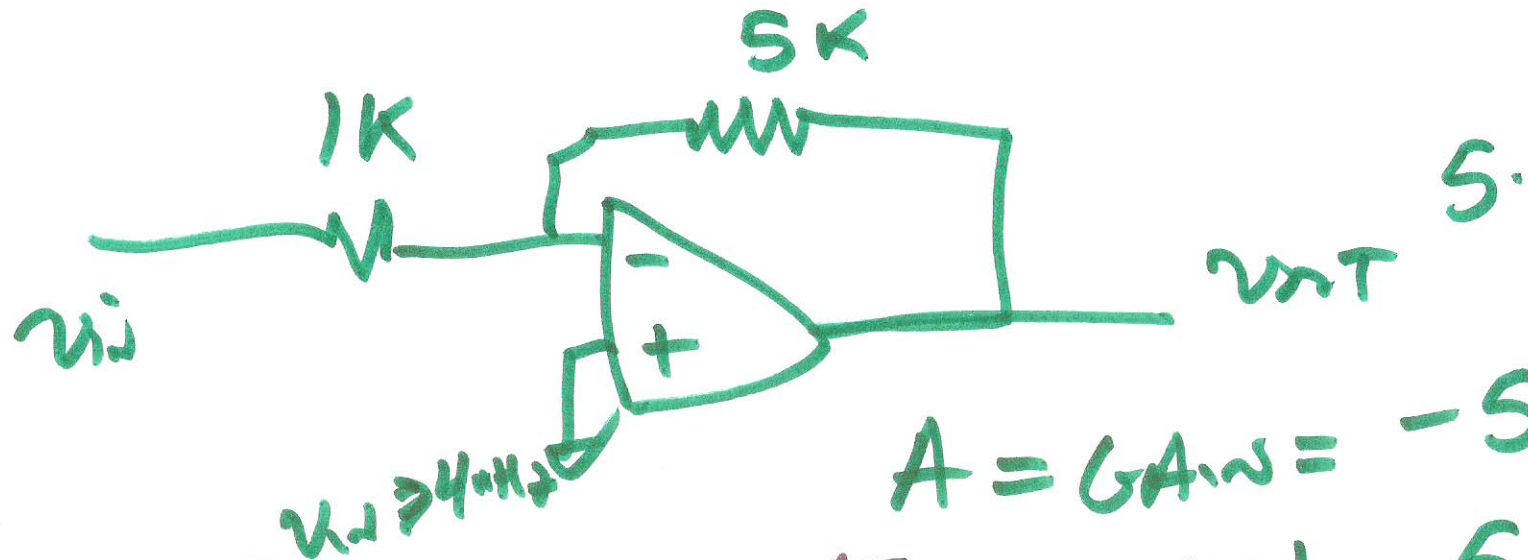10)


$$\text{op-amp } f_{\text{un}} = \text{gain} \cdot \text{BW} = 20 \text{ MHz}$$



$$A = \text{Gain} = -5$$

$$|A| = 5$$



$$\text{BW}|_{\text{CL}} = \frac{20 \text{ MHz}}{5} = 4 \text{ MHz}$$

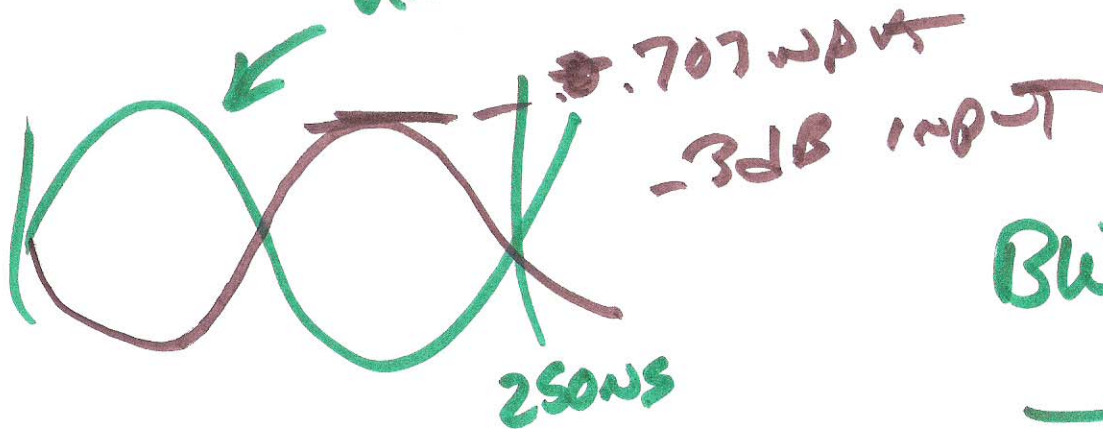

11)

$$A_{OL} = 10^3 \quad \text{Gain} \cdot BW = 20 \text{ MHz}$$

$$20 \log 10^3$$

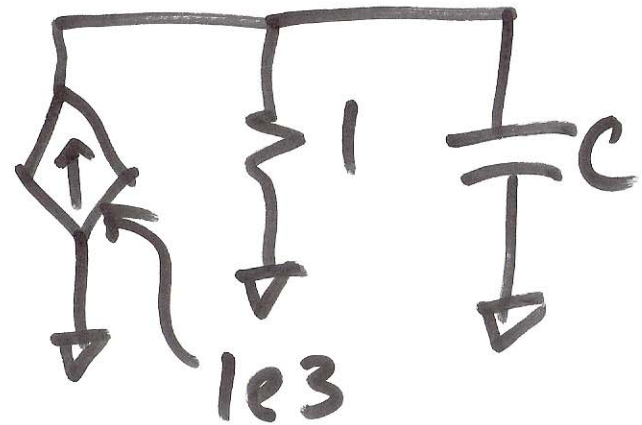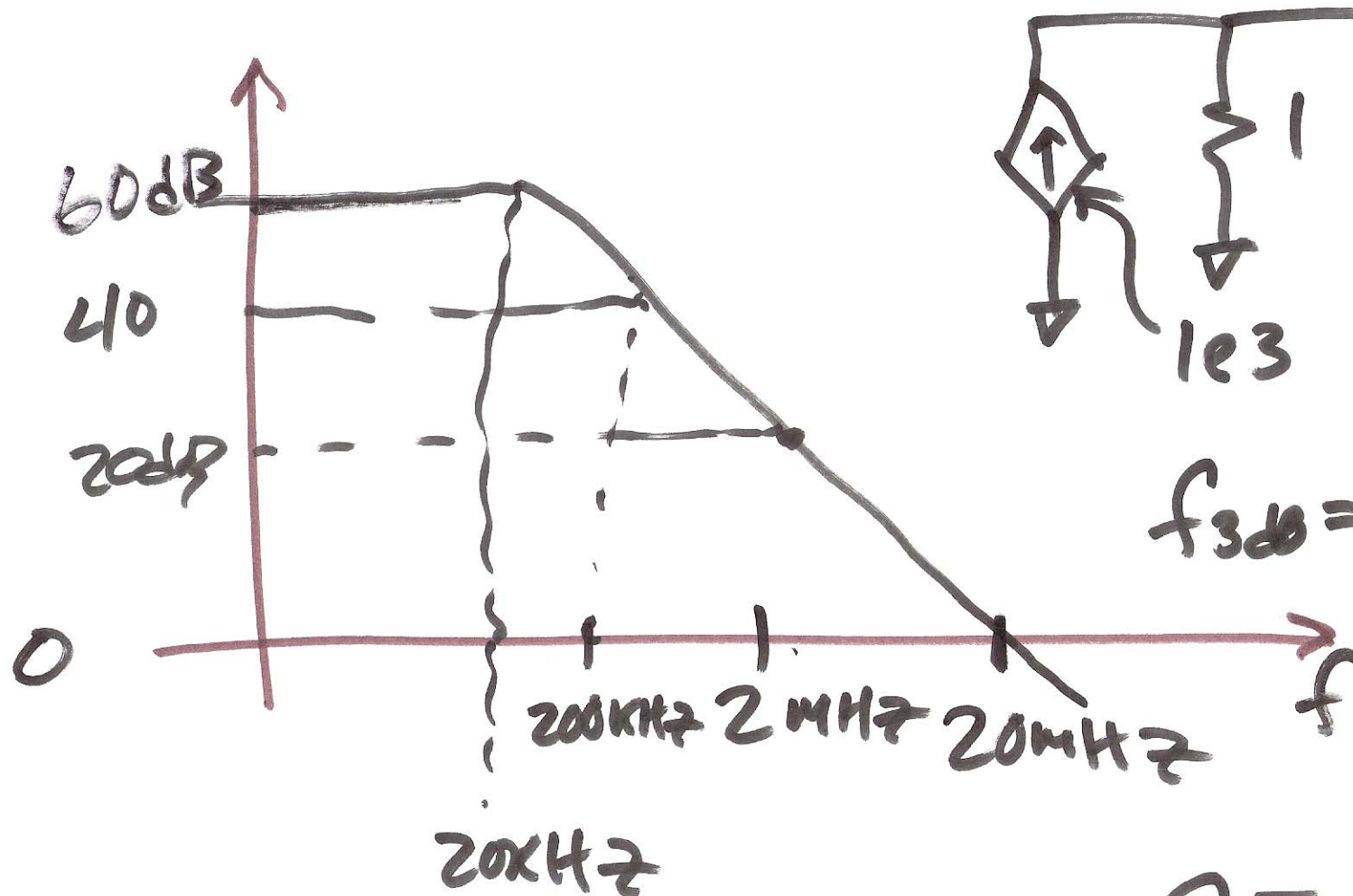

$$f_{3dB} = 20\text{K} = \frac{1}{2\pi \cdot 1C}$$

$$C = \frac{1}{2\pi \cdot 20\text{K}}$$

(12)