

# Low-Voltage Op-Amp

Tyler Ferreira

EE 420

Final Project

The objective of this project is to design a low-voltage op-amp, one that can operate with a VDD down to 2V while driving a 10pF and 1k load. I will use On Semiconductor's C5 process.

My design should be able to satisfy the following requirements:


- DC open-loop gain > 80dB under all load and VDD conditions
- Gain-bandwidth product should be > 1 MHz
- CMRR > 90dB at 100 kHz
- PSRR > 90dB at 100 kHz
- Slew-rate with maximum load > 1V/microsecond
- Input CMR extends above VDD and below ground
- Output swing within 100 mV of VDD and ground

I will use the following models text for my LTspice simulations:

NMOS				PMOS			
.MODEL NMOS NMOS (				.MODEL PMOS PMOS (			
+VERSION = 3.1	TNOM = 27	LEVEL = 8	TOX = 1.39E-8	+VERSION = 3.1	TNOM = 27	LEVEL = 8	TOX = 1.39E-8
+XJ = 1.5E-7	NCH = 1.7E17	VTH0 = 0.6696061	VTH0 = 0.6696061	+XJ = 1.5E-7	NCH = 1.7E17	VTH0 = -0.9214347	VTH0 = -0.9214347
+K1 = 0.8351612	K2 = -0.0839158	K3 = 23.1023856	K3 = 23.1023856	+K1 = 0.5553722	K2 = 8.763328E-3	K3 = 6.3063558	K3 = 6.3063558
+K3B = -7.6841108	W0 = 1E-8	NLX = 1E-9	NLX = 1E-9	+K3B = -0.6487362	W0 = 1.280703E-8	NLX = 2.593997E-8	NLX = 2.593997E-8
+DVT0W = 0	DVT1W = 0	DVT2W = 0	DVT2W = 0	+DVT0W = 0	DVT1W = 0	DVT2W = 0	DVT2W = 0
+DVT0 = 2.9047241	DVT1 = 0.4302695	DVT2 = -0.134857	DVT2 = -0.134857	+DVT0 = 2.5131165	DVT1 = 0.5480536	DVT2 = -0.1186489	DVT2 = -0.1186489
+U0 = 458.439679	UA = 1E-13	UB = 1.485499E-18	UB = 1.485499E-18	+U0 = 212.0166131	UA = 2.807115E-9	UB = 1E-21	UB = 1E-21
+UC = 1.629939E-11	VSAT = 1.643993E5	A0 = 0.6103537	A0 = 0.6103537	+UC = -5.82128E-11	VSAT = 1.713601E5	A0 = 0.8430019	A0 = 0.8430019
+AGS = 0.1194608	B0 = 2.674756E-6	B1 = 5E-6	B1 = 5E-6	+AGS = 0.1328608	B0 = 7.117912E-7	B1 = 5E-6	B1 = 5E-6
+KETA = -2.640681E-3	A1 = 8.219585E-5	A2 = 0.3564792	A2 = 0.3564792	+KETA = -3.674859E-3	A1 = 4.77502E-5	A2 = 0.3	A2 = 0.3
+RDSW = 1.387108E3	PRWG = 0.0299916	PRWB = 0.0363981	PRWB = 0.0363981	+RDSW = 2.837206E3	PRWG = -0.0363908	PRWB = -1.016722E-5	PRWB = -1.016722E-5
+WR = 1	WINT = 2.472348E-7	LINT = 3.597605E-8	LINT = 3.597605E-8	+WR = 1	WINT = 2.838038E-7	LINT = 5.528807E-8	LINT = 5.528807E-8
+XL = 0	XW = 0	DWG = -1.287163E-8	DWG = -1.287163E-8	+XL = 0	XW = 0	DWG = -1.606385E-8	DWG = -1.606385E-8
+DWB = 5.306586E-8	VOFF = 0	NFACTOR = 0.8365585	NFACTOR = 0.8365585	+DWB = 2.266386E-8	VOFF = -0.0558512	NFACTOR = 0.9342488	NFACTOR = 0.9342488
+CIT = 0	CDSC = 2.4E-4	CDSCD = 0	CDSCD = 0	+CIT = 0	CDSC = 2.4E-4	CDSCD = 0	CDSCD = 0
+CDSCB = 0	ETA0 = 0.0246738	ETAB = -1.406123E-3	ETAB = -1.406123E-3	+CDSCB = 0	ETA0 = 0.3251882	ETAB = -0.0580325	ETAB = -0.0580325
+DSUB = 0.2543458	PCLM = 2.5945188	PDIBLC1 = -0.4282336	PDIBLC1 = -0.4282336	+DSUB = 1	PCLM = 2.2409567	PDIBLC1 = 0.0411445	PDIBLC1 = 0.0411445
+PDIBLC2 = 2.311743E-3	PDIBLCB = -0.0272914	DROUT = 0.7283566	DROUT = 0.7283566	+PDIBLC2 = 3.355575E-3	PDIBLCB = -0.0551797	DROUT = 0.2036901	DROUT = 0.2036901
+PSCBE1 = 5.598623E8	PSCBE2 = 5.461645E-5	PVAG = 0	PVAG = 0	+PSCBE1 = 6.44809E9	PSCBE2 = 6.300848E-10	PVAG = 0	PVAG = 0
+DELTA = 0.01	RSH = 81.8	MOBMOD = 1	MOBMOD = 1	+DELTA = 0.01	RSH = 101.6	MOBMOD = 1	MOBMOD = 1
+PRT = 8.621	UTE = -1	KT1 = -0.2501	KT1 = -0.2501	+PRT = 59.494	UTE = -1	KT1 = -0.2942	KT1 = -0.2942
+KT1L = -2.58E-9	KT2 = 0	UA1 = 5.4E-10	UA1 = 5.4E-10	+KT1L = 1.68E-9	KT2 = 0	UA1 = 4.5E-9	UA1 = 4.5E-9
+UB1 = -4.8E-19	UC1 = -7.5E-11	AT = 1E5	AT = 1E5	+UB1 = -6.3E-18	UC1 = -1E-10	AT = 1E3	AT = 1E3
+WL = 0	WLN = 1	WW = 0	WW = 0	+WL = 0	WLN = 1	WW = 0	WW = 0
+WWN = 1	WWL = 0	LL = 0	LL = 0	+WWN = 1	WWL = 0	LL = 0	LL = 0
+LLN = 1	LW = 0	LWN = 1	LWN = 1	+LLN = 1	LW = 0	LWN = 1	LWN = 1
+LWL = 0	CAPMOD = 2	XPART = 0.5	XPART = 0.5	+LWL = 0	CAPMOD = 2	XPART = 0.5	XPART = 0.5
+CGDO = 2E-10	CGSO = 2E-10	CGBO = 1E-9	CGBO = 1E-9	+CGDO = 2.9E-10	CGSO = 2.9E-10	CGBO = 1E-9	CGBO = 1E-9
+CJ = 4.197772E-4	PB = 0.99	MJ = 0.4515044	MJ = 0.4515044	+CJ = 7.235528E-4	PB = 0.9527355	MJ = 0.4955293	MJ = 0.4955293
+CJSW = 3.242724E-10	PBSW = 0.1	MJSW = 0.1153991	MJSW = 0.1153991	+CJSW = 2.692786E-10	PBSW = 0.99	MJSW = 0.2958392	MJSW = 0.2958392
+CJSWG = 1.64E-10	PBSWG = 0.1	MJSWG = 0.1153991	MJSWG = 0.1153991	+CJSWG = 6.4E-11	PBSWG = 0.99	MJSWG = 0.2958392	MJSWG = 0.2958392
+CF = 0	PVTH0 = 0.0585501	PRDSW = 133.285505	PRDSW = 133.285505	+CF = 0	PVTH0 = 5.98016E-3	PRDSW = 14.8598424	PRDSW = 14.8598424
+PK2 = -0.0299638	WKETA = -0.0248758	LKETA = 1.173187E-3	LKETA = 1.173187E-3	+PK2 = 3.73981E-3	WKETA = 5.292165E-3	LKETA = -4.205905E-3	LKETA = -4.205905E-3
+AF = 1	KF = 0)			+AF = 1	KF = 0)		
*				*			

I started my project by designing my bias circuit. A bias circuit is used to generate known voltages to apply to the gates of my circuits transistors. The voltages generated by my bias circuit will supply/sink my circuit with a known bias current. I first built the general short channel biasing circuit and tuned my sizes and resistor according to the bias current I was looking for. I chose to use a bias current of 5uA to keep my cascode branch voltages below VDD.


Image of my bias circuit:

 

LTspice file: mybiascircuit.asc



I created a symbol to represent this circuit to be used in my op-amp schematics. This will make my op-amp schematic easier to understand.

Image of my bias circuit symbol:

 


LTspice file: mybiascircuit.asy

  Testing my bias circuit by using current mirrors:



LTspice file: biascircuit\_test.asc

 I will also vary my VDD to see how the current changes with increases in power supply voltage. By doing this simulation I will be able to see how long my bias circuit will give me the correct bias voltages.



LTSpice file: biascircuit\_test1.asc

This simulation shows the current through each branch in my bias circuit as my VDD varies from 0 to 4 V. All of my branch currents are around 5uA before the power supply reaches 2V. The current begins to rise linearly when VDD passes 3.2V. This is good for our design since the voltages we will obtain from our circuit will give us 5uA from 2V to 3.2V.


Now that I have my bias circuit I will create the schematic for my op-amp. I will use an NMOS and PMOS diff amp connected to a push-pull amplifier for my general design. This topology will ensure that my input common-mode range extends above VDD and below ground and be able to drive the given load.



The basic operation of the diff amp is to compare the inputs on nodes Vm and Vp and amplify the difference between them. This topology allows an input CMR that extends above VDD and below ground. I decided to use split length input transistors to connect a compensation capacitor that will increase my circuit stability.

The push-pull stage of my op-amp is important to be able to drive the required load and meet the slew rate specification. This is done by increasing the widths of the output transistors so that enough current may flow to the load. The amplifier will also amplify the output of the diff amp, increasing the overall gain of my op-amp.


Image of my push-pull amplifier stage:

 

LTspice file: myopamp.asc

The top PMOS and bottom NMOS are used to source/sink current through this stage and are connected to the differential amplifier. The middle transistors are connected to the bias circuit and will limit the current flowing to the input of the push-pull. The widths are half the size of the other transistors to ensure half of the current will flow through the two branches to match the total current sink of the NMOS devices and current supply of the PMOS devices.

 The symbol I made to represent my op-amp circuit:




LTspice file: myopamp.asy

The top pin is connected to VDD in my circuit and the bottom pin is connected to ground.


This symbol will be used in place of the original schematic to make the circuits easier to understand and easier to run different simulations. The first simulation I will perform is the frequency response of my op-amp while varying my power supply voltage.

Frequency response schematic:

 

LTspice file: opamp\_ac\_analysis1.asc

Simulation results:

 



LTspice file: opamp\_ac\_analysis1.raw

VDD	DC Gain	Bandwidth	Phase at 0dB	Power
2	98.9dB	13.2MHz	-131°	2.16mW
3	100.2dB	13.6MHz	-136°	3.31mW
4	100.8dB	21.7 MHz	-144°	4.71mW
5	101.0dB	30.1 MHz	-149°	6.62mW

These simulations show me that I have a DC open-loop gain > 80dB and a gain-bandwidth product > 1MHz. My design has satisfied two of the requirements so far. One tradeoff I had to make was removing the split length transistor compensation capacitor to satisfy the CMRR requirement. Since I removed these capacitors I lost some high frequency stability and pushed my gain-bandwidth product further out.

I will now perform a simulation to show my op-amps common-mode rejection ratio.

 
 
Common-mode rejection ratio is important for amplifier design because it allows the amplifier to reject input noise to the system. Below is the schematic and simulation that I made to show the CMRR.



LTspice file: opamp\_CMRR.asc



In the above simulation I could obtain a common-mode rejection ratio of 91.7dB at 100kHz satisfying the CMRR requirement.

  I will now check the power supply rejection ratio of my op-amp. Below is the schematic and simulation for the positive power supply rejection ratio.



LTspice file: opamp\_PSRR\_plus.asc

 
 
Below is the schematic and simulation for the negative power supply rejection ratio.



LTspice file: opamp\_PSRR\_minus.asc

Looking at the PSRR plus and minus of my op-amp I was not able to obtain the design requirement of the project. After many trials I was not able to obtain PSRR > 90dB at 100kHz while still meeting the other 6 requirements.

  The next requirement for my project is to have a slew-rate greater than 1V/us. The slew-rate is how quickly my circuit will charge and discharge a capacitive load. Below is the schematic and corresponding simulation results.





LTspice file: opamp\_transient2.asc

Table of cursor values for the above simulation:

VDD	2	3	4	5
Slew-Rate	2.50V/us	5.81V/us	8.68V/us	12.3V/us

I was able to get my op-amp design to have a slew-rate greater than 1V/us. I can also fix the overshoot of the output by adding compensation capacitors to the split length transistors at the cost of my CMRR.

  I will now test my op-amps output swing by putting the op-amp in a follower configuration and sweeping the input voltage and comparing it the output which changes in VDD.





LTspice file: opamp\_dc\_sweep1.asc

Table with cursor values for the above simulation:

VDD	0V	1V	2V	3V	4V	5V
Vin	0V	575.5mV	1.95V	2.95V	3.92V	4.92V
Vout	0V	112.3mV	1.92V	2.93V	3.92V	4.92V

  I will also do a simulation holding the minus terminal at a constant voltage and varying the plus terminal. This will show the full output swing of my op-amp.





LTspice file: opamp\_dc\_sweep2.asc

In my simulation my output will swing from 2.31mV to 1.99V which is within 100mV of ground and VDD respectively. My op-amp satisfies my output swing design requirement.

I will test the stability of my output when there is a pulsed input. I will do this by putting my op-amp in the follower configuration and pulse the positive terminal. I will compare the output signal to my input signal.

Schematic:

  



LTspice file: opamp\_transient1.asc

I have some ringing on my output which can be lowered by changing the lengths of my bias transistors. If I decrease the length of the bias current sources the ringing will lower. I can also add compensation capacitors to the split length transistors to lower the ringing.



MOSFET Parameters followed by the simulations I used to obtain them:

Parameter	NMOS Device	PMOS Device	Comments
Bias current, ID	$5\mu A$	$5\mu A$	Chosen Bias ID
W/L	$60\mu/1.2\mu$	$180\mu/1.2\mu$	Selected
Vds,sat and Vsd,sat	25mV	25mV	Found in ro sim
Vovn and Vovp	30mV	30mV	1.5% VDD
Vgs and Vsg	730mV	930mV	Vth+Vov
Vthn and Vthp	700mV	900mV	Found in sims
C'ox	$2.5fF/\mu m^2$	$2.5fF/\mu m^2$	$\frac{\epsilon_{ox}}{t_{ox}}$
Coxn and Coxp	$180fF$	$540fF$	C'ox *WL
Cgsn and Csgp	$120fF$	$360fF$	$\frac{2}{3}Cox$
Cgdn and Cdgp	$12fF$	$52.2fF$	CGDO * W
gmn and gmp	148uA/V	136uA/V	Found in sims
ron and rop	$1.14M\Omega$	$1.06M\Omega$	Found in sims
gmn*ron and gmp*rop	168V/V	144V/V	
$\lambda_n$ and $\lambda_p$	$0.175V^{-1}$	$0.188V^{-1}$	$\frac{1}{I_{D,sat} * r_o}$
$f_{Tn}$ and $f_{Tp}$	177.8MHz	64.56MHz	Found in sims



## NMOS VGS Curve

  



## NMOS Output Resistance

  



## NMOS Transconductance

  



## NMOS Transition Frequency

  



## PMOS VSG Curve

  

## PMOS Output Resistance

  

## PMOS Transconductance

  

## PMOS Transition Frequency

